
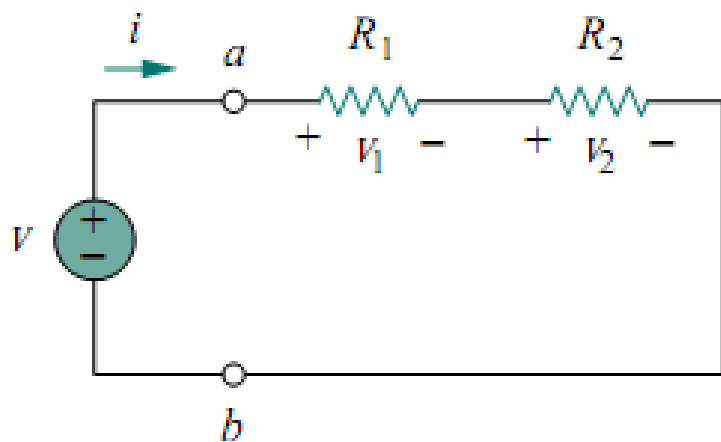


Basic Laws (2)

Series Resistors and Voltage Division

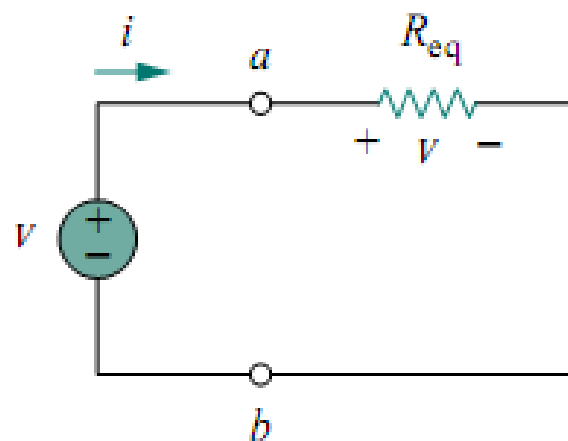


$$v = v_1 + v_2 = i(R_1 + R_2)$$



$$v = i R_{eq}$$

$$R_{eq} = R_1 + R_2$$

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

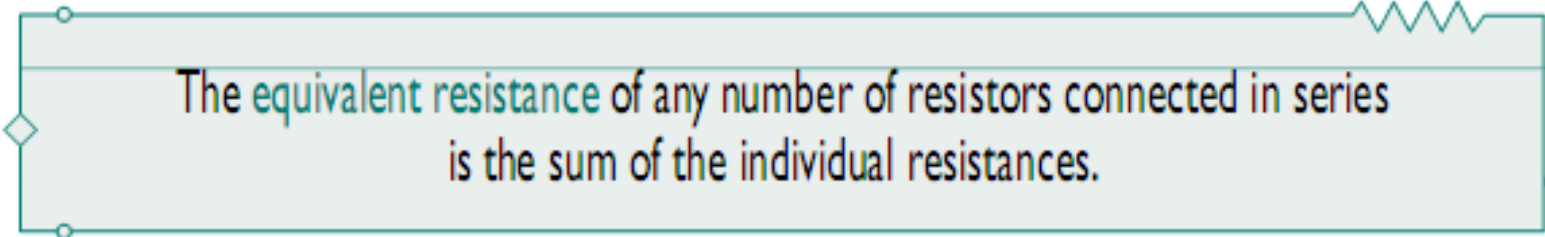
A circuit diagram showing a series connection of resistors. A horizontal wire at the top has a resistor symbol (zigzag line) on the right side. A vertical wire on the left has a diamond-shaped voltage source symbol. The text is centered within a light blue rectangular box that spans the width of the circuit diagram.

The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

Parallel Resistors and Current Division

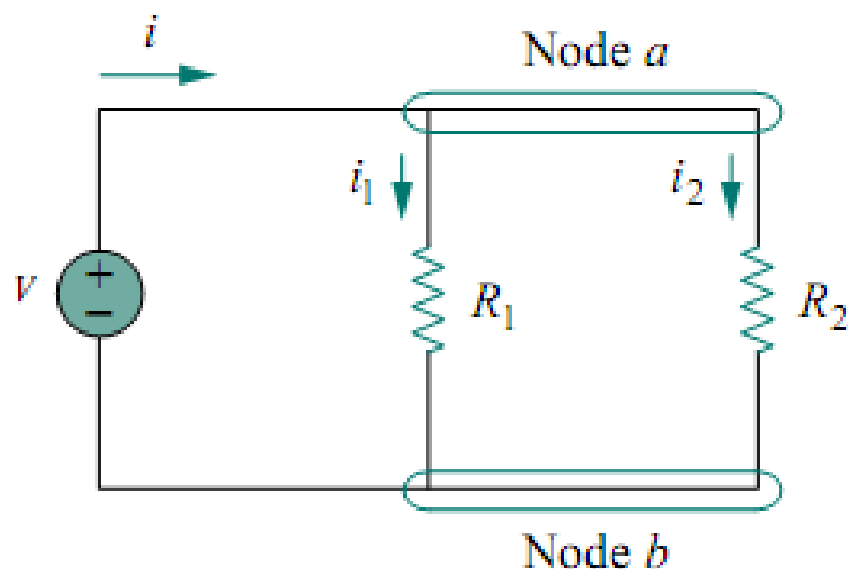

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{\text{eq}}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{\text{eq}}}$$

The equivalent resistance of two parallel resistors is equal to the product of their resistances divided by their sum.

$$v = i R_{\text{eq}} = \frac{i R_1 R_2}{R_1 + R_2}$$

$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

$$i_1 = \frac{G_1}{G_1 + G_2} i$$

$$i_2 = \frac{G_2}{G_1 + G_2} i$$

The equivalent conductance of resistors connected in parallel is the sum of their individual conductances.


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$

$$G_{\text{eq}} = G_1 + G_2 + G_3 + \cdots + G_N$$

$$i_n = \frac{G_n}{G_1 + G_2 + \cdots + G_N} i$$

Example

Find R_{eq} for the circuit.

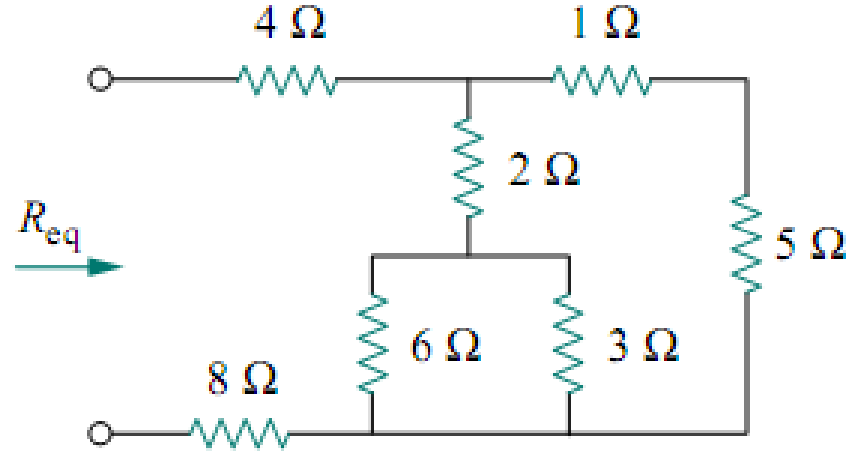


Solution

The 6- Ω and 3- Ω resistors are in parallel, so their equivalent resistance is

$$6\ \Omega \parallel 3\ \Omega = \frac{6 \times 3}{6 + 3} = 2\ \Omega$$

Also, the 1- Ω and 5- Ω resistors are in series, hence their equivalent resistance is

$$1\ \Omega + 5\ \Omega = 6\ \Omega$$

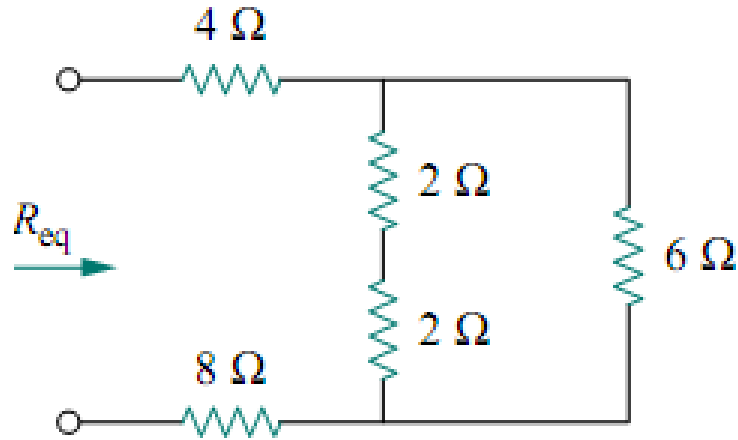


In Fig. above, we notice that the two $2\text{-}\Omega$ resistors are in series, so the equivalent resistance is

$$2\ \Omega + 2\ \Omega = 4\ \Omega$$

This $4\text{-}\Omega$ resistor is now in parallel with the $6\text{-}\Omega$ resistor; their equivalent resistance is

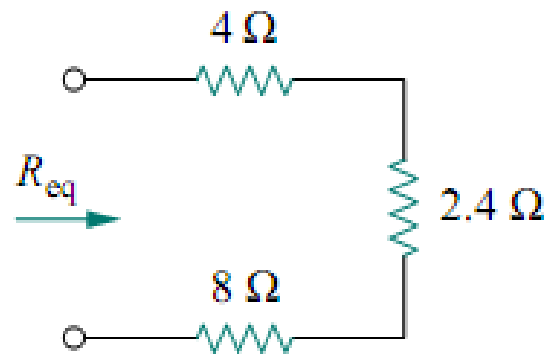
$$4\ \Omega \parallel 6\ \Omega = \frac{4 \times 6}{4 + 6} = 2.4\ \Omega$$




$$R_{eq} = 4\ \Omega + 2.4\ \Omega + 8\ \Omega = 14.4\ \Omega$$

Practice Problems (A)


1. Find R_{ab}

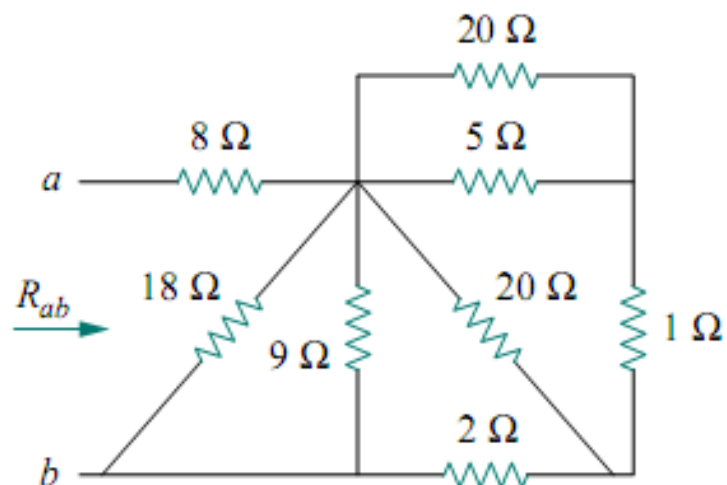


2. Find R_{ab}

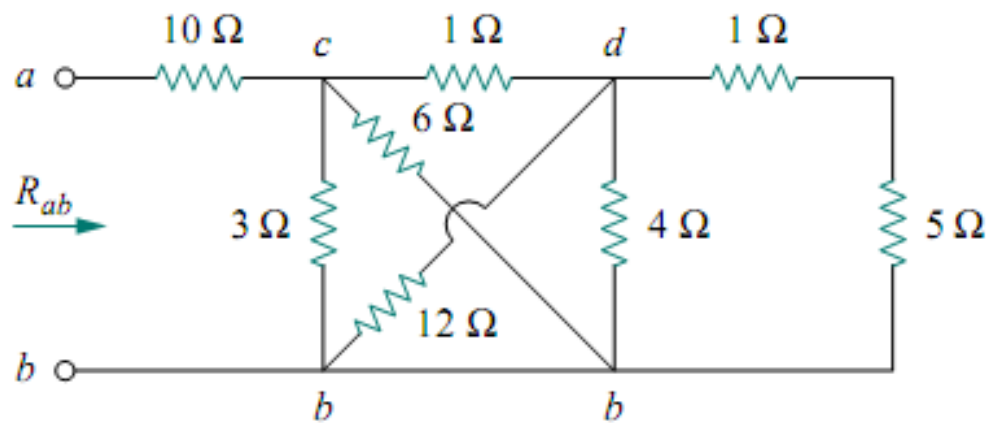


3. Find R_{eq} at terminals a - b

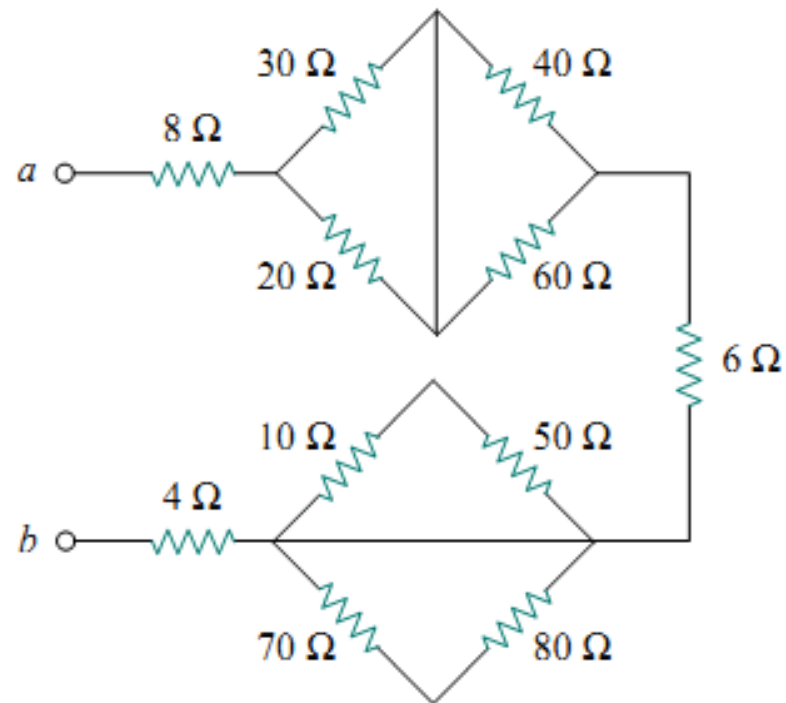


4. Find G_{eq}

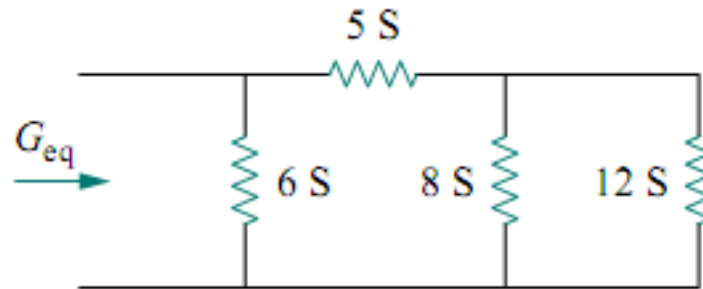

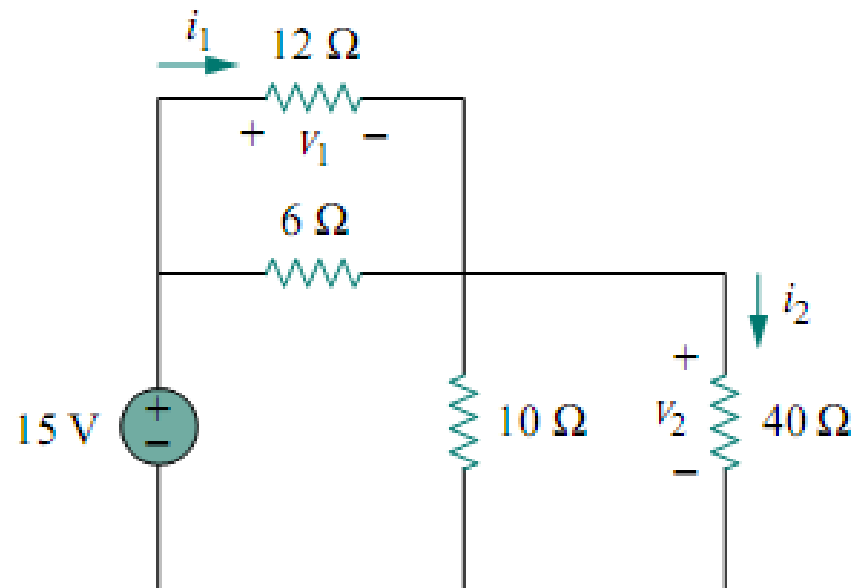
5. Find v_1 and v_2 in the circuit, and calculate the power dissipated in $12\text{-}\Omega$ and $40\text{-}\Omega$ resistors



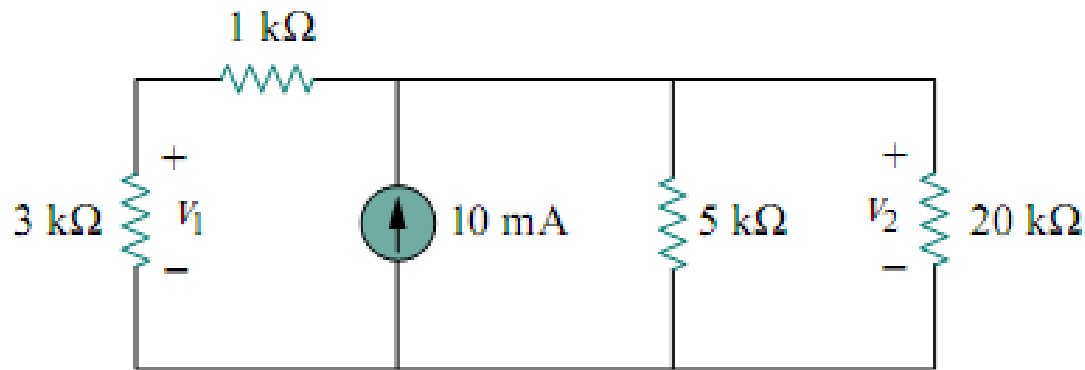
6. For the circuit, find: (a) v_1 and v_2 , (b) the power dissipated in the 3-k Ω and 20-k Ω resistors, and (c) the power supplied by the current source.




Wye-Delta Transformations

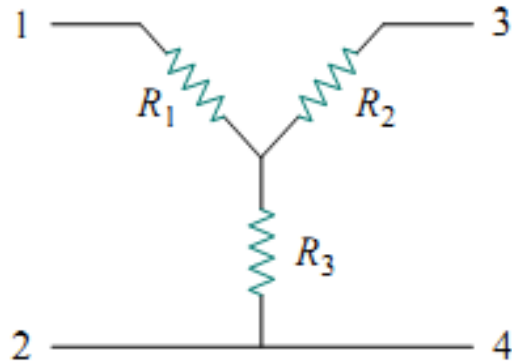


Y - network

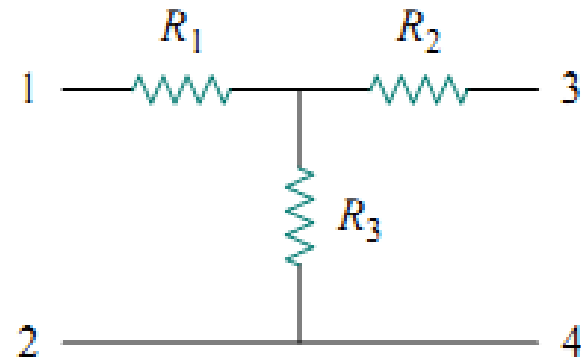

T - network

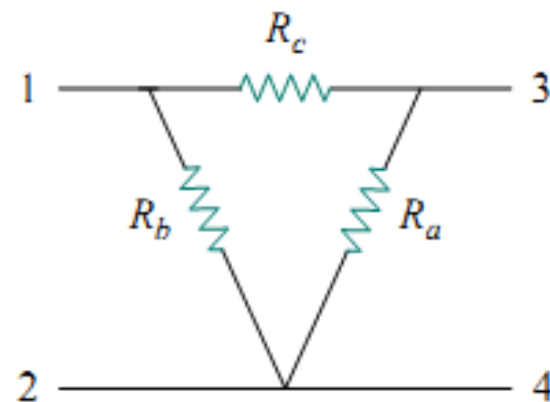

Δ - network

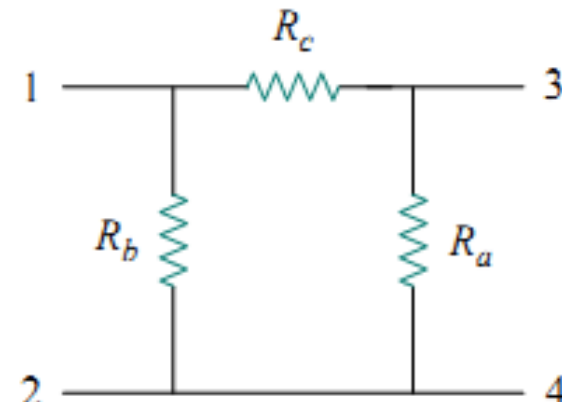

Π - network

$$R_{12}(Y) = R_1 + R_3$$

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$


Setting $R_{12}(Y) = R_{12}(\Delta)$ gives $R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$ **A**

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$
 B

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$
 C

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c}$$
 D=A-C

Delta to Wye Conversion

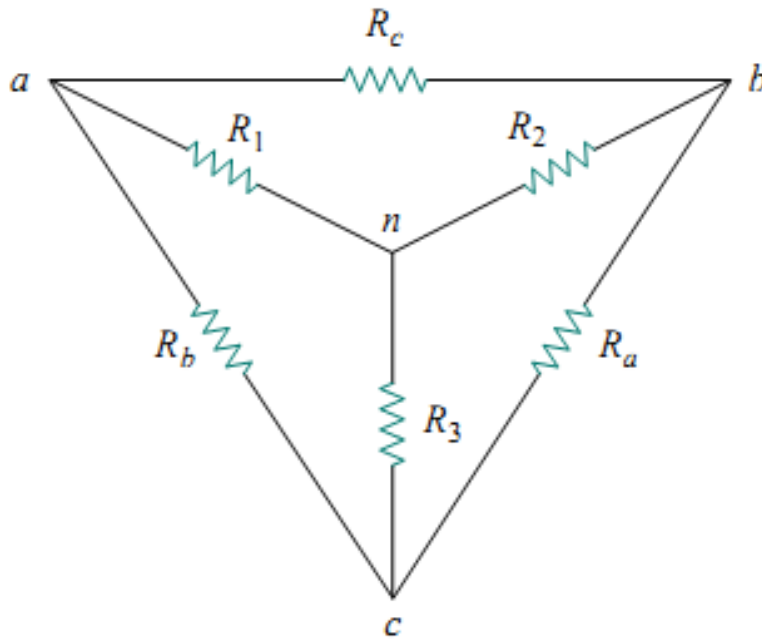

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$E = D + B$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$F = D - B$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$G = A - E$$


Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three Δ resistors.

Wye to Delta Conversion

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

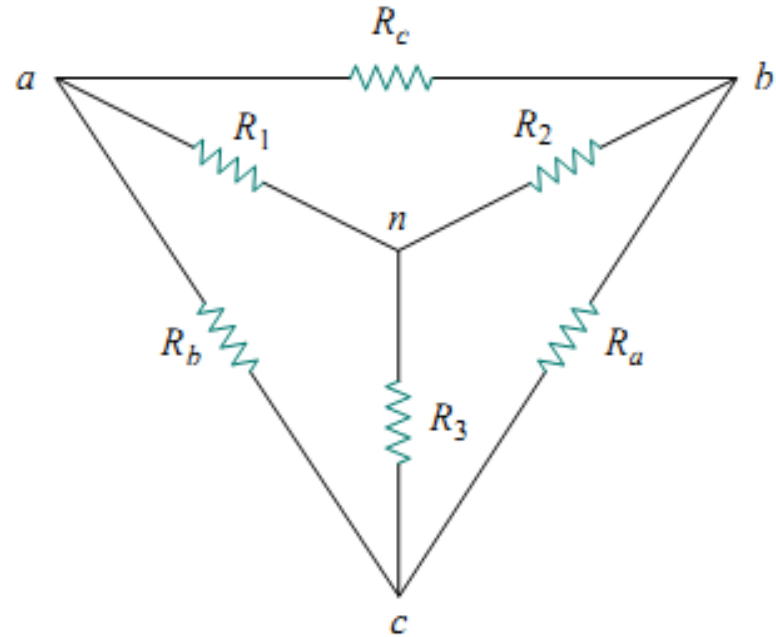
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

Practice Problems (B)

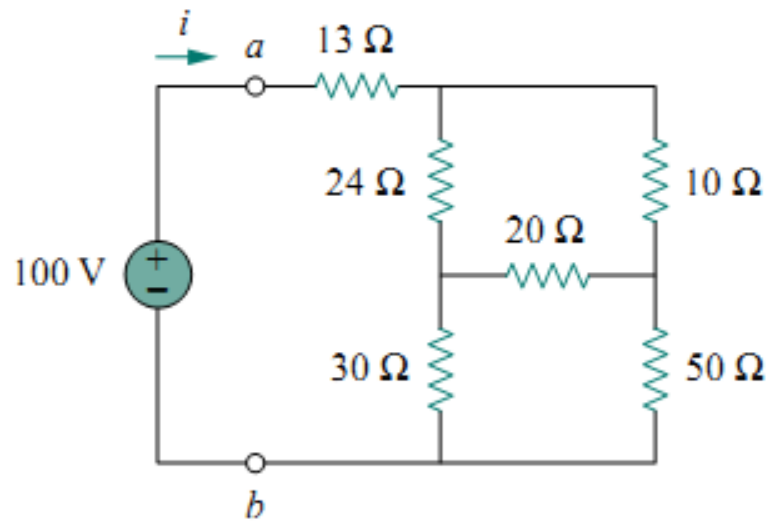
1. Find R_{ab} and i for bridge network below



2. Find R_{eq} at terminals a - b

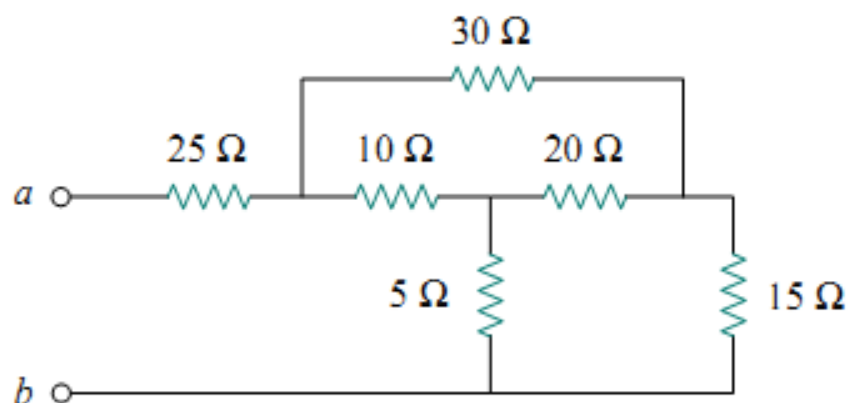

3. Find R_{eq} at terminals a - b

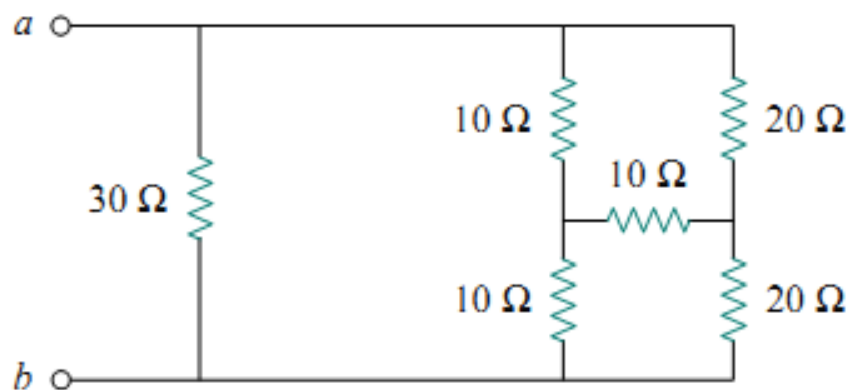

Selected Problems

2.32 Find V_o and I_o in the circuit of Fig. 2.96.

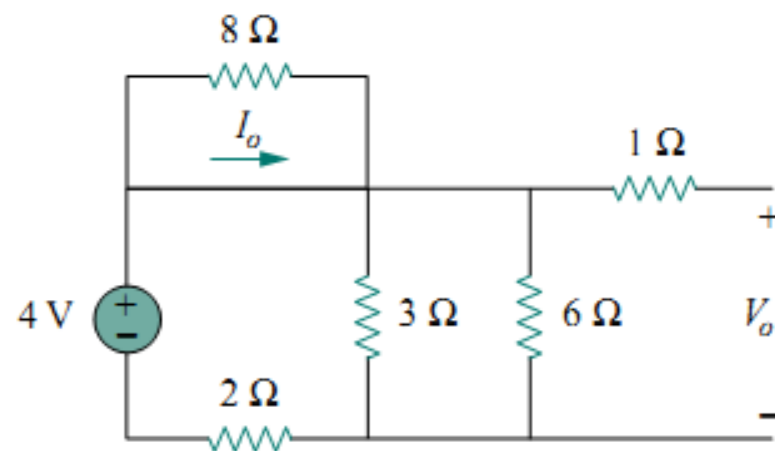


Figure 2.96 For Prob. 2.32.

2.36 For the ladder network in Fig. 2.100, find I and R_{eq} .

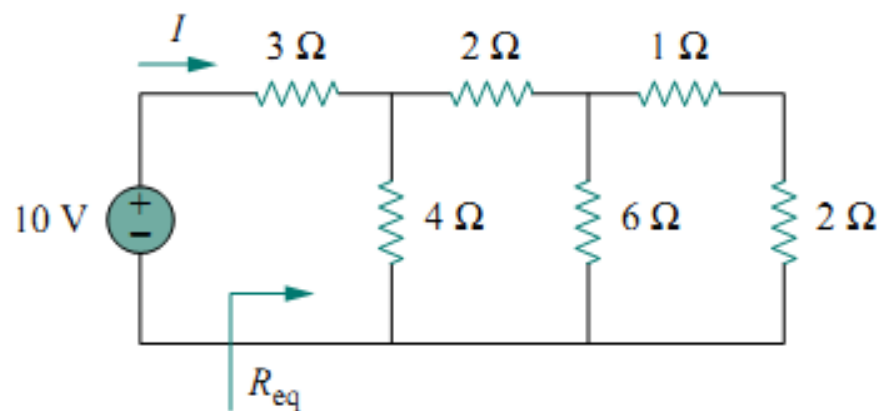


Figure 2.100 For Prob. 2.36.

2.42

Find the equivalent resistance R_{ab} in the circuit of Fig. 2.106.

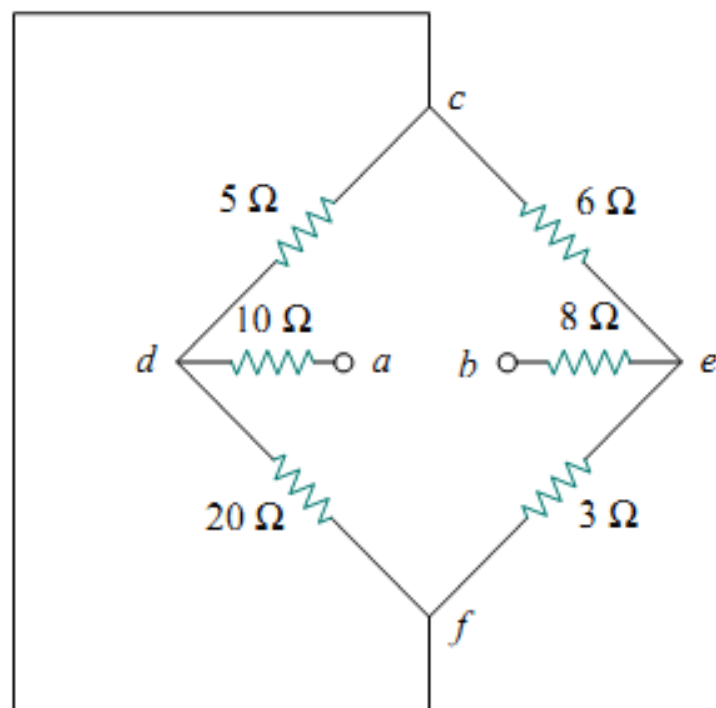


Figure 2.106 For Prob. 2.42.