

Fundamental of Digital Design



Oleh : Ahmad Zaini

TE.141323 Rangkaian Digital

Teknik Multimedia dan Jaringan, Teknik Elektro

FTI - ITS

Active and Inactive States

ACTIVE – a descriptor denoting an action condition

INACTIVE – a descriptor denoting a condition which is NOT ACTIVE

ACTIVE = Logic '1'

INACTIVE = Logic '0'


Activation Level Indicators

(H) Meaning ACTIVE HIGH

(L) Meaning ACTIVE LOW

Ex : Reset (L)
Load (H)

Positive and Negative Logic

 

Positive and Negative Logic

HV \longleftrightarrow Logic '1'

LV \longleftrightarrow Logic '0'

Positive Logic System

HV \longleftrightarrow Logic '0'

LV \longleftrightarrow Logic '1'


Negative Logic System

HV \longleftrightarrow 1 (H) = 0 (L)


LV \longleftrightarrow 0 (H) = 1 (L)

Implication

Positive and Negative Logic

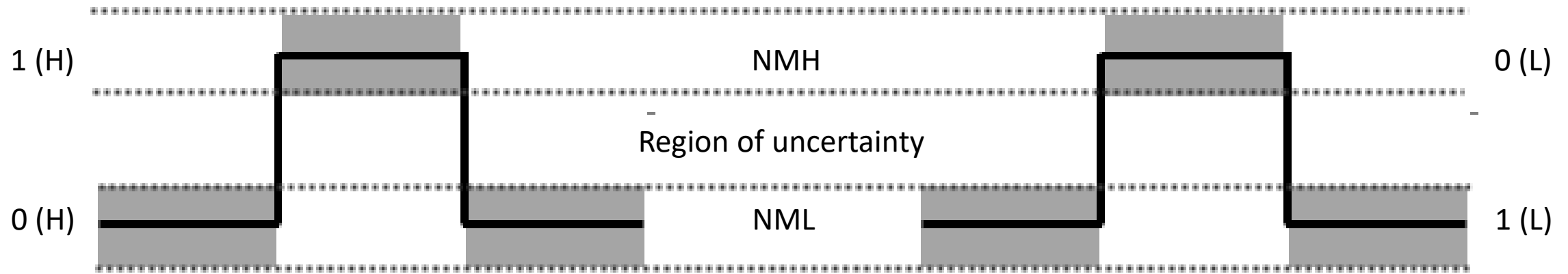

Logic Level Conversion – The Inverter


 


X_i	X_o
0	V _{DD}
V _{DD}	0


X_i	X_o
LV	HV
HV	LV

X(H)	X(L)
0	0
1	1

X(L)	X(H)
1	1
0	0

  


AND and OR

 

The outputs of a logic AND circuit is ACTIVE if, and only if, ALL inputs are ACTIVE

 
$$Y = A \cdot B \cdot C \cdot \dots \cdot Z$$



The outputs of a logic OR circuit is ACTIVE if, one or more of the inputs are ACTIVE

$$Y = A + B + C + \dots + Z$$

NAND gate realization of AND and OR (1)

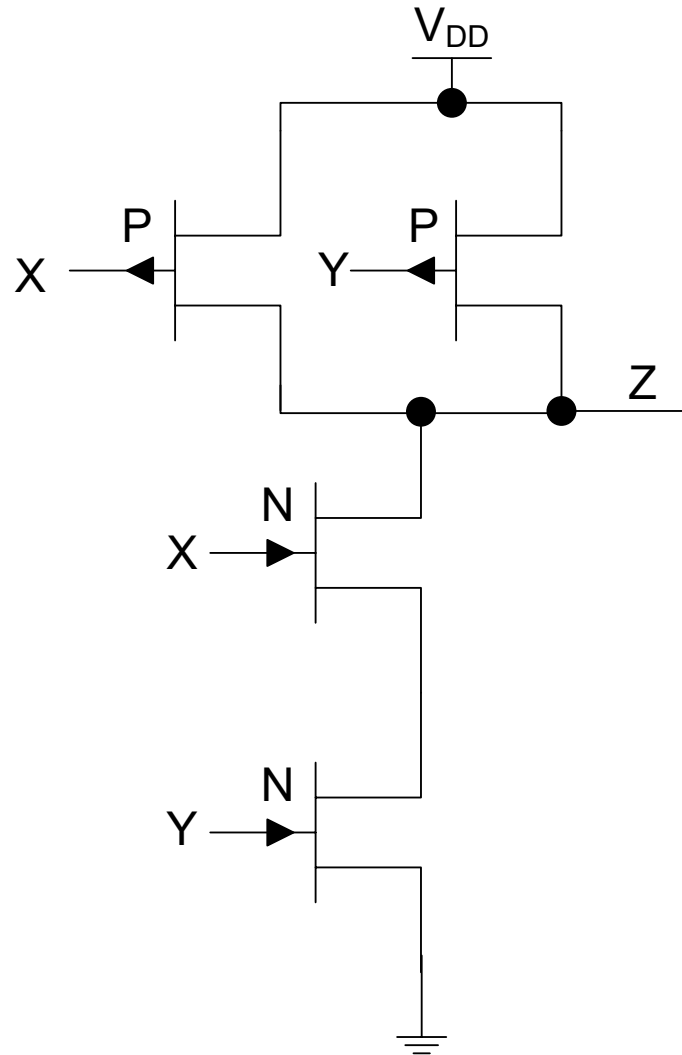

X	Y	Z
0	0	5
0	5	5
5	0	5
5	5	0



X	Y	Z
LV	LV	HV
LV	HV	HV
HV	LV	HV
HV	HV	LV

NAND gate realization of AND and OR (2)


X(H)	Y(H)	Z(L)
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	Z
LV	LV	HV
LV	HV	HV
HV	LV	HV
HV	HV	LV

X(L)	Y(L)	Z(H)
1	1	1
1	0	1
0	1	1
0	0	0

  

NOR gate realization of AND and OR (1)

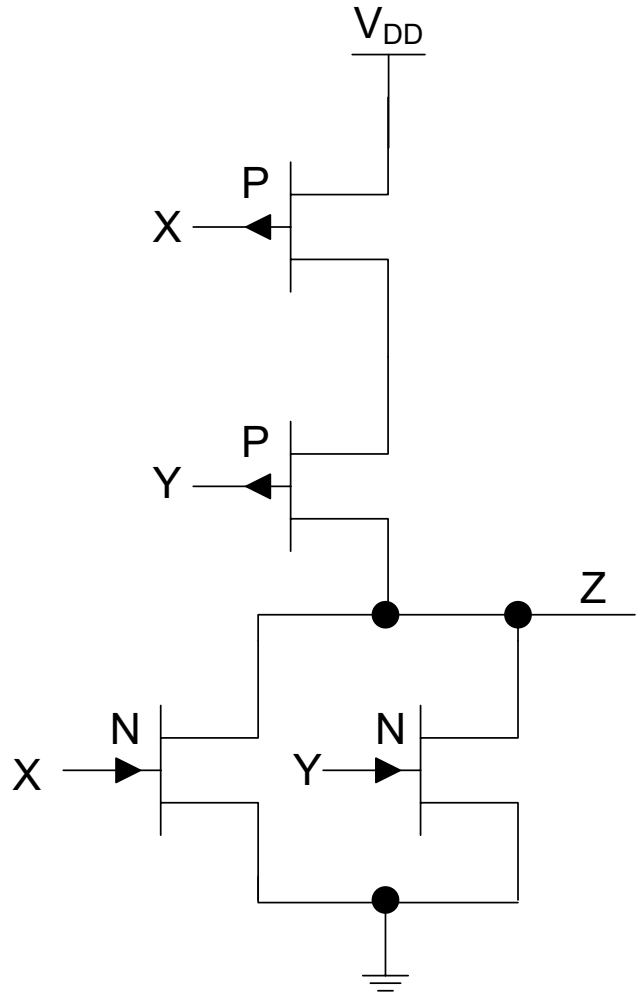

X	Y	Z
0	0	5
0	5	0
5	0	0
5	5	0



X	Y	Z
LV	LV	HV
LV	HV	LV
HV	LV	LV
HV	HV	LV

NOR gate realization of AND and OR (2)





X(H)	Y(H)	Z(L)
0	0	0
0	1	1
1	0	1
1	1	1

X	Y	Z
LV	LV	HV
LV	HV	LV
HV	LV	LV
HV	HV	LV


X(L)	Y(L)	Z(H)
1	1	1
1	0	0
0	1	0
0	0	0

  

NAND and NOR Logic Level Conversion

    

AND gate realization of AND and OR (1)

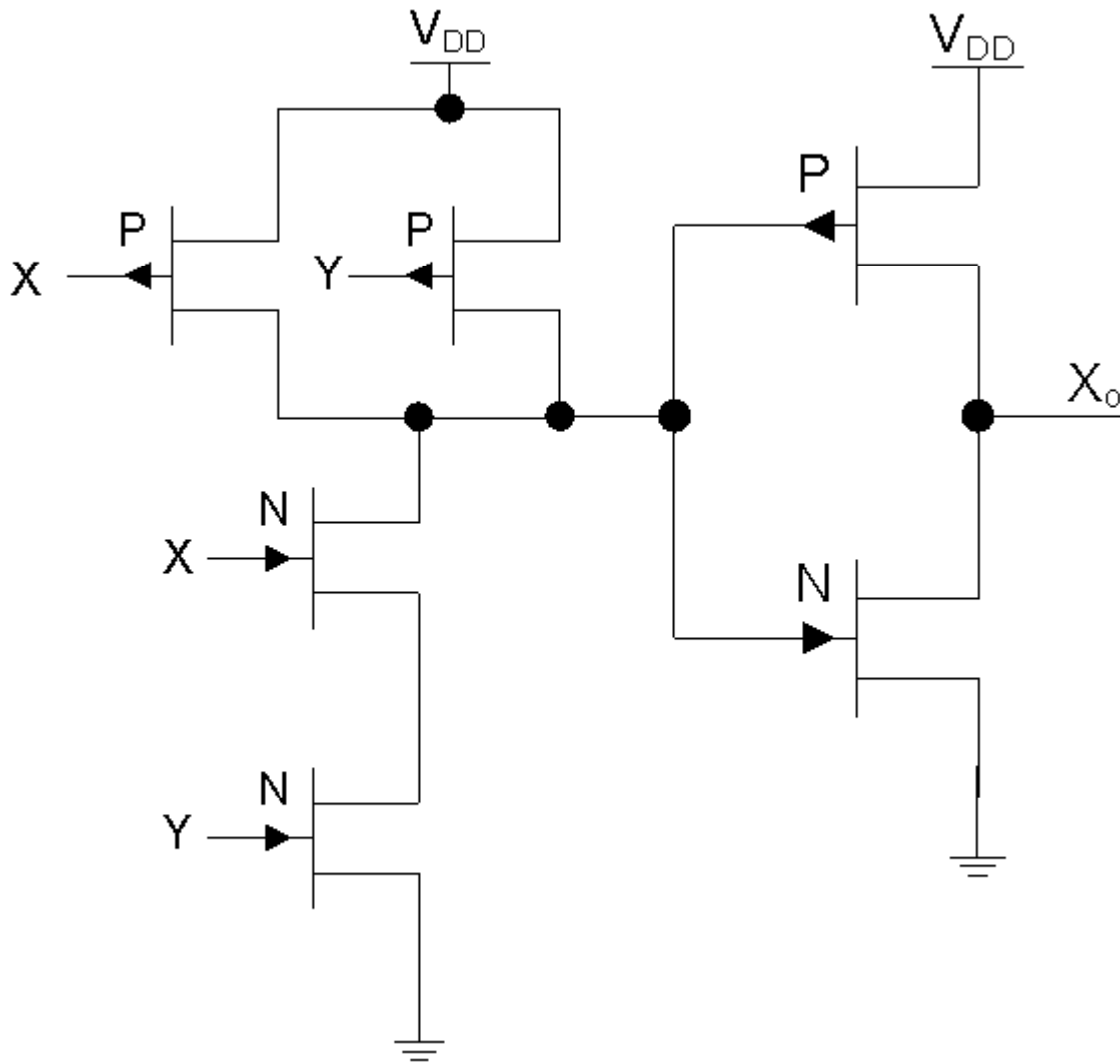

X	Y	Z
0	0	0
0	5	0
5	0	0
5	5	5



X	Y	Z
LV	LV	LV
LV	HV	LV
HV	LV	LV
HV	HV	HV

AND gate realization of AND and OR (2)


X(H)	Y(H)	Z(H)
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	Z
LV	LV	LV
LV	HV	LV
HV	LV	LV
HV	HV	HV

X(L)	Y(L)	Z(L)
1	1	1
1	0	1
0	1	1
0	0	0

  

OR gate realization of AND and OR (1)

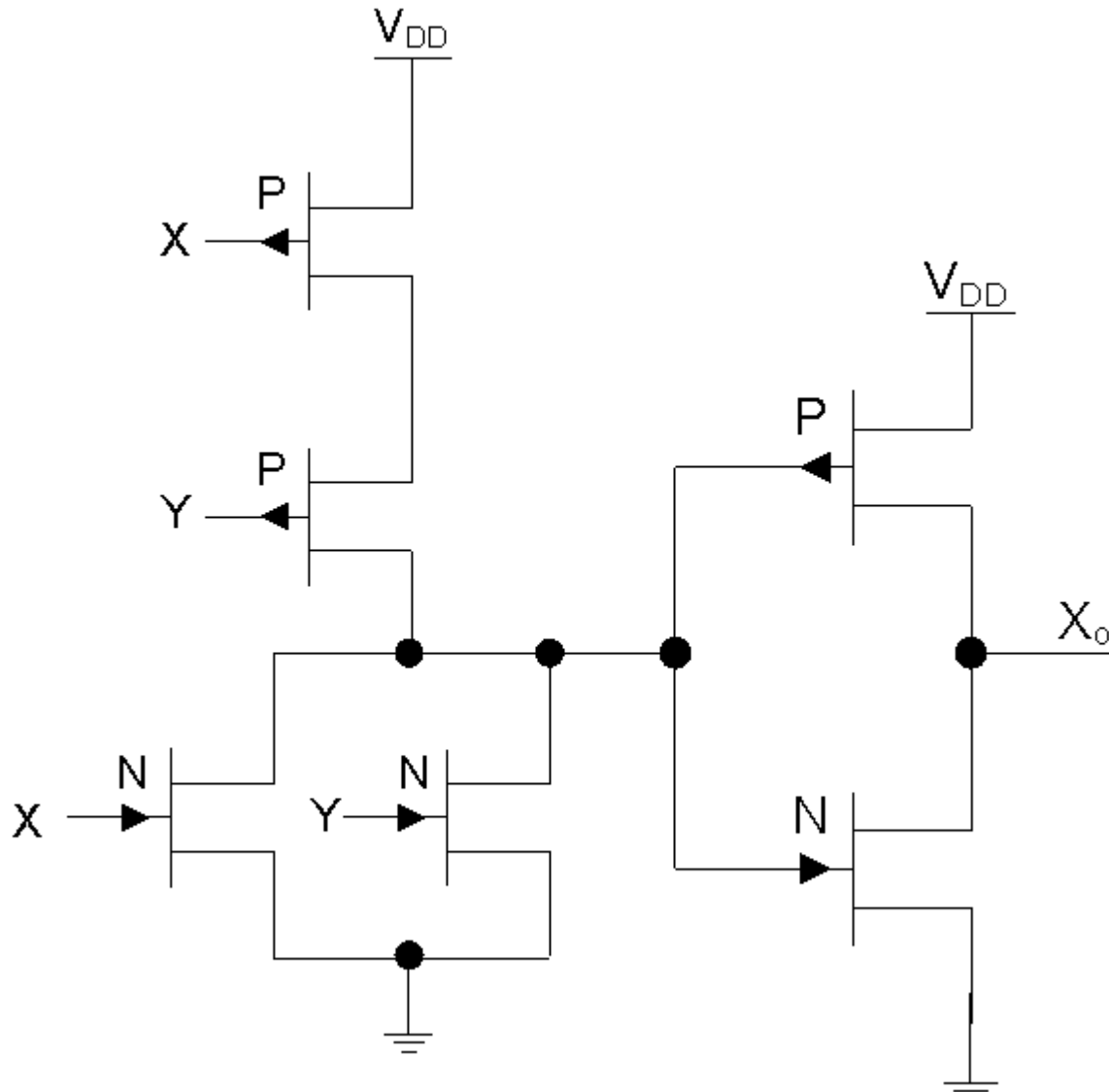

X	Y	Z
0	0	0
0	5	5
5	0	5
5	5	5



X	Y	Z
LV	LV	LV
LV	HV	HV
HV	LV	HV
HV	HV	HV

OR gate realization of AND and OR (2)

X(H)	Y(H)	Z(H)
0	0	0
0	1	1
1	0	1
1	1	1

X	Y	Z
LV	LV	LV
LV	HV	HV
HV	LV	HV
HV	HV	HV


X(L)	Y(L)	Z(L)
1	1	1
1	0	0
0	1	0
0	0	0

  

Logic Level Incompatibility


The input logic level doesn't meet with line input gate logic level

 Place the incompatibility “ ∇ ” flag on the line input gate to indicate incompatibility logic level




Complement
 
$$\alpha(L) = \bar{\alpha}(H) \qquad \bar{\alpha}(L) = \alpha(H)$$




Reading of Logic circuit

“ Input to Output State ”

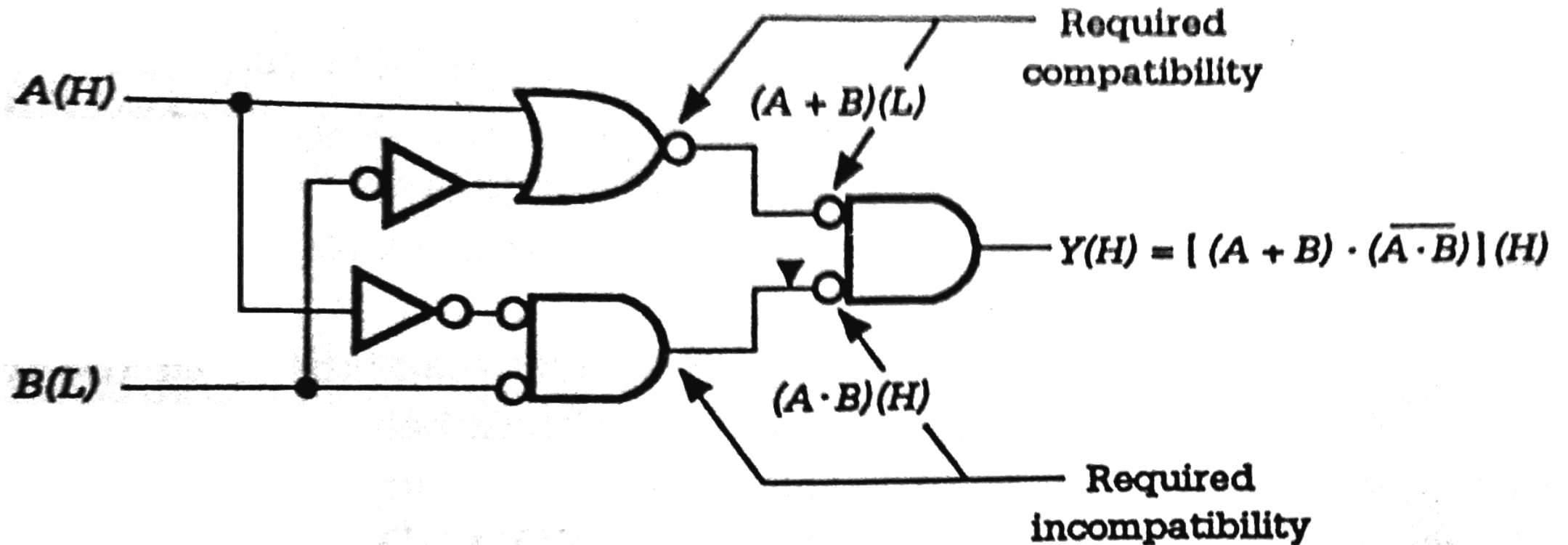


Construction of Logic circuit

 


“ Output to Input State “

Function XOR and EQV

$\oplus \rightarrow XOR$

 

$\odot \rightarrow EQV$

 


The output of a logic XOR circuit symbol is ACTIVE if one or the other of two inputs is ACTIVE but not both ACTIVE or INACTIVE

The output of a logic EQV circuit symbol is ACTIVE if and only if both inputs are ACTIVE or if both inputs are INACTIVE

$$X = (\bar{A} \cdot B) + (A \cdot \bar{B}) = A \oplus B$$

$$X = (A \cdot B) + (\bar{A} \cdot \bar{B}) = A \odot B$$

 XOR gate realization of XOR and EQV function (1)



X	Y	Z
0	0	0
0	5	5
5	0	5
5	5	0



X	Y	Z
LV	LV	LV
LV	HV	HV
HV	LV	HV
HV	HV	LV

XOR gate realization of XOR and EQV function (2)


X(H)	Y(H)	Z(H)
0	0	0
0	1	1
1	0	1
1	1	0

X	Y	Z
LV	LV	LV
LV	HV	HV
HV	LV	HV
HV	HV	LV

X(H)	Y(H)	Z(L)
0	0	1
0	1	0
1	0	0
1	1	1

  

 EQV gate realization of XOR and EQV function (1)



X	Y	Z
0	0	5
0	5	0
5	0	0
5	5	5



X	Y	Z
LV	LV	HV
LV	HV	LV
HV	LV	LV
HV	HV	HV

EQV gate realization of XOR and EQV function (2)

X(H)	Y(H)	Z(H)
0	0	1
0	1	0
1	0	0
1	1	1


X	Y	Z
LV	LV	HV
LV	HV	LV
HV	LV	LV
HV	HV	HV

X(H)	Y(H)	Z(L)
0	0	0
0	1	1
1	0	1
1	1	0

  


Controlled Logic Level Conversion

X(L)	Y(L)	Z(H)
1	1	0
1	0	1
0	1	1
0	0	0

 


$X(L) \rightarrow X(H)$

 


Transfer

X(H)	Y(H)	Z(L)
0	0	1
0	1	0
1	0	0
1	1	1

 

$X(H) \rightarrow X(L)$

 

Transfer