




DC Circuits

First Order Circuits

The Source Free Circuits

The natural response of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.

RC Circuit

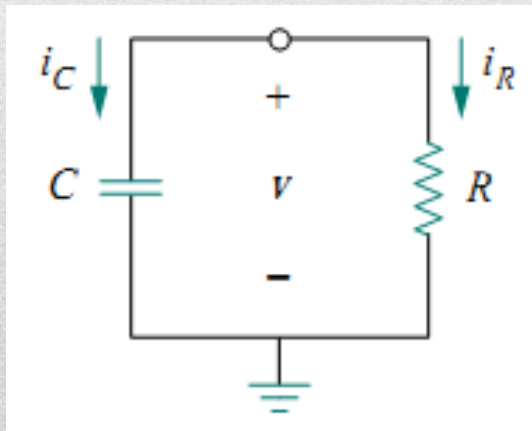


$$i_C + i_R = 0$$
$$C \frac{dv}{dt} + \frac{v}{R} = 0$$
$$\frac{dv}{dt} + \frac{v}{RC} = 0$$

$$v(t) = V_0 e^{-t/RC}$$

The time constant of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8 percent of its initial value.¹
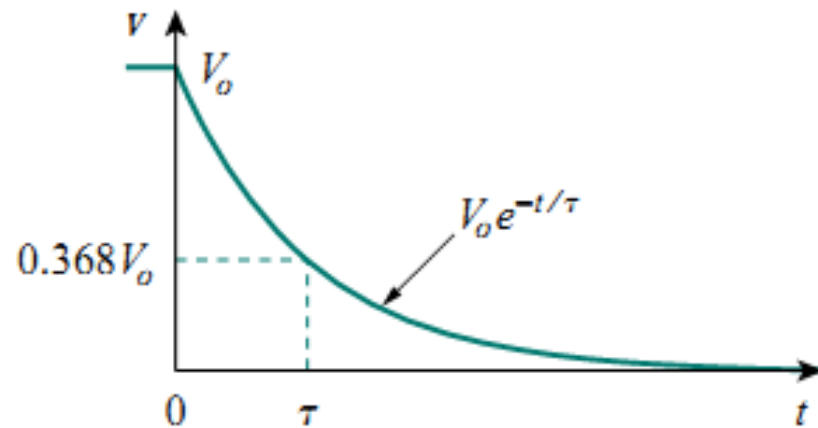
$$V_0 e^{-\tau/RC} = V_0 e^{-1} = 0.368 V_0$$



$$\tau = RC$$


$$v(t) = V_0 e^{-t/\tau}$$

The Key to Working with a Source-free RC Circuit is Finding:

1. The initial voltage $v(0) = V_0$ across the capacitor.
2. The time constant τ .

When a circuit contains a single capacitor and several resistors and dependent sources, the Thevenin equivalent can be found at the terminals of the capacitor to form a simple RC circuit. Also, one can use Thevenin's theorem when several capacitors can be combined to form a single equivalent capacitor.

RL Circuit

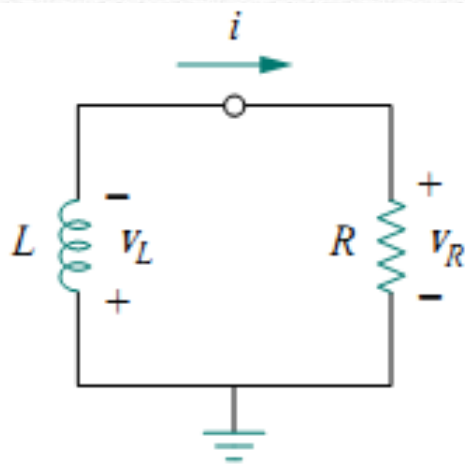

$$v_L + v_R = 0$$


$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

$$i(t) = I_0 e^{-Rt/L}$$

$$\tau = \frac{L}{R}$$

$$i(t) = I_0 e^{-t/\tau}$$

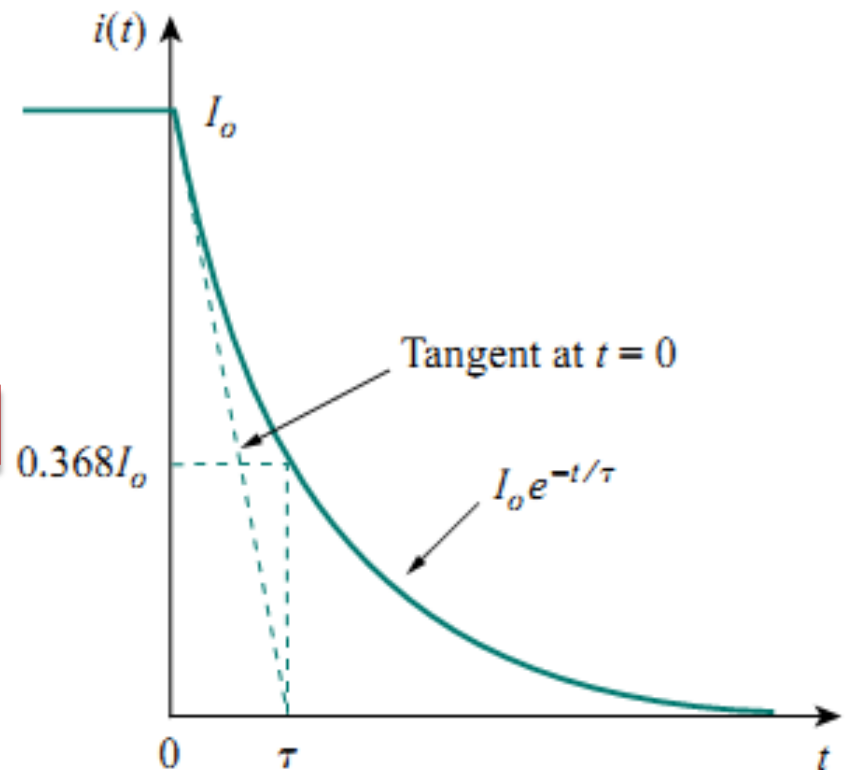

The Key to Working with a Source-free RL Circuit is to Find:

1. The initial current $i(0) = I_0$ through the inductor.
2. The time constant τ of the circuit.


When a circuit has a single inductor and several resistors and dependent sources, the Thevenin equivalent can be found at the terminals of the inductor to form a simple RL circuit. Also, one can use Thevenin's theorem when several inductors can be combined to form a single equivalent inductor.

Singularity Functions


Singularity functions are functions that either are discontinuous or have discontinuous derivatives.

Unit Step Function

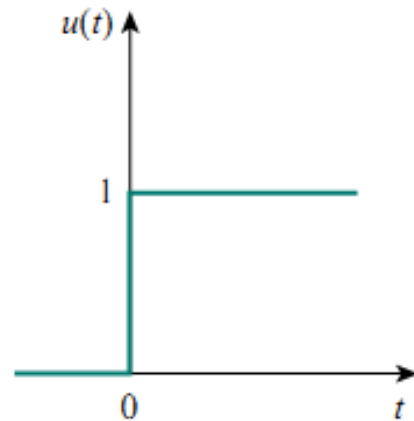
The unit step function $u(t)$ is 0 for negative values of t and 1 for positive values of t .


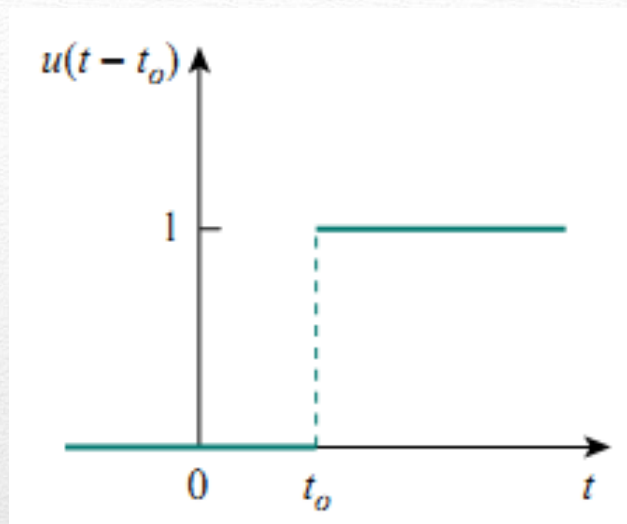
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




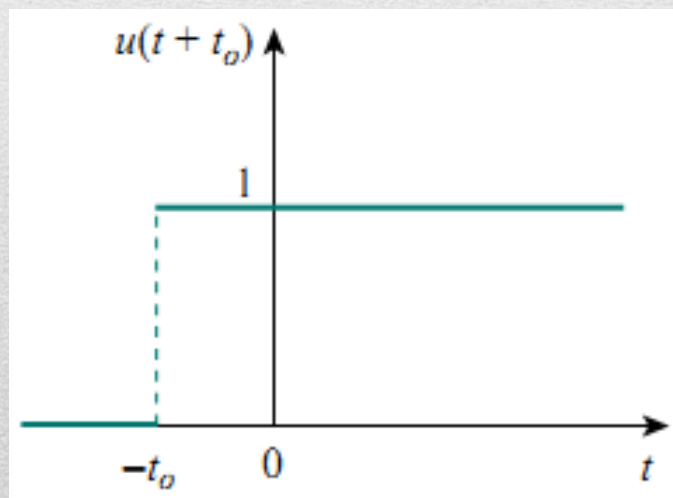
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$



$$u(t + t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$


$$v(t) = V_0 u(t - t_0)$$
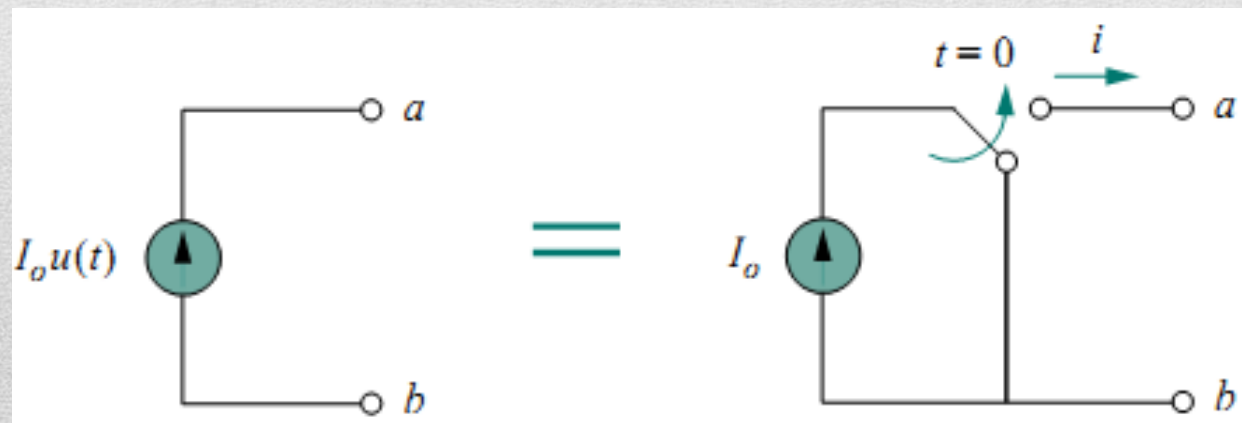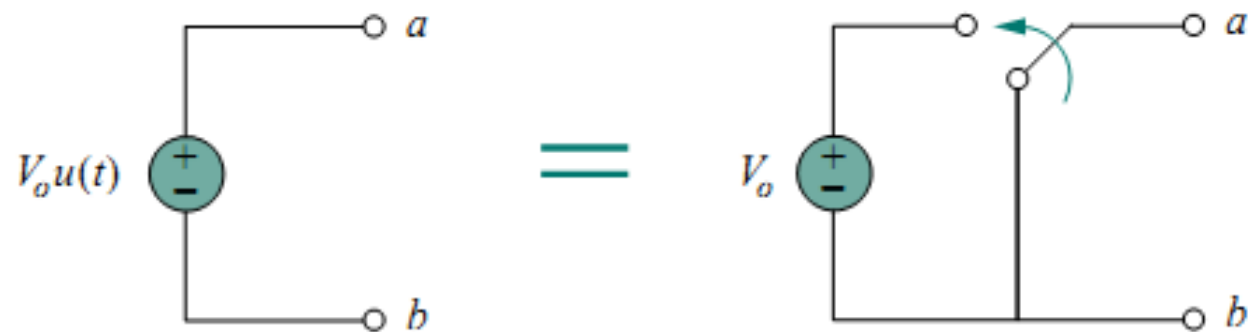
$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \end{cases}$$



Unit Impulse Function
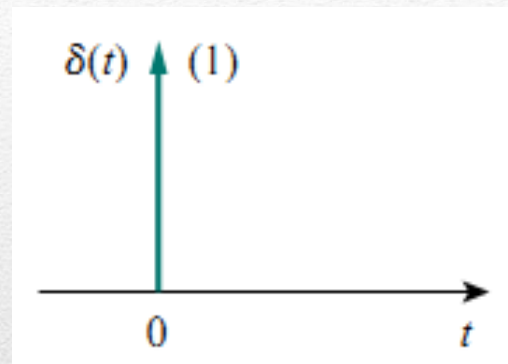
$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ \text{Undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$




The unit impulse function $\delta(t)$ is zero everywhere except at $t = 0$, where it is undefined.

Unit Ramp Function

$$r(t) = \int_{-\infty}^t u(t) dt = tu(t)$$
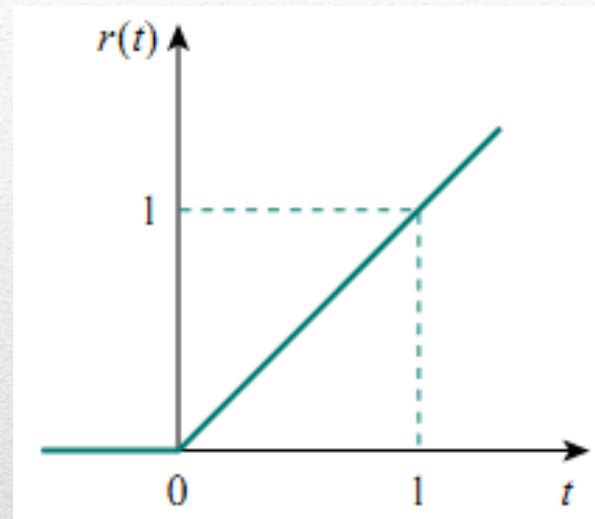
$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$





The unit ramp function is zero for negative values of t and has a unit slope for positive values of t .



Step Response

The step response of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.

RC Circuit

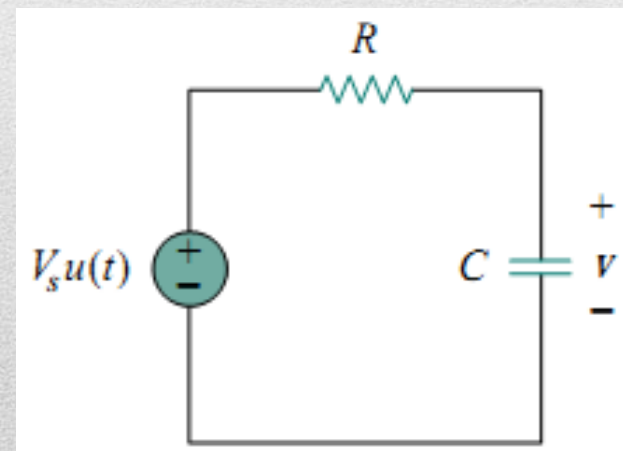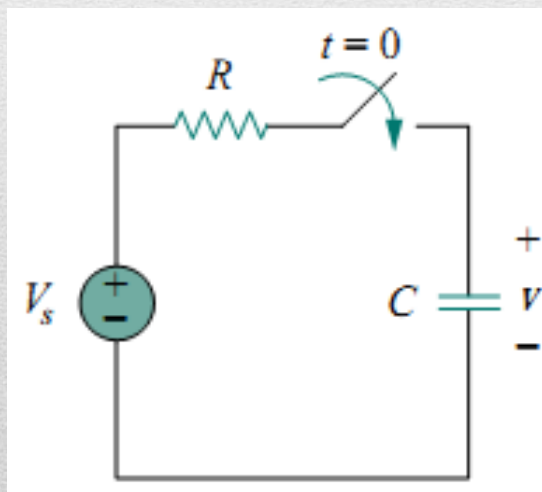

RL Circuit

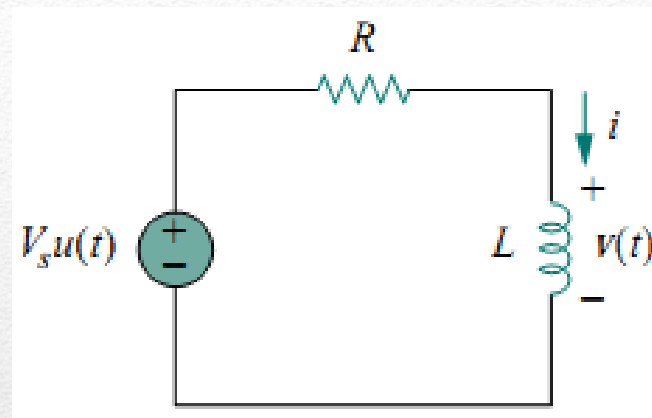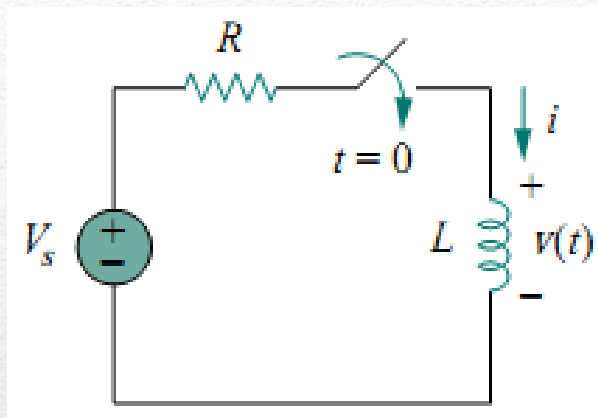


Complete Response


The **complete response** of the circuit is the sum of the **natural response** and the **forced response**.

$$v = v_f + v_n$$

$$i = i_n + i_f$$

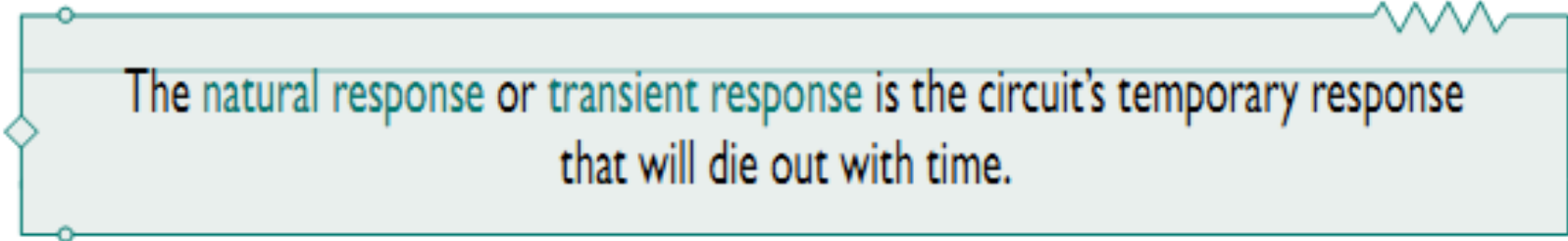

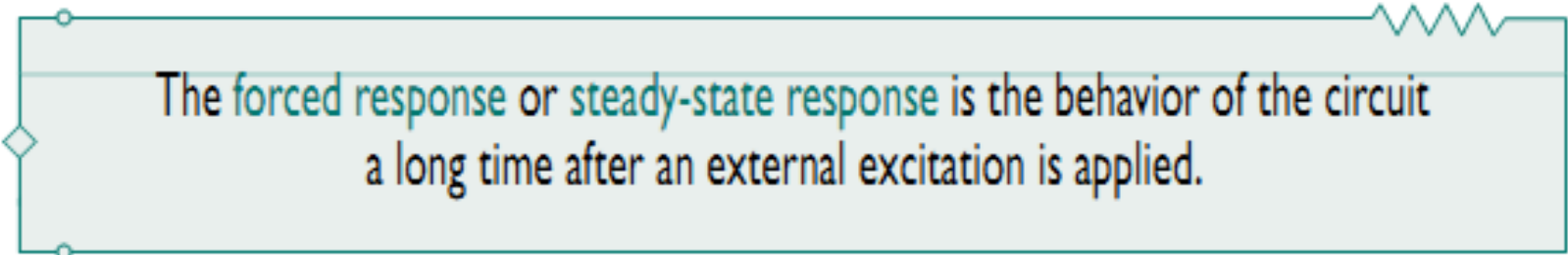The natural response or transient response is the circuit's temporary response that will die out with time.




The forced response or steady-state response is the behavior of the circuit a long time after an external excitation is applied.

General Solution

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

Complete Response of RC Circuit

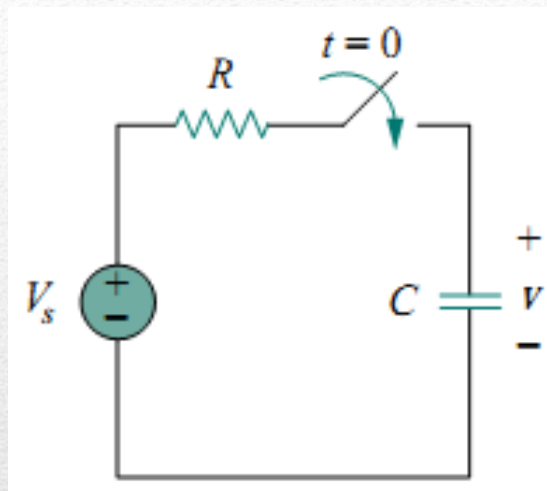


$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$
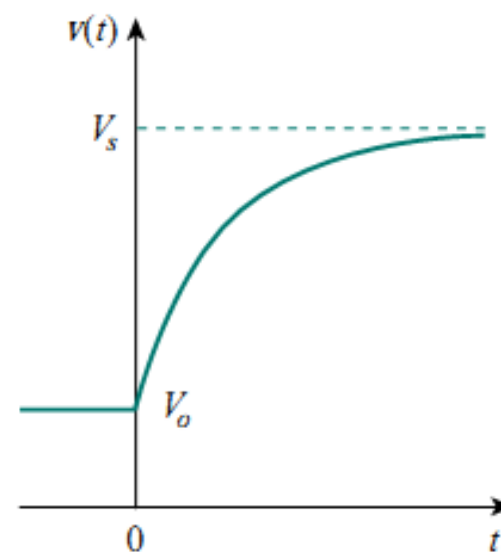
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t \geq 0 \end{cases}$$




Complete Response of RL Circuit

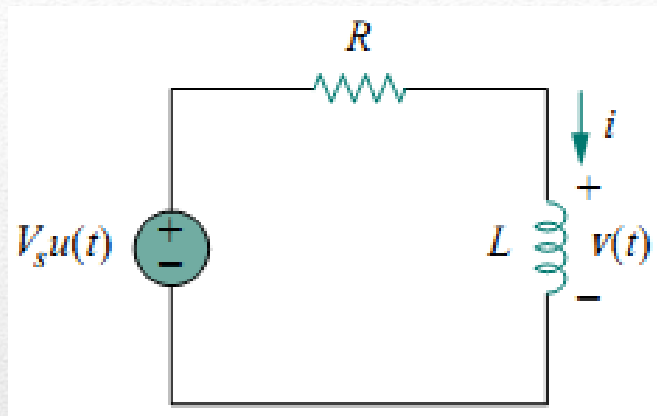


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$
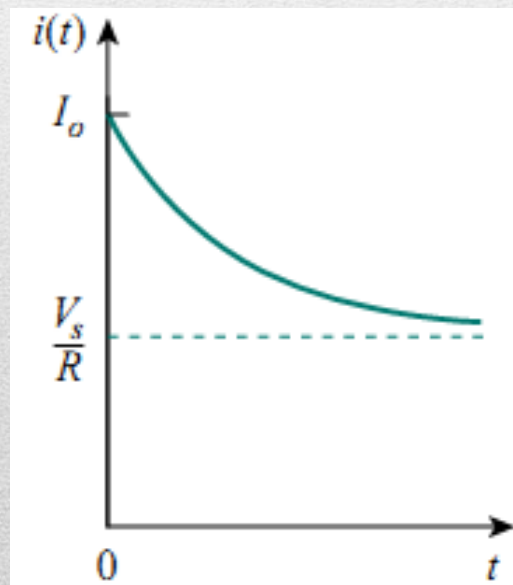
$$i(t) = \begin{cases} I_o & t < 0 \\ \frac{V_s}{R} + \left(I_o - \frac{V_s}{R}\right)e^{-\frac{R}{L}t} & t > 0 \end{cases}$$



Practice Problems

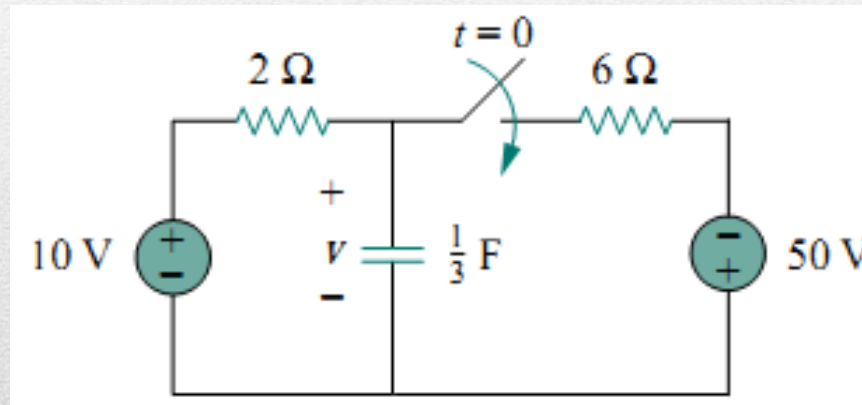- 1 Find $v(t)$ for $t > 0$. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$



Answer: $-5 + 15e^{-2t}$ V, 0.5182 V.

Solution

Method 1

$$v(0) = 10 \text{ V}$$

$$v(\infty) = \frac{6}{6+2} 10 + \frac{2}{2+6} (-50) = \frac{60-100}{8} = -5 \text{ V}$$

$$\tau = (2 \parallel 6) \frac{1}{3} = \frac{12}{8} \frac{1}{3} = \frac{1}{2}$$


$$v(t) = v_f(t) + v_n(t)$$

$$v(t) = v(\infty) + Ae^{-\frac{t}{\tau}}$$

$$v(t) = -5 + Ae^{-2t}$$

$$\text{For } t = 0 : v(0) = -5 + A$$

$$10 = -5 + A \Rightarrow A = 15$$

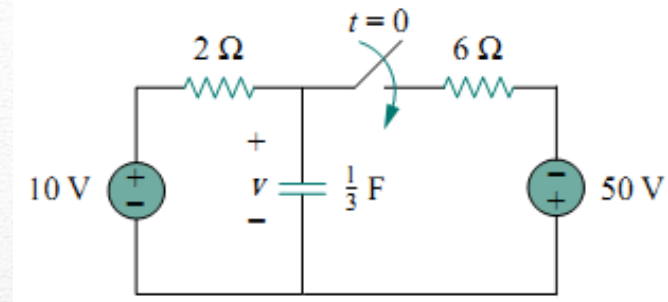

$$v(t) = -5 + 15e^{-2t} \text{ V}$$

$$t = 0.5 : v(0.5) = -5 + 15e^{-2(0.5)}$$

$$v(0.5) = -5 + 15 \times 0.3679$$

$$v(0.5) = 0.5182 \text{ V}$$

Method 2

$$v(0) = 10 \text{ V}$$

$$v(\infty) = \frac{6}{6+2} 10 + \frac{2}{2+6} (-50) = \frac{60-100}{8} = -5 \text{ V}$$

$$\tau = (2 \parallel 6) \frac{1}{3} = \frac{12}{8} \frac{1}{3} = \frac{1}{2}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$


$$v(t) = -5 + [10 - (-5)]e^{-2t}$$

$$v(t) = -5 + 15e^{-2t} \text{ V}$$


$$t = 0.5 : v(0.5) = -5 + 15e^{-2(0.5)}$$

$$v(0.5) = -5 + 15 \times 0.3679$$

$$v(0.5) = 0.5182 \text{ V}$$

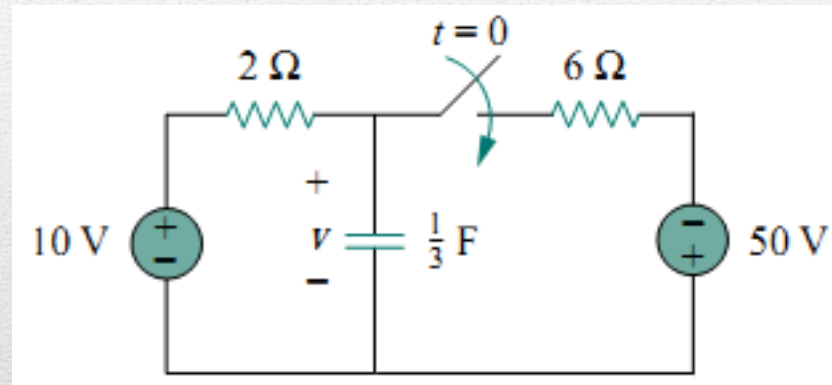

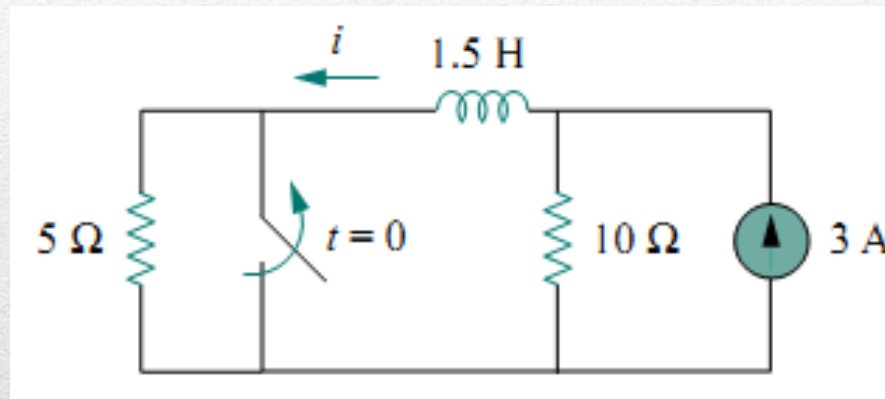- 2 The switch has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$



Answer: $(2 + e^{-10t})\text{ A}, t > 0.$

Solution

$$i(0) = 3 \text{ A}$$


$$i(\infty) = \frac{10}{5 + 10} (3) = 2 \text{ A}$$

$$\tau = \frac{1.5}{15} = \frac{1}{10}$$


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

$$i(t) = 2 + [3 - 2]e^{-10t}$$


$$i(t) = 2 + e^{-10t} \text{ A}$$

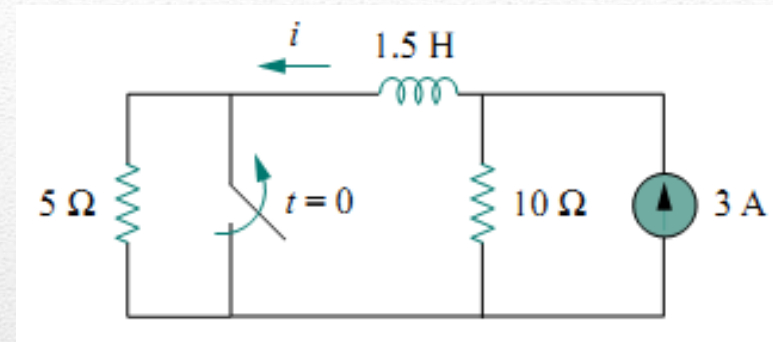

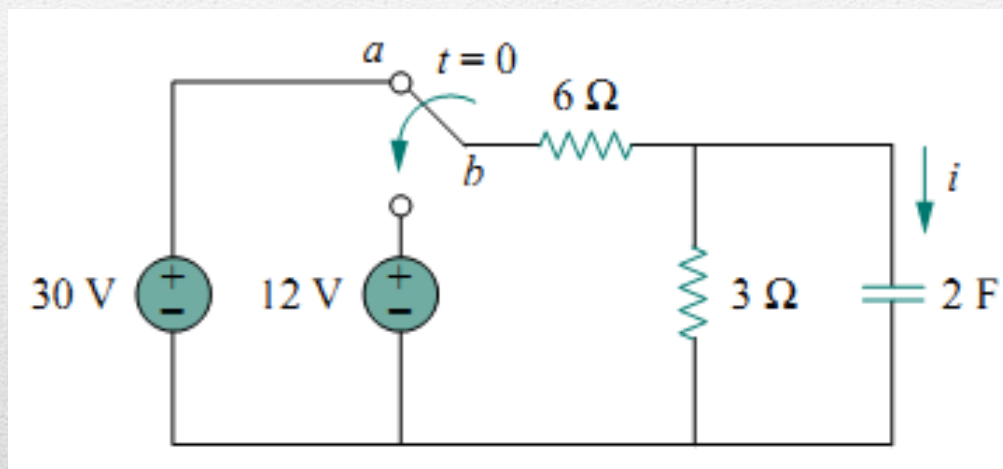- 3 The switch in has been in position a for a long time. At $t = 0$, it moves to position b . Calculate $i(t)$ for all $t > 0$.



Solution

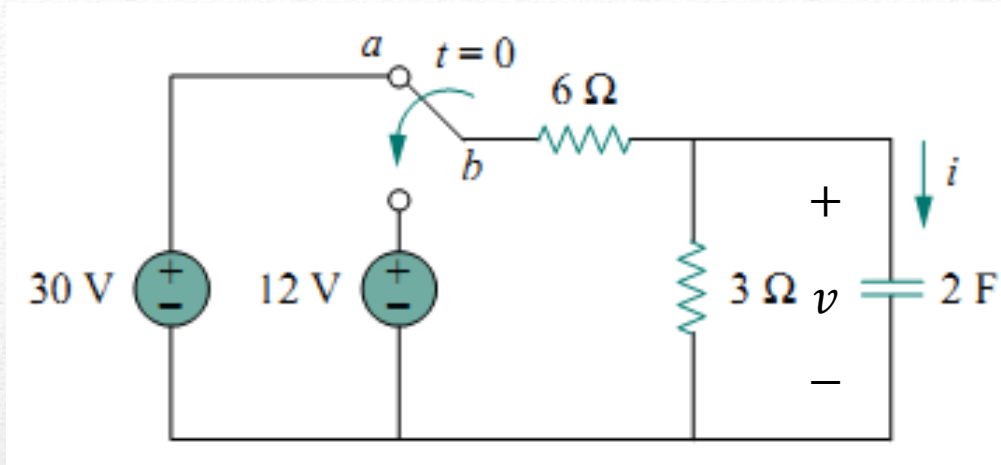

$$t < 0 \quad v(t) = \frac{3}{3+6} 30 = 10 \text{ V}$$

$$i(t) = 0 \text{ A}$$

$$t = 0 \quad v(0) = 10 \text{ V}$$

$$t > 0 \quad v(\infty) = \frac{3}{3+6} 12 = 4 \text{ V}$$

$$\tau = (6 \parallel 3)2 = 4$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

$$v(t) = 4 + [10 - 4]e^{-0.25t}$$

$$v(t) = 4 + 6e^{-0.25t} \text{ V}$$

$$i(t) = 2 \frac{dv(t)}{dt} = 2(-0.25)6e^{-0.25t}$$

$$i(t) = -3e^{-0.25t} \text{ A}$$

$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \\ -3e^{-0.25t} \text{ A} & t > 0 \end{cases}$$