







DC Circuits


Second Order Circuits

Introduction

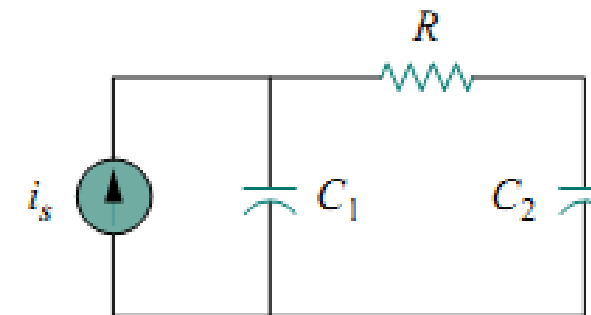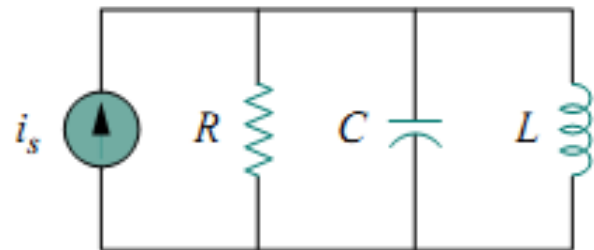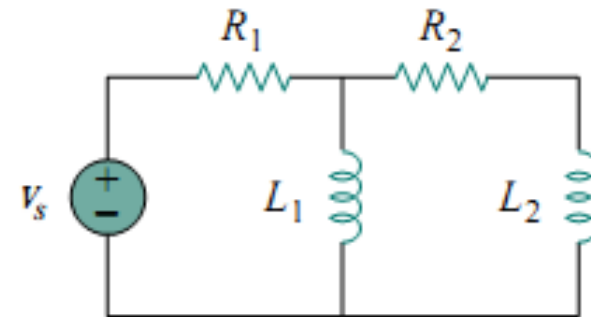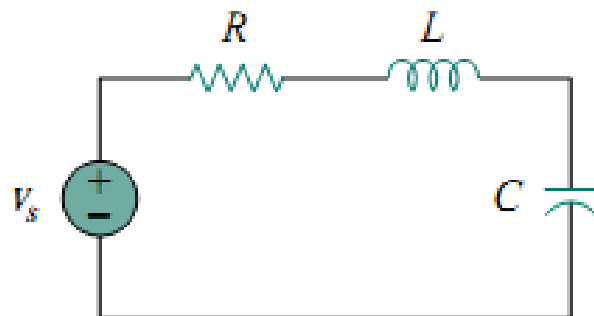A second-order circuit is characterized by a second-order differential equation. It consists of resistors and the equivalent of two energy storage elements.



Finding Initial and Final Values

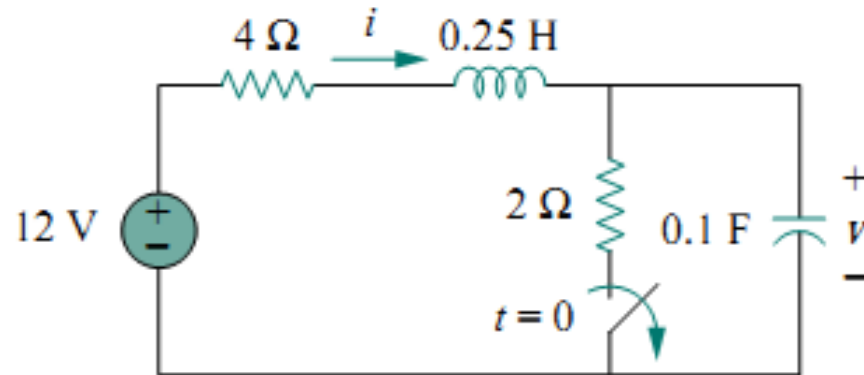


Find: (a) $i(0^+)$, $v(0^+)$, (b) $di(0^+)/dt$, $dv(0^+)/dt$, (c) $i(\infty)$, $v(\infty)$.

The capacitor voltage is always continuous $\Rightarrow v(0^+) = v(0^-)$


The inductor current is always continuous $\Rightarrow i(0^+) = i(0^-)$

Equivalent circuit


$t = 0^-$

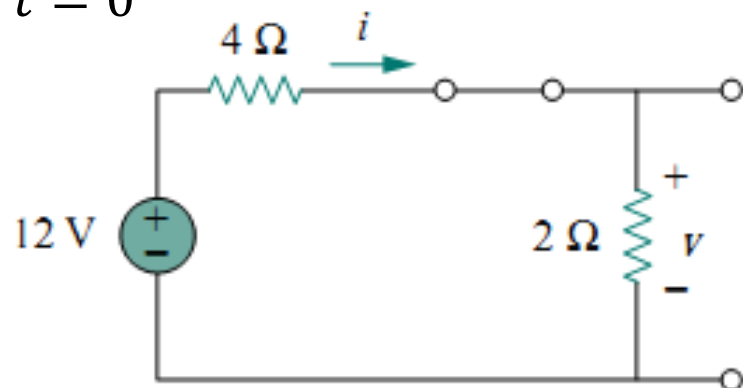


$t = 0^+$

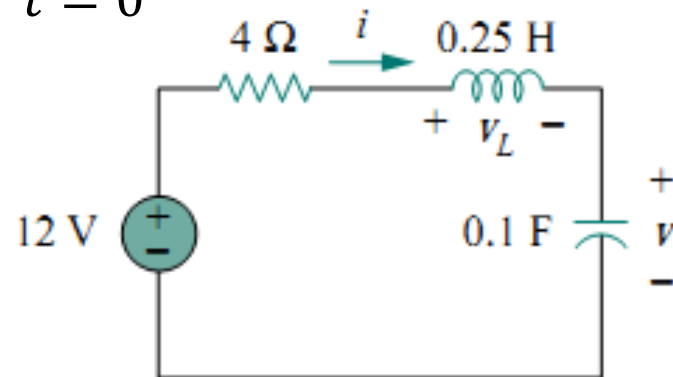

$t \rightarrow \infty$

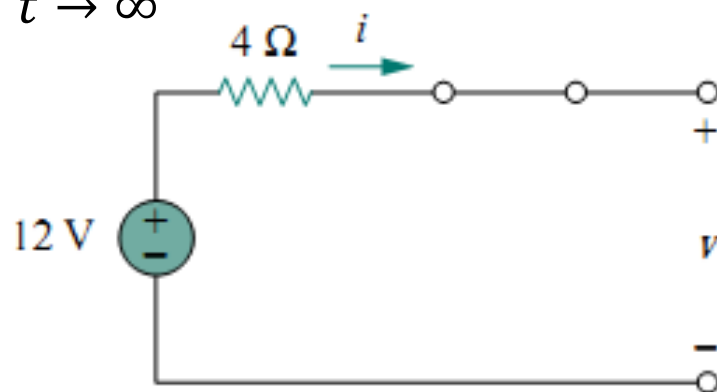

$t = 0^-$

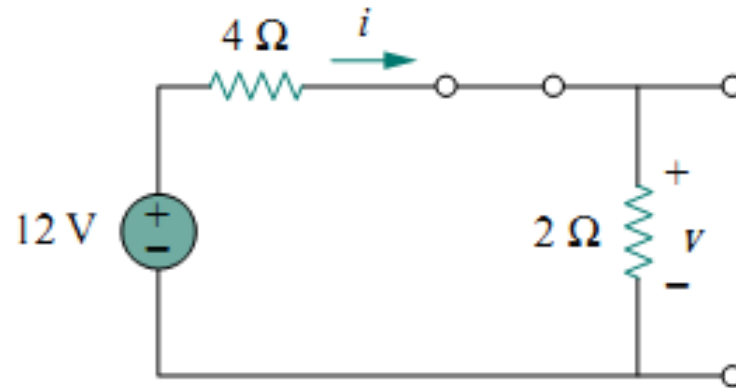


$$i(0^-) = \frac{12}{4 + 2} = 2 \text{ A}, \quad v(0^-) = 2i(0^-) = 4 \text{ V}$$

As the inductor current and the capacitor voltage cannot change abruptly

$$i(0^+) = i(0^-) = 2 \text{ A}, \quad v(0^+) = v(0^-) = 4 \text{ V}$$

$t = 0^+$

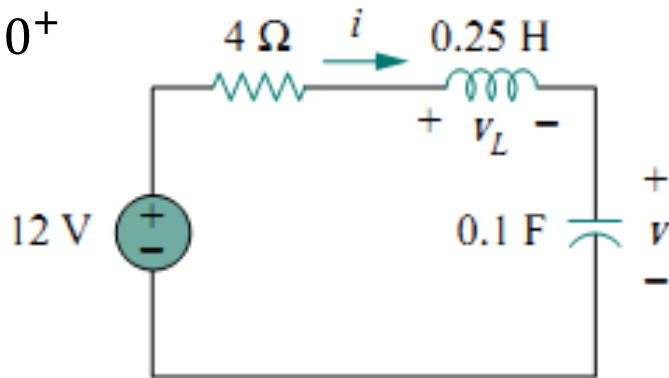

The same current flows through both the inductor and capacitor

$$i_C(0^+) = i(0^+) = 2 \text{ A}$$

$$C \, dv/dt = i_C, \, dv/dt = i_C/C,$$



$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{2}{0.1} = 20 \text{ V/s}$$

$$L \, di/dt = v_L, \, di/dt = v_L/L$$




$$-12 + 4i(0^+) + v_L(0^+) + v(0^+) = 0$$

$$v_L(0^+) = 12 - 8 - 4 = 0$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{0}{0.25} = 0 \text{ A/s}$$


$t \rightarrow \infty$

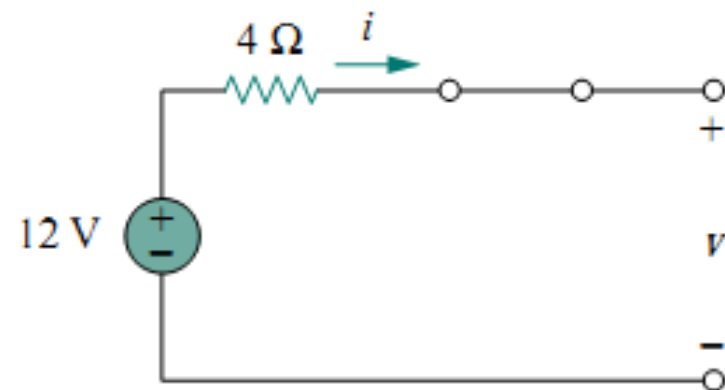

$$i(\infty) = 0 \text{ A}, \quad v(\infty) = 12 \text{ V}$$

Practice Problems

1

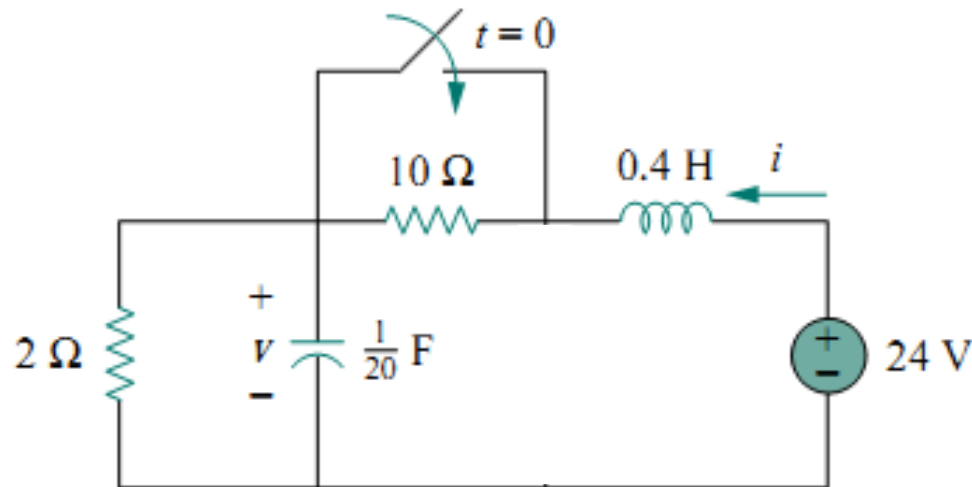


Determine:

(a) $i(0^+)$, $v(0^+)$, (b) $di(0^+)/dt$, $dv(0^+)/dt$, (c) $i(\infty)$, $v(\infty)$.

Answer: (a) 2 A, 4 V, (b) 50 A/s, 0 V/s, (c) 12 A, 24 V.

2

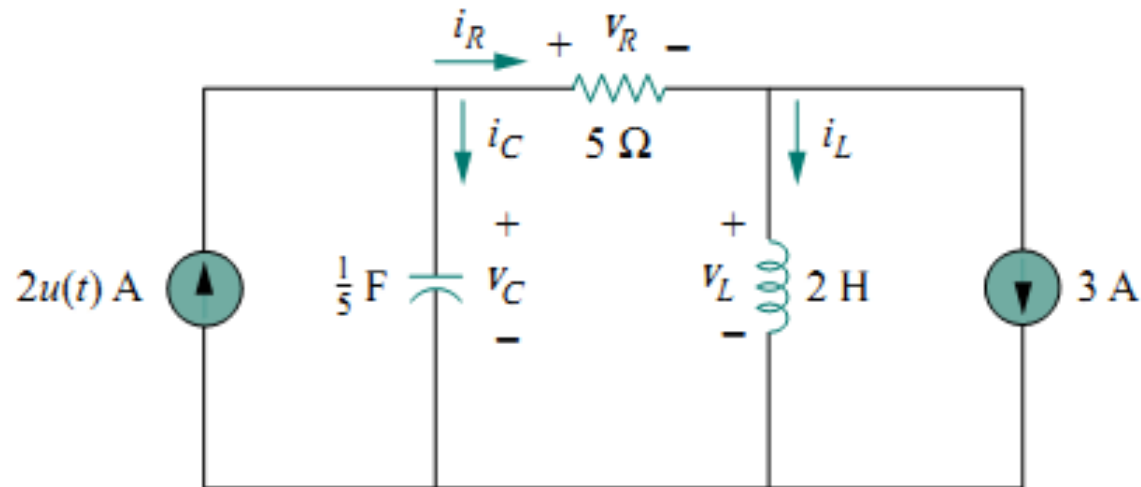


- Find:
- (a) $i_L(0^+)$, $v_C(0^+)$, $v_R(0^+)$,
 - (b) $di_L(0^+)/dt$, $dv_C(0^+)/dt$, $dv_R(0^+)/dt$,
 - (c) $i_L(\infty)$, $v_C(\infty)$, $v_R(\infty)$.

Answer: (a) -3 A, 0 , 0 , (b) 0 , 10 V/s, 0 , (c) -1 A, 10 V, 10 V.

Source Free RLC Circuits


Series RLC Circuit

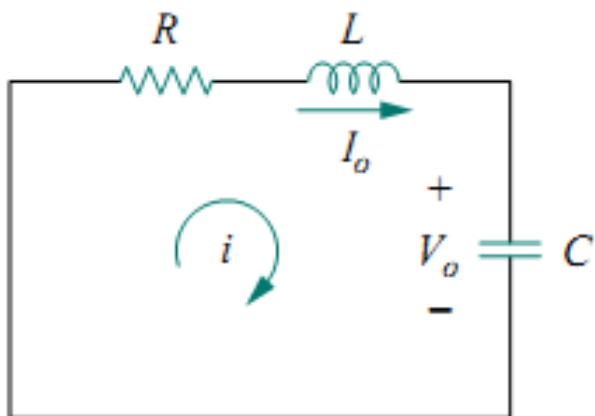

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i \, dt = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

Parallel RLC Circuit

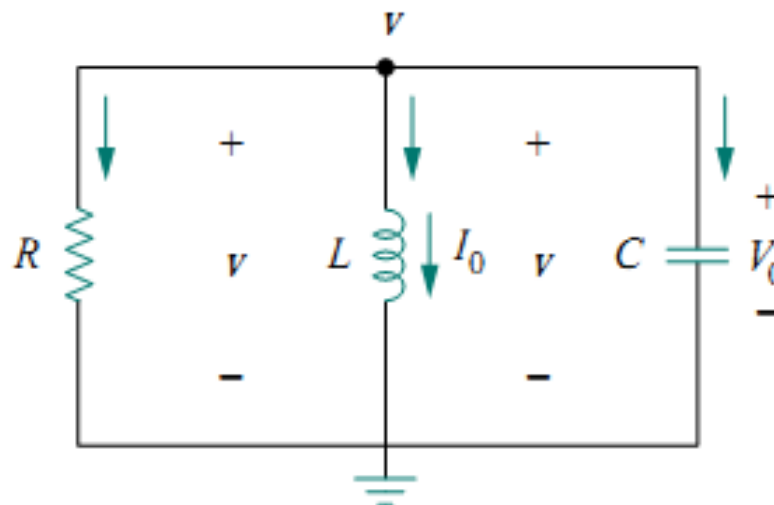

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v \, dt + C \frac{dv}{dt} = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

General Equation

$$\frac{d^2x}{dt^2} + 2\alpha \frac{dx}{dt} + \omega_0^2 x = 0$$

Series RLC Circuit

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Parallel RLC Circuit

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

General Solution

Overdamped Case ($\alpha > \omega_0$)

$$x = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{dx}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Critically Damped Case ($\alpha = \omega_0$)

$$x = e^{-\alpha t} (A_1 t + A_2)$$

$$\frac{dx}{dt} = e^{-\alpha t} (A_1 - \alpha(A_1 t + A_2))$$


Underdamped Case ($\alpha < \omega_0$)

$$x = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$\frac{dx}{dt} = e^{-\alpha t} ((A_2 \omega_d - A_1 \alpha) \cos \omega_d t - (A_1 \omega_d + A_2 \alpha) \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Example

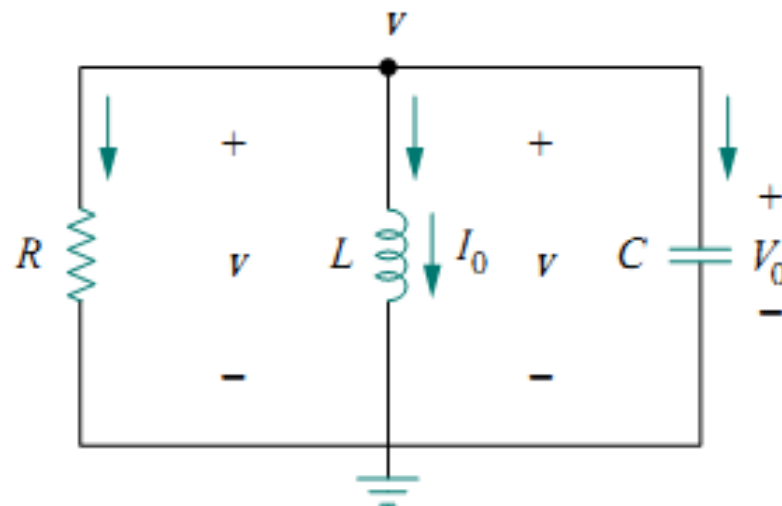

find $v(t)$ for $t > 0$, assuming $v(0) =$


5 V , $i(0) = 0$, $L = 1 \text{ H}$, and $C = 10 \text{ mF}$.

Consider these cases: $R = 1.923 \text{ } \Omega$, $R = 5 \text{ } \Omega$, and $R = 6.25 \text{ } \Omega$.

CASE 1 If $R = 1.923 \text{ } \Omega$, $v(t) = 10.625e^{-2t} - 5.625e^{-50t}$


CASE 2 When $R = 5 \text{ } \Omega$, $v(t) = (5 + 150t)e^{-10t} \text{ V}$

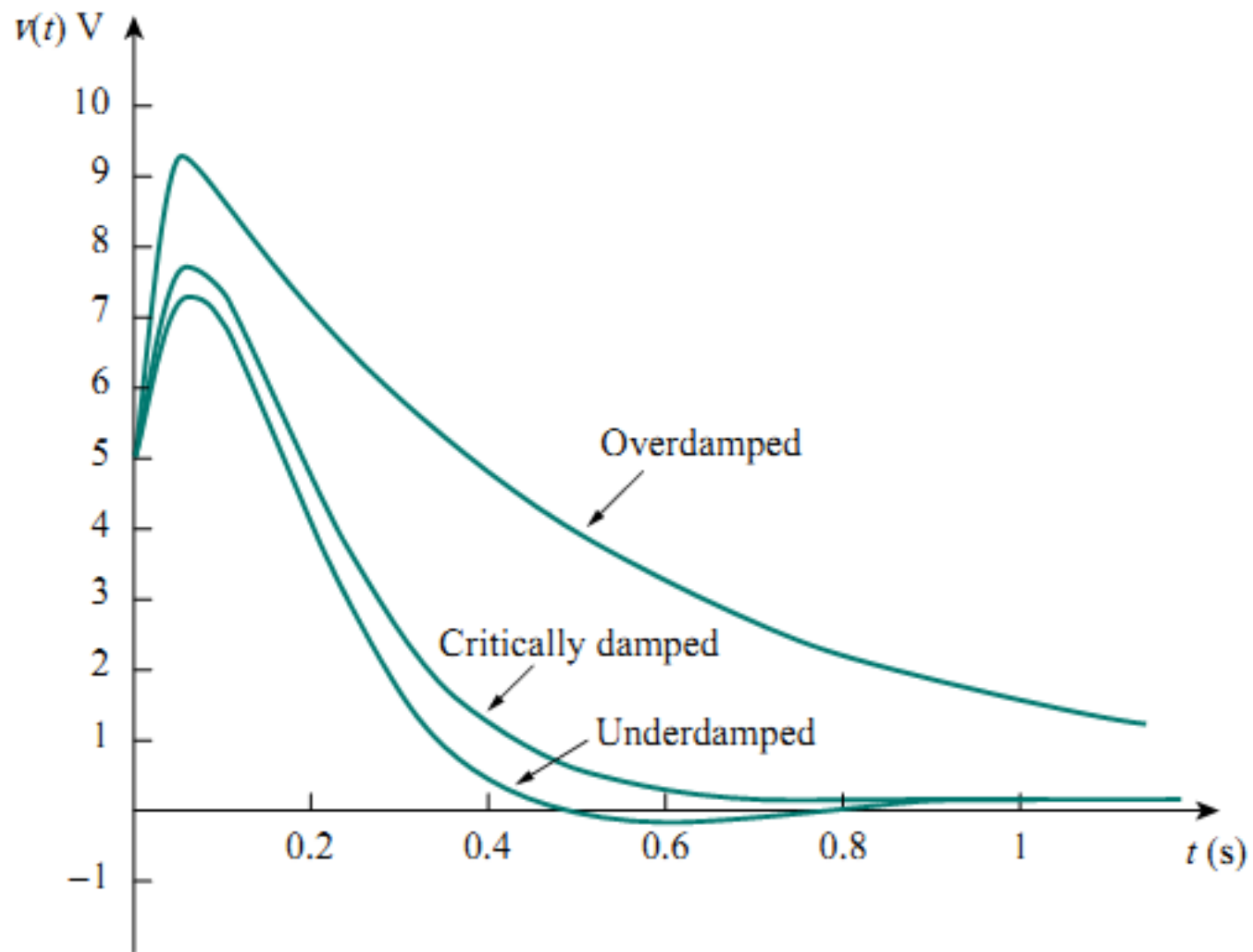CASE 3 When $R = 6.25 \text{ } \Omega$, $v(t) = (5 \cos 6t + 20 \sin 6t)e^{-8t}$



Practice Problem

Find $v(t)$ for $t > 0$.

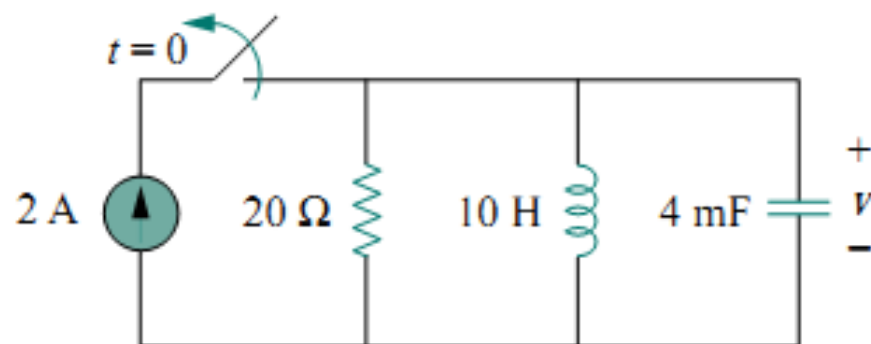


Answer: $66.67(e^{-10t} - e^{-2.5t})\text{ V}$.

Step Response of RLC Circuits


The complete response of the circuit is the sum of the natural response and the forced response.

$$x(t) = x_f(t) + x_n(t)$$

the $x_f = x(\infty)$ is the final value and $x_n(t)$ is the natural response.




The natural response or transient response is the circuit's temporary response that will die out with time.



The forced response or steady-state response is the behavior of the circuit a long time after an external excitation is applied.

Example 1

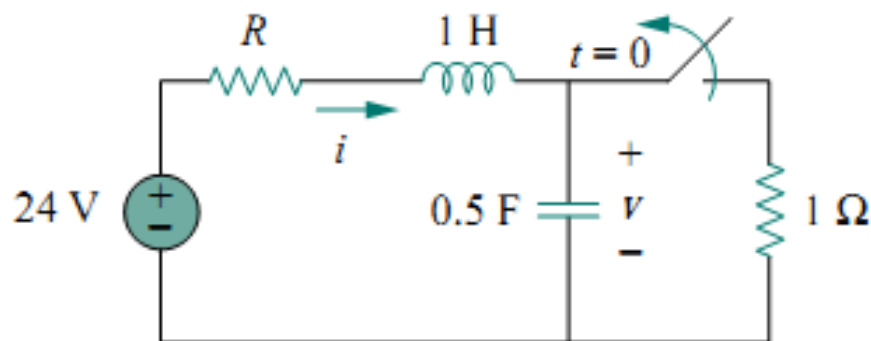

find $v(t)$ and $i(t)$ for $t > 0$. Consider these cases: $R = 5 \Omega$, $R = 4 \Omega$, and $R = 1 \Omega$.

CASE I When $R = 5 \Omega$

$$v(t) = 24 + \frac{4}{3}(-16e^{-t} + e^{-4t}) \text{ V}$$

$$i(t) = \frac{4}{3}(4e^{-t} - e^{-4t}) \text{ A}$$

CASE 2 When $R = 4 \Omega$


$$v(t) = 24 + (-19.5 + 57t)e^{-2t} \text{ V}$$

$$i(t) = (4.5 - 28.5t)e^{-2t} \text{ A}$$


CASE 3 When $R = 1 \Omega$

$$v(t) = 24 + (21.694 \sin 1.936t - 12 \cos 1.936t)e^{-0.5t} \text{ V}$$

$$i(t) = (3.1 \sin 1.936t + 12 \cos 1.936t)e^{-0.5t} \text{ A}$$

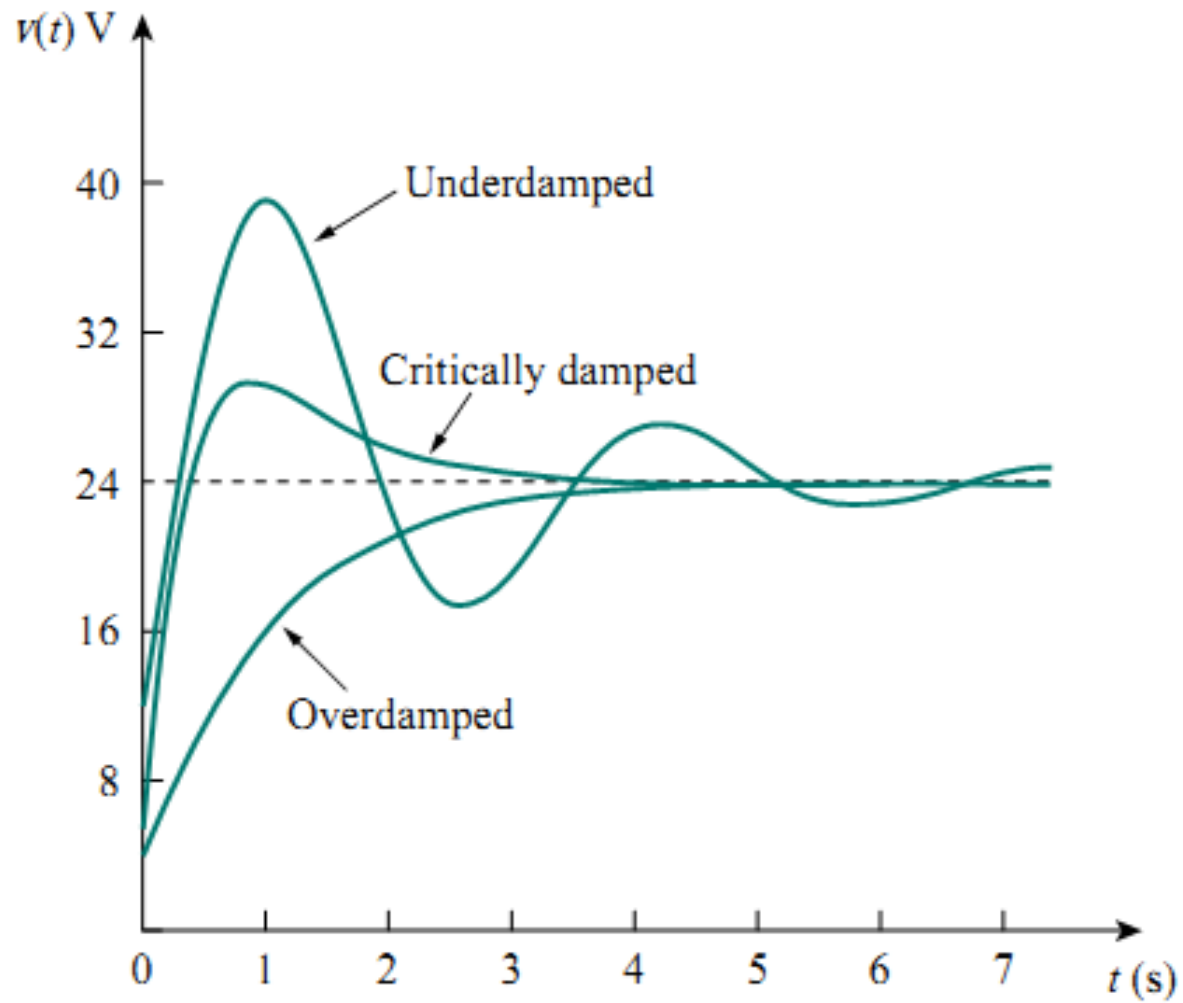


Example 2

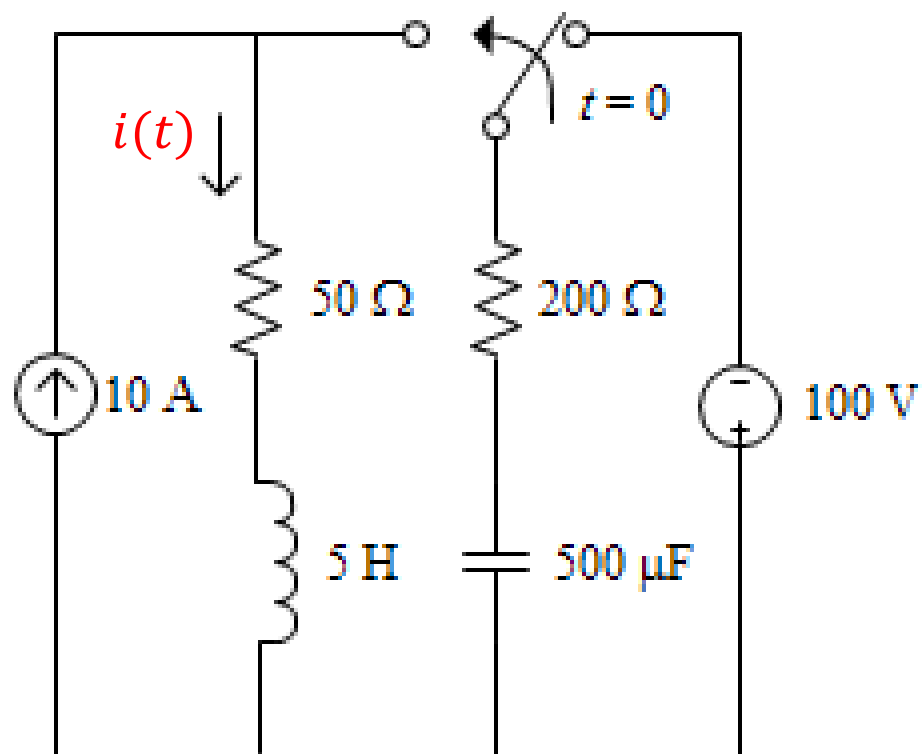

Find $i(t)$ for $-\infty < t < \infty$

$$t = 0^-$$

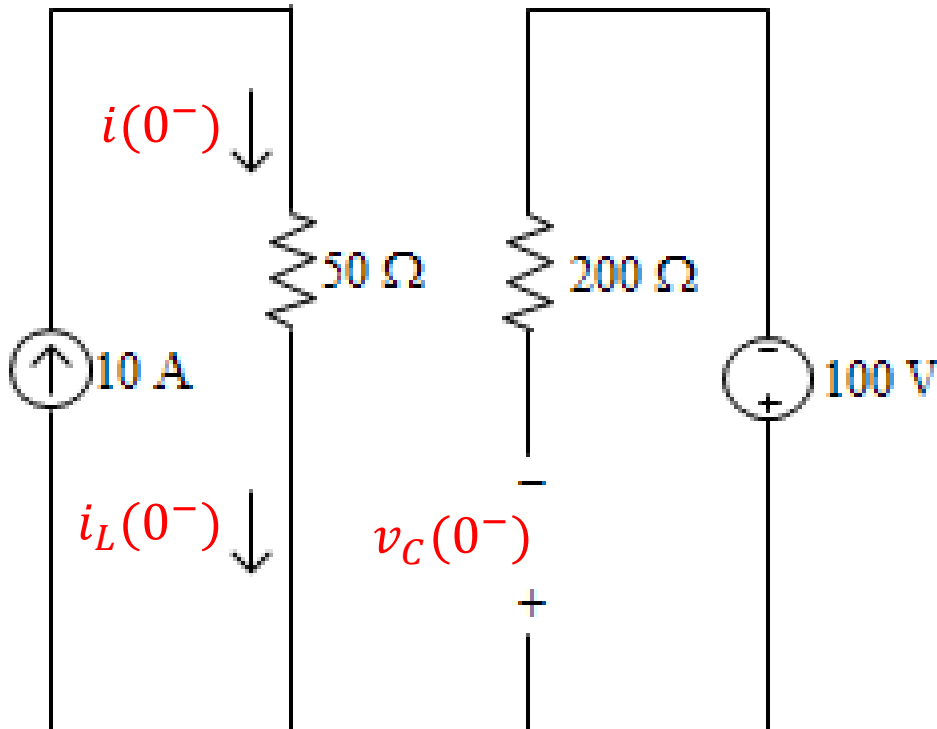


$$i(0^-) = 10\text{ A}$$

$$i_L(0^-) = i(0^-) = 10\text{ A}$$

$$v_C(0^-) = 100\text{ V}$$

$t = 0^+$

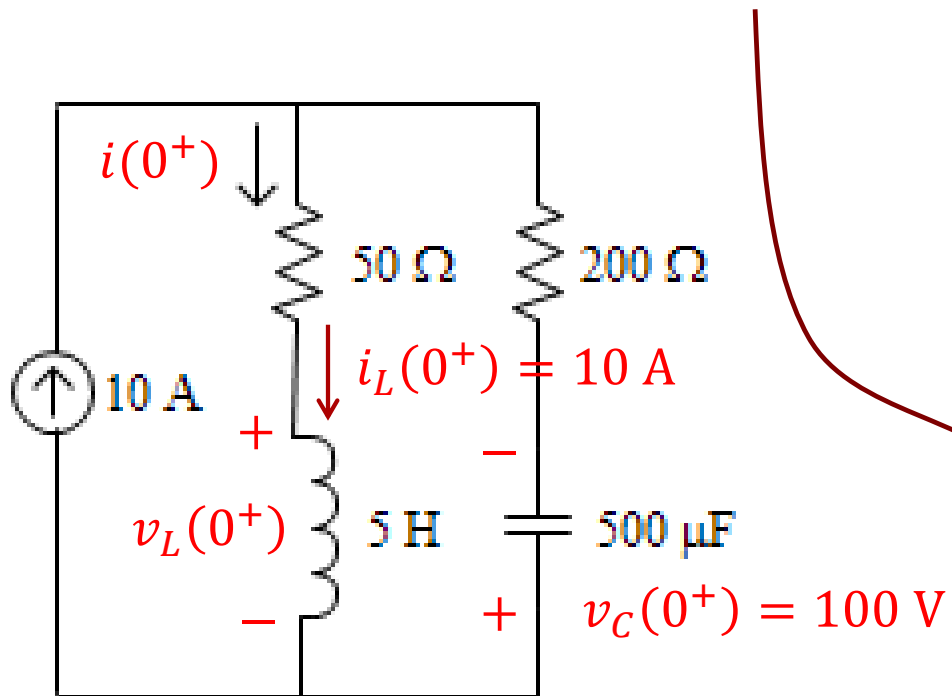


$$i_L(0^+) = i_L(0^-) = 10\text{ A}$$

$$v_C(0^+) = v_C(0^-) = 100\text{ V}$$

$$i(0^+) = i_L(0^+) = 10\text{ A}$$
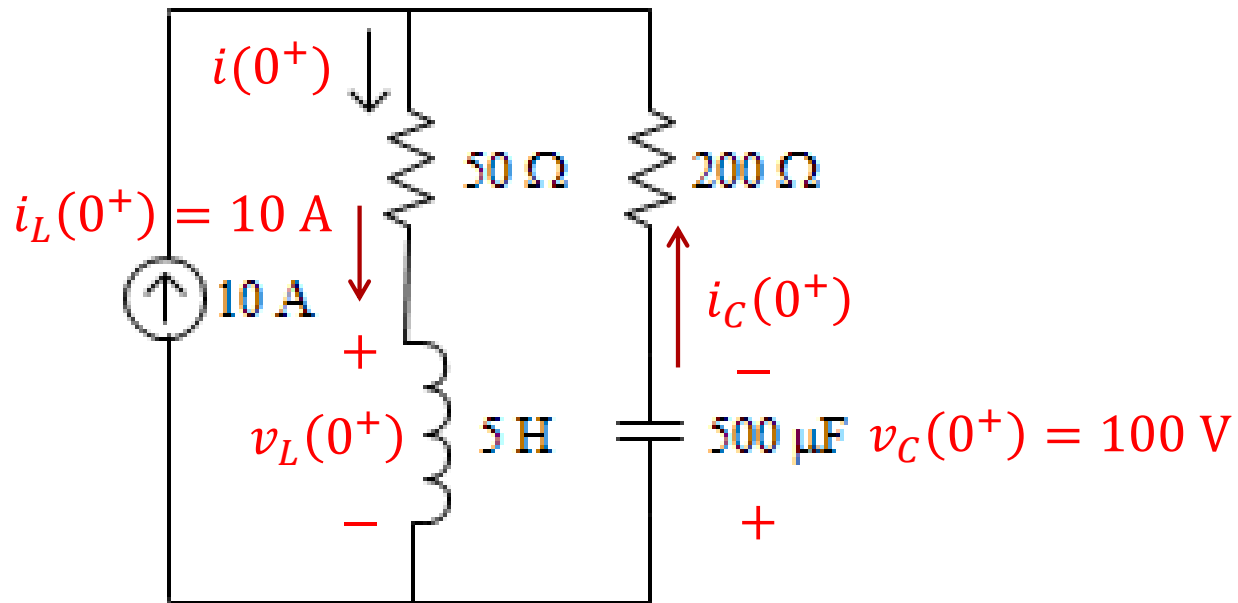
$$\frac{di(0^+)}{dt} = \frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L}$$



$$50 i(0^+) + v_L(0^+) + v_C(0^+) + 200 i_C(0^+) = 0$$


$$50 (10) + v_L(0^+) + 100 + 200 (0) = 0$$

$$v_L(0^+) = -600 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{-600}{5}$$

$$\frac{di(0^+)}{dt} = -120 \text{ A/s}$$

$t \rightarrow \infty$

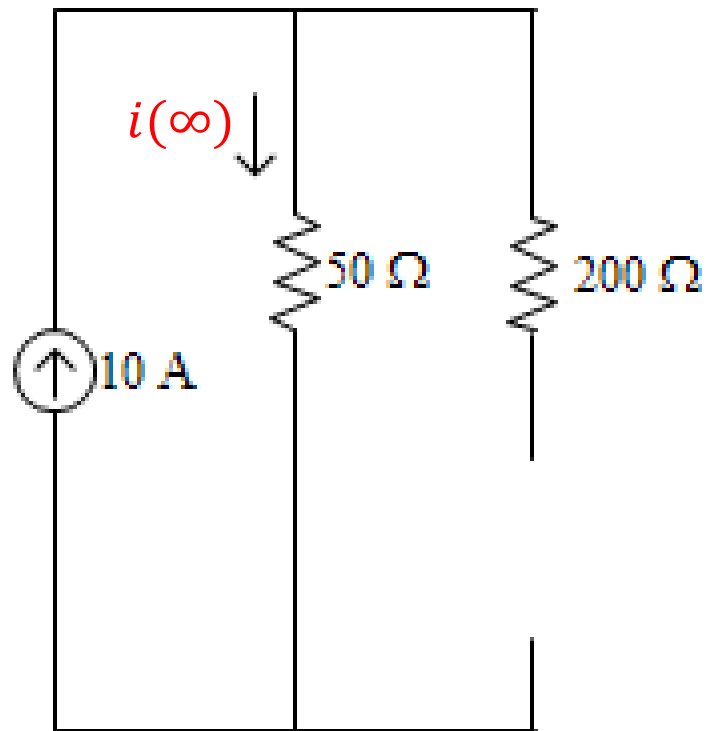

$$i(\infty) = 10 \text{ A}$$

The natural response

$$\alpha = \frac{R}{2L} = \frac{(200 + 50)}{2(5)} = 25$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5(500 \cdot 10^{-6})}} = \frac{100}{5} = 20$$

$$\alpha > \omega_0 \Rightarrow \text{Overdamped}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -25 \pm \sqrt{625 - 400} = -25 \pm 15$$

$$s_1 = -10 \quad s_2 = -40$$

$$i_n(t) = A_1 e^{-10t} + A_2 e^{-40t} \text{ A}$$

The forced response

$$i_f(t) = i(\infty) = 10 \text{ A}$$

The complete response

$$i(t) = i_f(t) + i_n(t)$$

$$i(t) = 10 + A_1 e^{-10t} + A_2 e^{-40t} \text{ A}$$

$$\frac{di(t)}{dt} = -10 A_1 e^{-10t} - 40 A_2 e^{-40t} \text{ A/s}$$

$$t = 0^+$$

$$i(0^+) = 10 + A_1 + A_2$$

$$10 = 10 + A_1 + A_2$$

$$\frac{di(0^+)}{dt} = -10 A_1 - 40 A_2$$

$$-120 = -10 A_1 - 40 A_2$$

$$A_1 + A_2 = 0 \quad (1)$$

$$A_1 + 4 A_2 = 12 \quad (2)$$


From equation (1) and (2) : $A_1 = -4$ $A_2 = 4$

The complete response

$$i(t) = 10 - 4 e^{-10t} + 4 e^{-40t} \text{ A} \quad (t > 0)$$


The complete response for $-\infty < t < \infty$
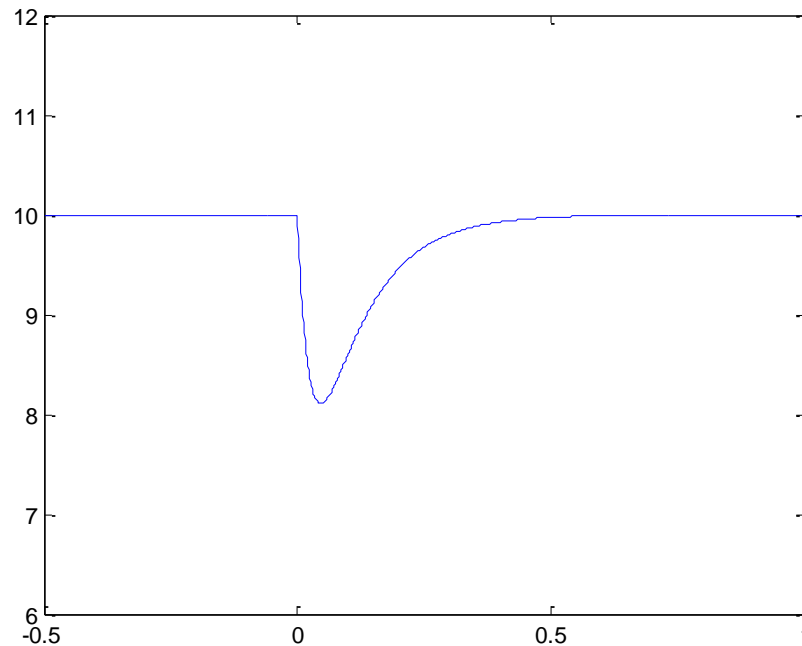
$$i(t) = \begin{cases} 10 \text{ A} & t < 0 \\ 10 - 4 e^{-10t} + 4 e^{-40t} \text{ A} & t > 0 \end{cases}$$




Practice Problem

1 Find $v(t)$ and $v_R(t)$ for $t > 0$.

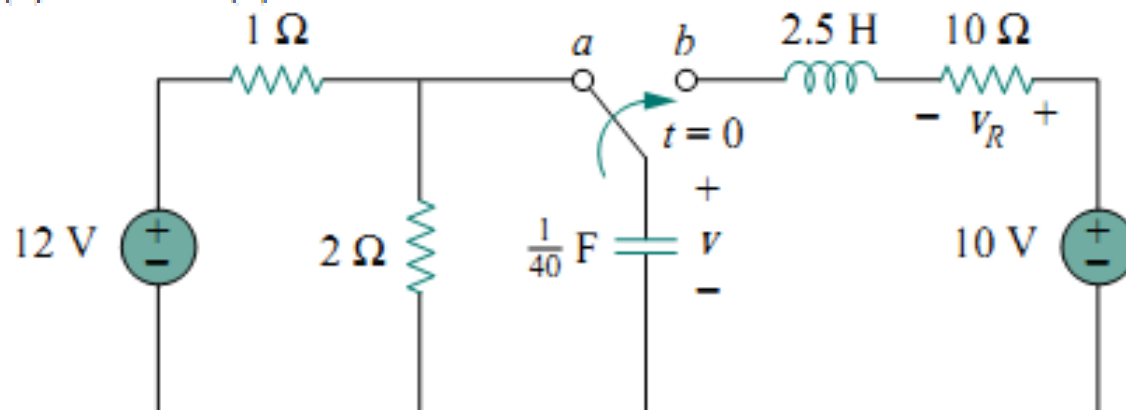

Answer: $10 - (1.1547 \sin 3.464t + 2 \cos 3.464t)e^{-2t}$ V,
 $2.31e^{-2t} \sin 3.464t$ V.

2 Find $i(t)$ and $v(t)$ for $t > 0$

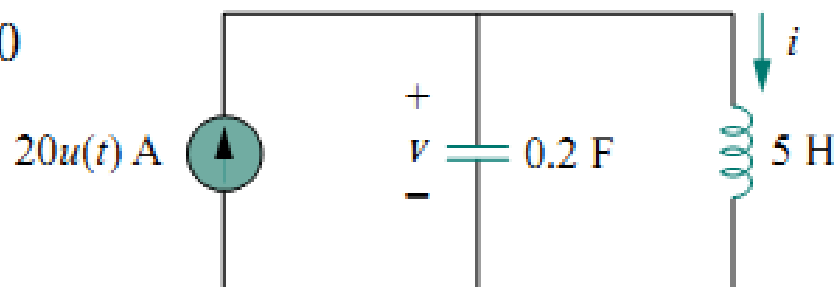

Answer: $20(1 - \cos t)$ A, $100 \sin t$ V.