

# DIODA APPLICATION




Oleh:  
**Suwito**

*mas.suwito@gmail.com*

*masaji@elect-eng.its.ac.id*

**Departemen Teknik Elektro  
Institut Teknologi Sepuluh Nopember  
2009**

# GARIS BEBAN DAN TITIK OPERASI DIODA

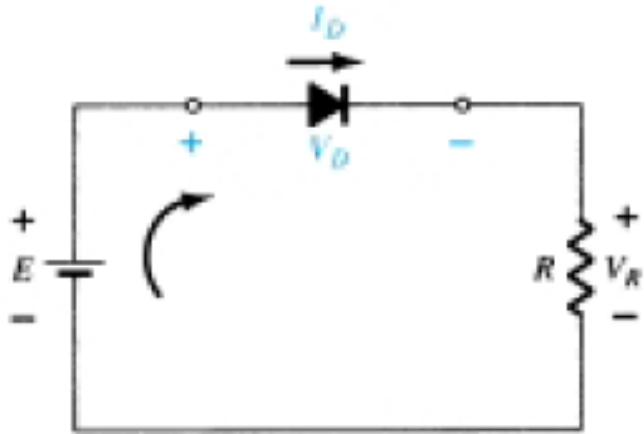

Saat  $V_D = 0 \rightarrow$  Titik Jenuh (Saturation Point)

$$\begin{aligned} E &= V_D + I_D R \\ &= 0 \text{ V} + I_D R \end{aligned}$$

$$I_D = \frac{E}{R} \Big|_{V_D=0 \text{ V}}$$

Saat  $I_D = 0 \rightarrow$  Titik Putus (Cut Off Point)


$$\begin{aligned} E &= V_D + I_D R \\ &= V_D + (0 \text{ A}) R \end{aligned}$$

$$V_D = E \Big|_{I_D=0 \text{ A}}$$


$$E - V_D - V_R = 0$$

$$E = V_D + I_D R$$

# GARIS BEBAN DAN TITIK OPERASI

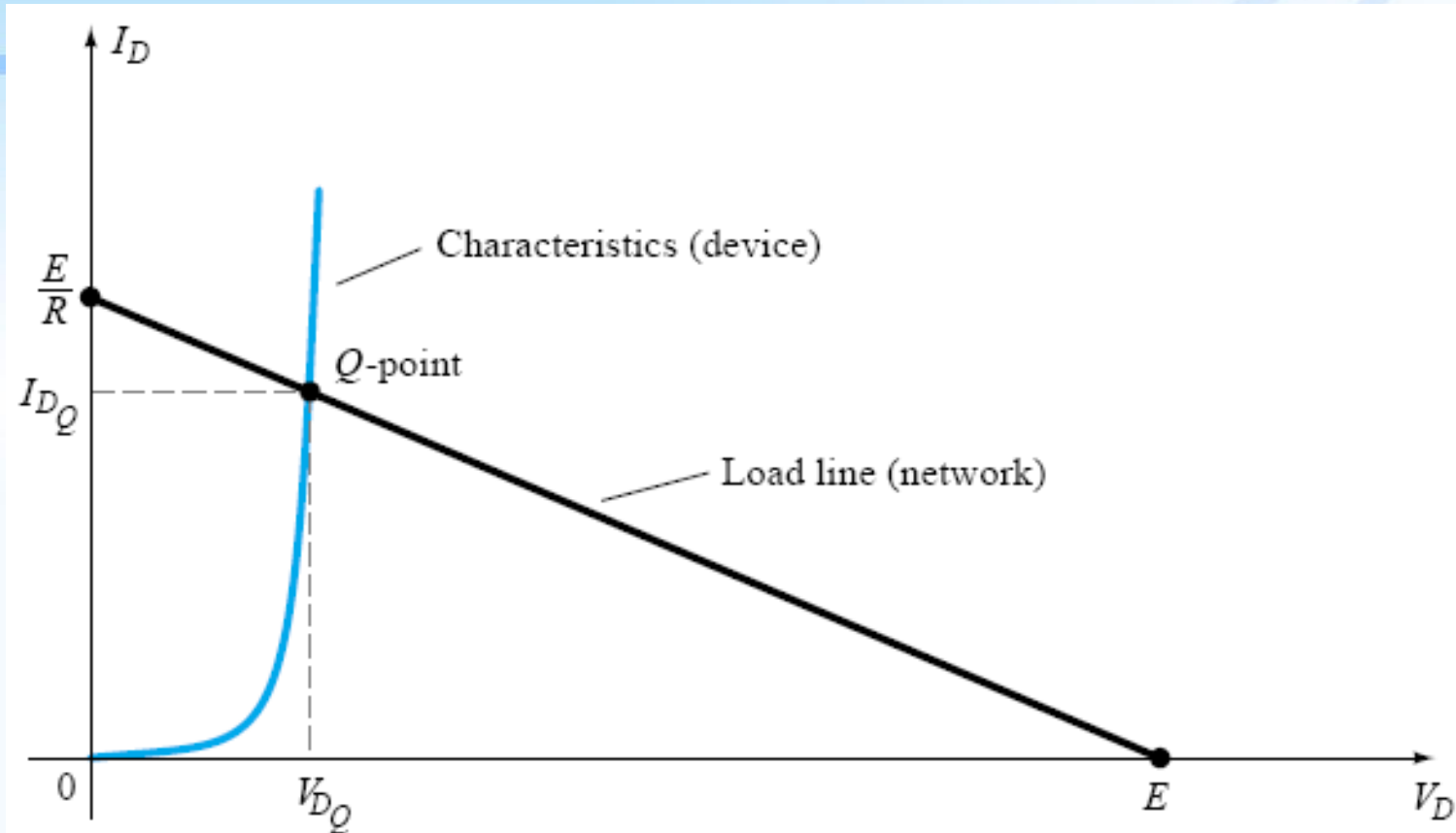

# GARIS BEBAN DAN TITIK OPERASI DIODA

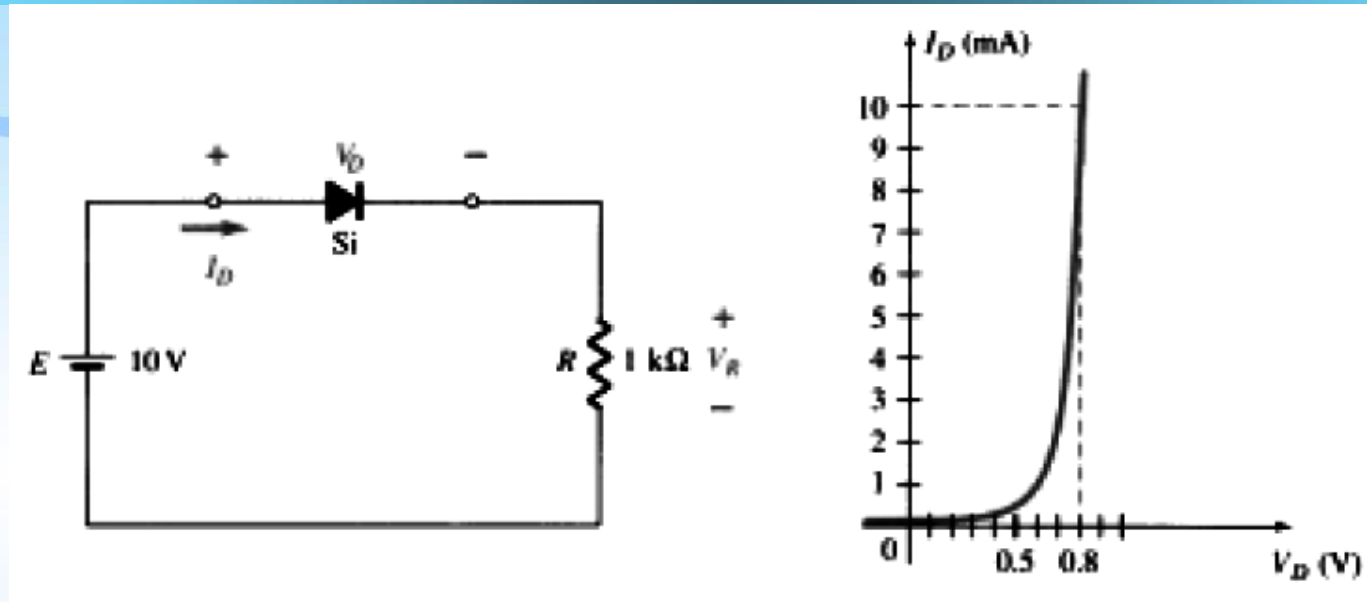

□ Tentukan :

- $V_{DQ}$  dan  $I_{DQ}$ .
- $V_R$ .

# GARIS BEBAN DAN TITIK OPERASI DIODA

## □ Solusi


$$I_D = \frac{E}{R} \Big|_{V_D=0\text{ V}} = \frac{10\text{ V}}{2\text{ k}\Omega} = 10\text{ mA}$$

$$V_D = E \Big|_{I_D=0\text{ A}} = 10\text{ V}$$



$$V_{D_Q} \cong 0.78\text{ V}$$

$$I_{D_Q} \cong 9.25\text{ mA}$$

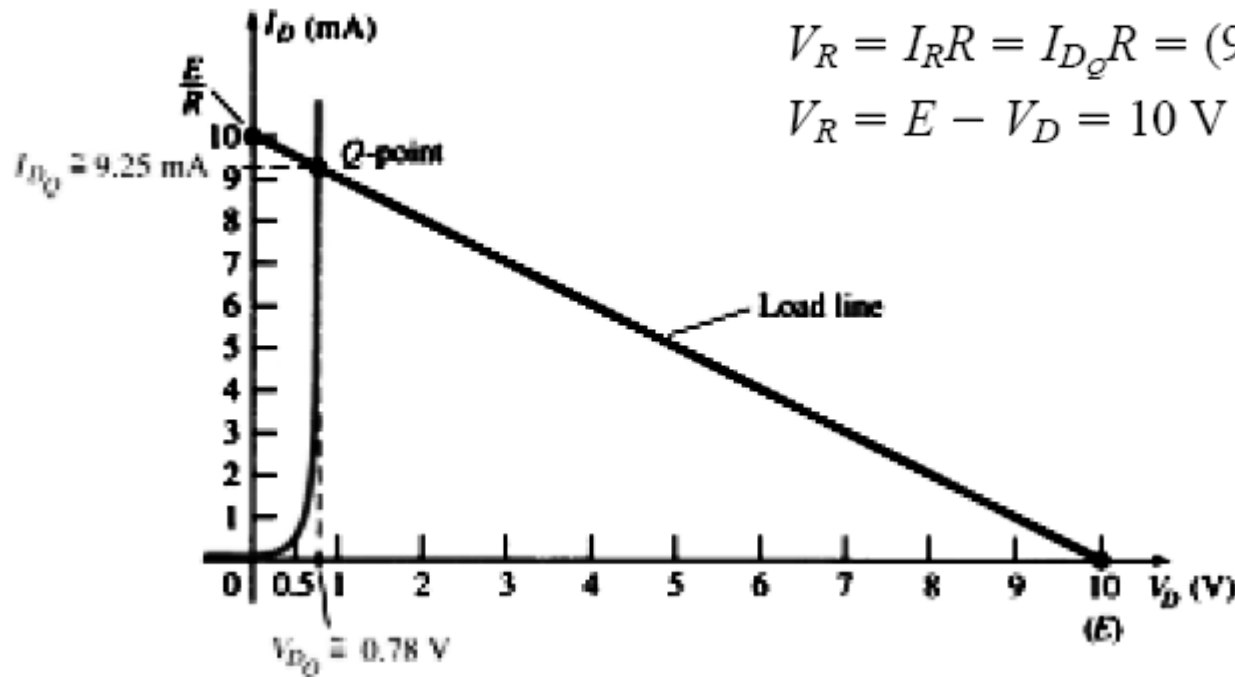

$$V_R = I_R R = I_{D_Q} R = (9.25\text{ mA})(1\text{ k}\Omega) = 9.25\text{ V}$$

$$V_R = E - V_D = 10\text{ V} - 0.78\text{ V} = 9.22\text{ V}$$

# GARIS BEBAN DAN TITIK OPERASI DIODA

□ Jika pendekatannya dengan model dioda sederhana

$$I_D = \frac{E}{R} \Big|_{V_D=0\text{ V}} = \frac{10\text{ V}}{2\text{ k}\Omega} = 10\text{ mA}$$

$$V_D = E \Big|_{I_D=0\text{ A}} = 10\text{ V}$$




$$V_{D_Q} = 0.7\text{ V}$$

$$I_{D_Q} = 9.25\text{ mA}$$


$$V_R = I_R R = I_{D_Q} R = (9.25\text{ mA})(1\text{ k}\Omega) = 9.25\text{ V}$$
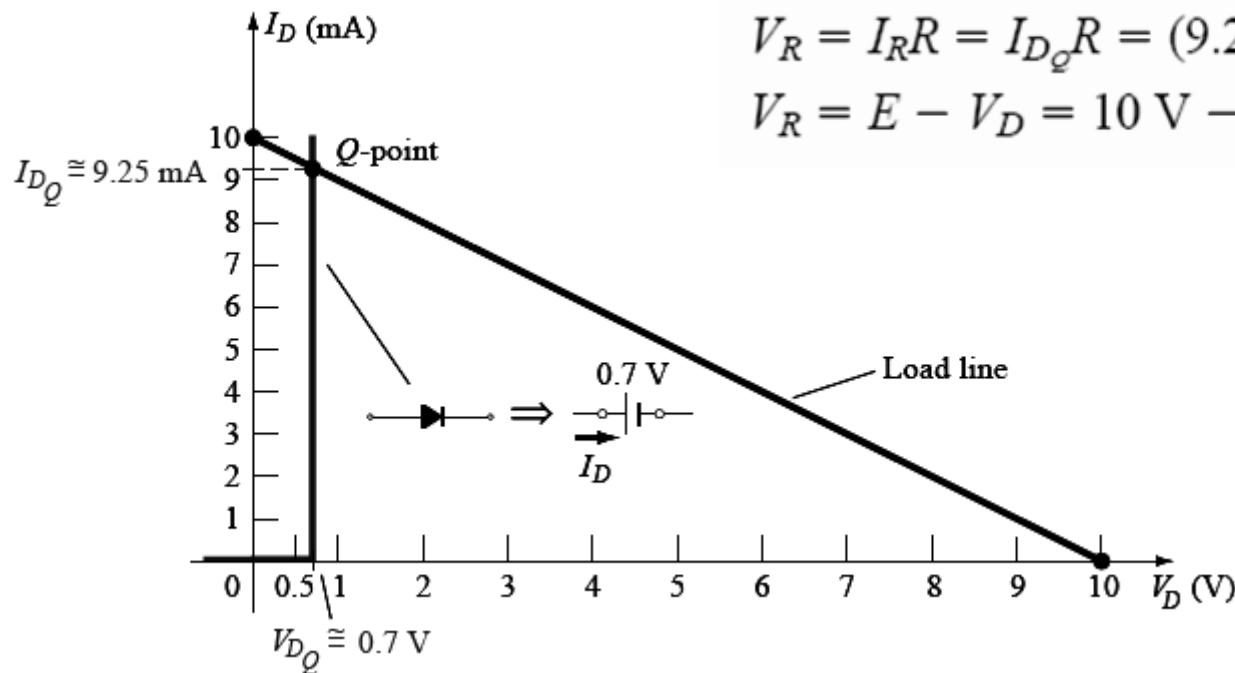
$$V_R = E - V_D = 10\text{ V} - 0.70\text{ V} = 9.3\text{ V}$$


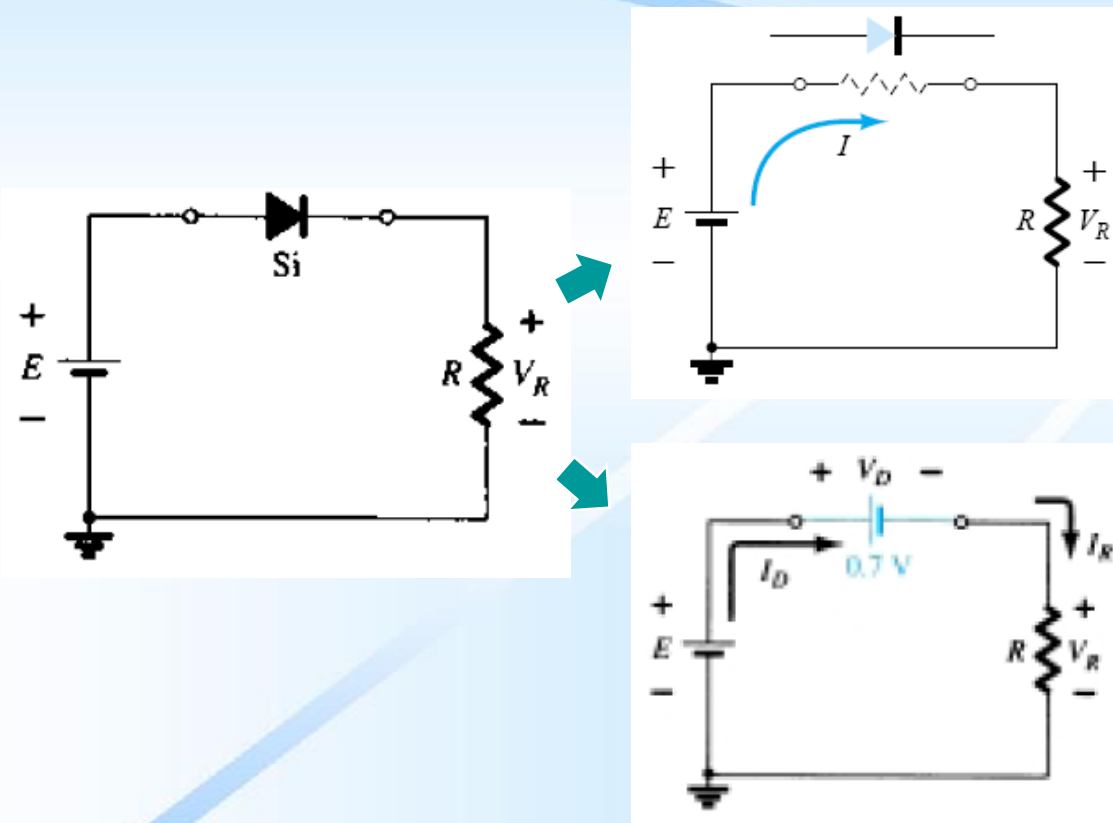
# DC INPUT

- ❑ Dioda dikatakan dalam kondisi “ON” jika arus  $I_D$  dari sumber searah dengan tanda pada simbol dioda atau forward bias.






$$V_D = V_T$$

$$V_R = E - V_T$$

$$I_D = I_R = \frac{V_R}{R}$$

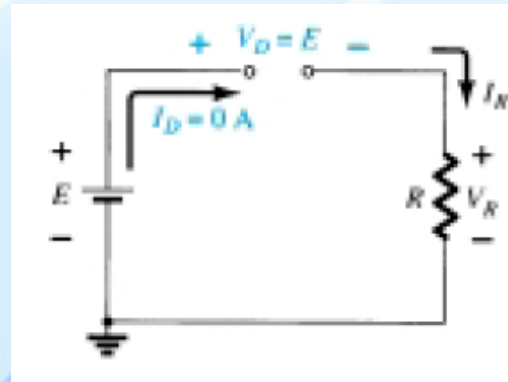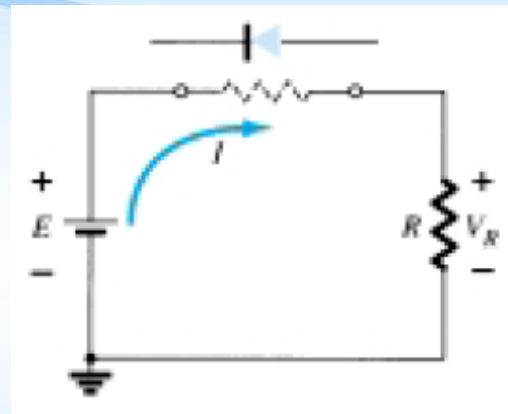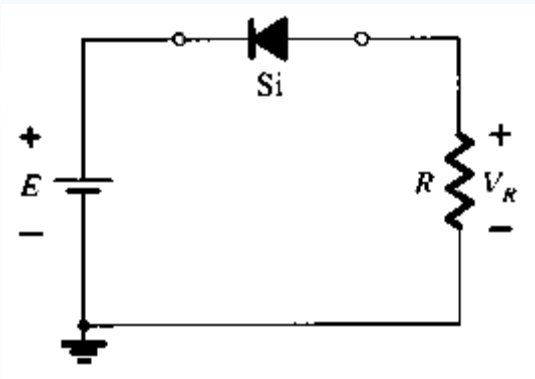
# DC INPUT

- ❑ Dioda dikatakan dalam kondisi “OFF” jika arus  $I_D$  dari sumber berlawanan arah dengan tanda pada simbol dioda atau forward bias.






## DC INPUT

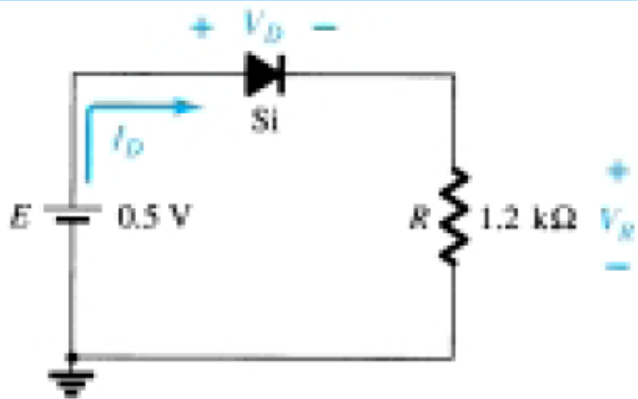


$$I_D = 0\text{ A}$$

$$V_R = I_R R = I_D R = (0\text{ A}) 1.2\text{ k}\Omega = 0\text{ V}$$

$$V_D = E = 0.5\text{ V}$$

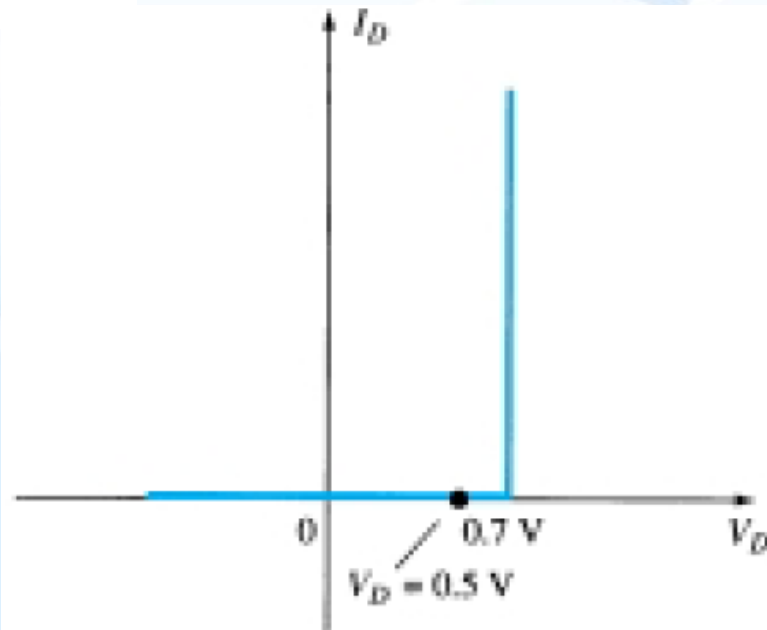



## DC INPUT

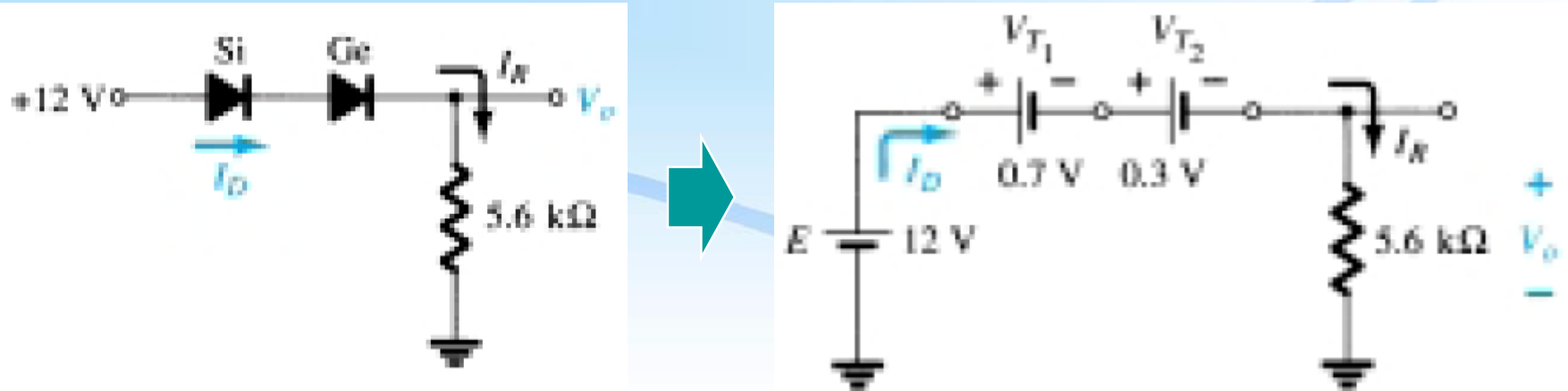

$$V_o = E - V_{T_1} - V_{T_2} = 12 \text{ V} - 0.7 \text{ V} - 0.3 \text{ V} = \mathbf{11 \text{ V}}$$




$$I_D = I_R = \frac{V_R}{R} = \frac{V_o}{R} = \frac{11 \text{ V}}{5.6 \text{ k}\Omega} \cong \mathbf{1.96 \text{ mA}}$$

## DC INPUT

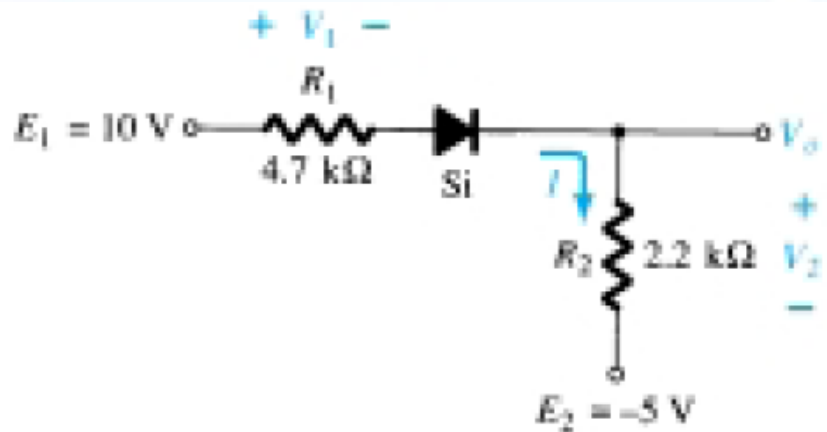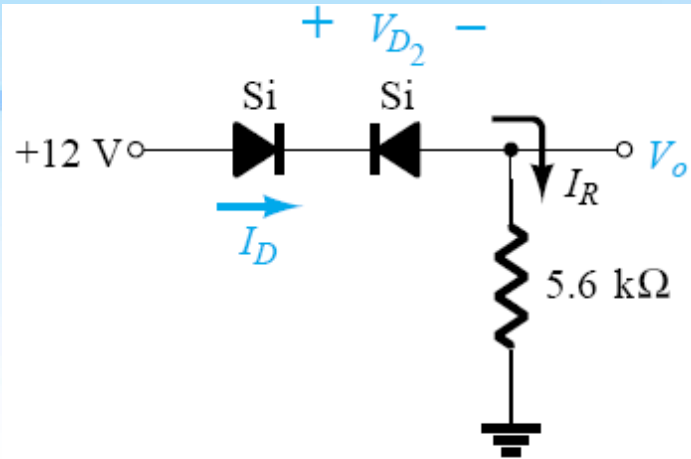




PR

# OR GATE DENGAN DIODA

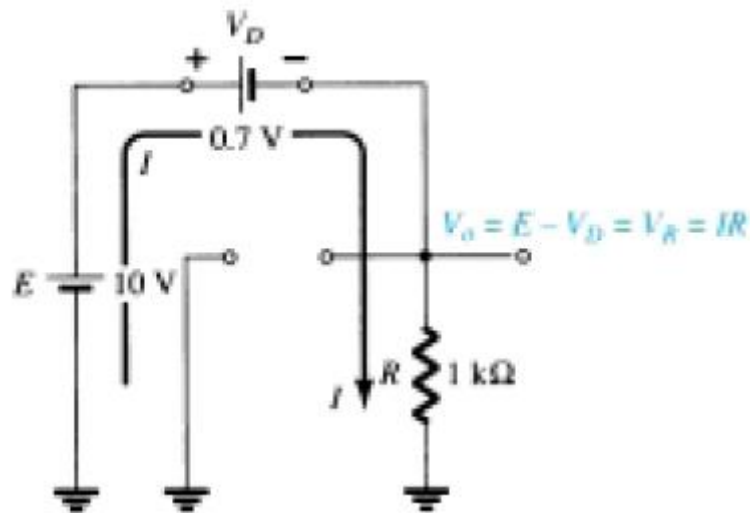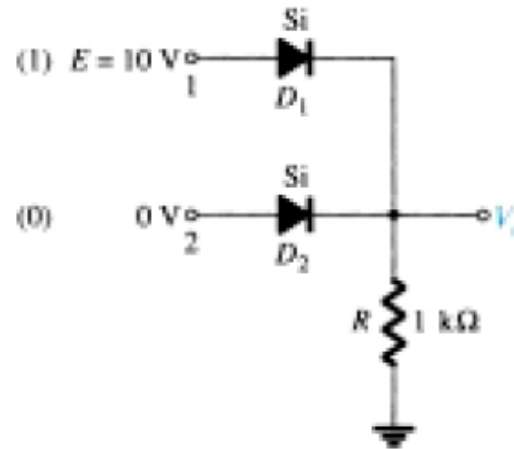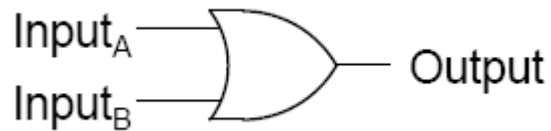



$$I = \frac{E - V_D}{R} = \frac{10 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = 9.3 \text{ mA}$$

# AND GATE DENGAN DIODA

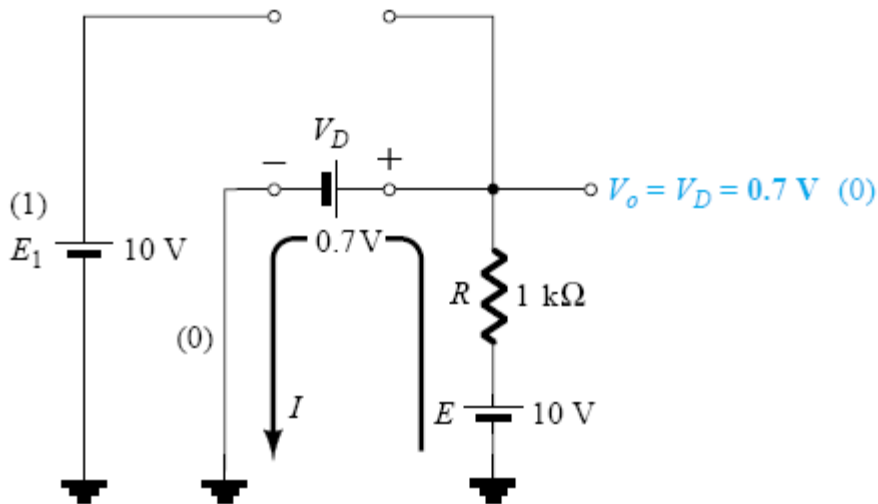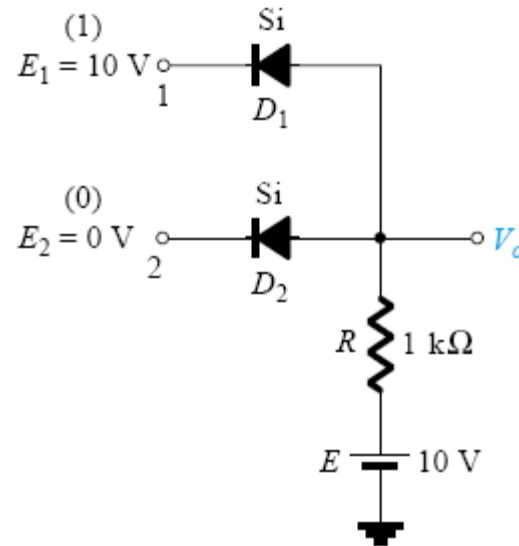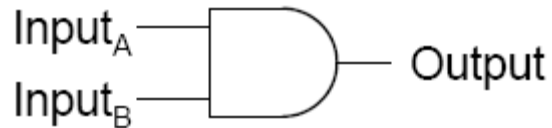

$$I = \frac{E - V_D}{R} = \frac{10\text{ V} - 0.7\text{ V}}{1\text{ k}\Omega} = 9.3\text{ mA}$$

# HALF WAVE RECTIFICATION

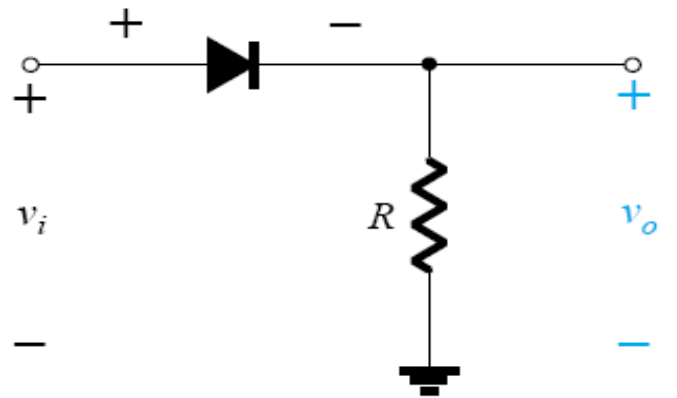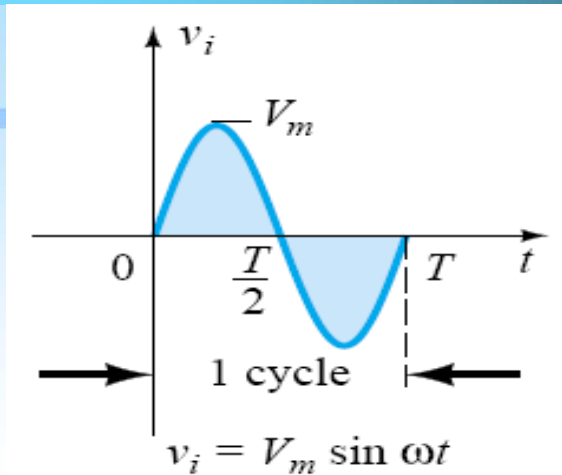


$$V_{eff} = V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$


- ❑ Tegangan (arus) efektif atau rms (*root-mean-square*) adalah tegangan (arus) yang terukur oleh voltmeter (amper-meter).

# AC INPUT → HALF WAVE RECTIFIER


Saat Fase Positif

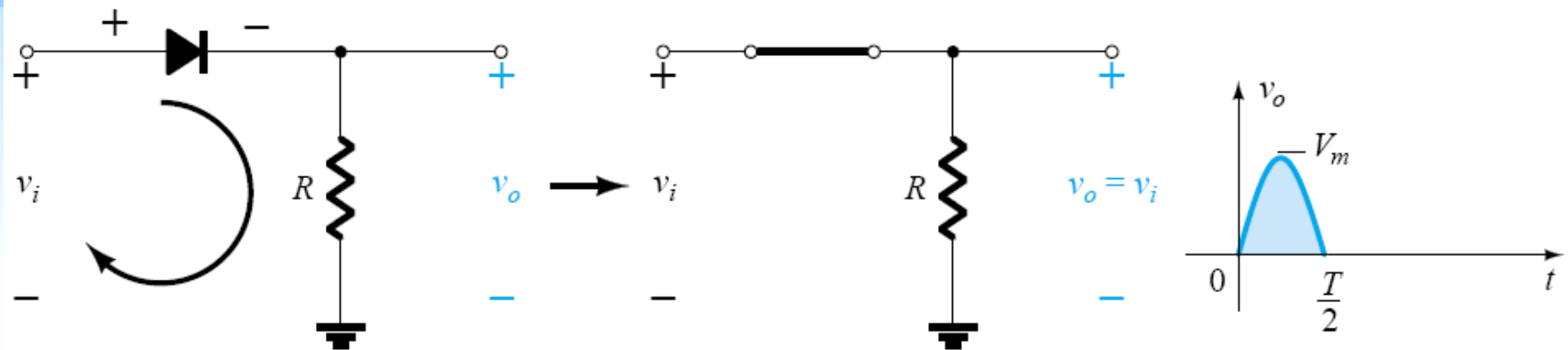

Saat Fase Negatif

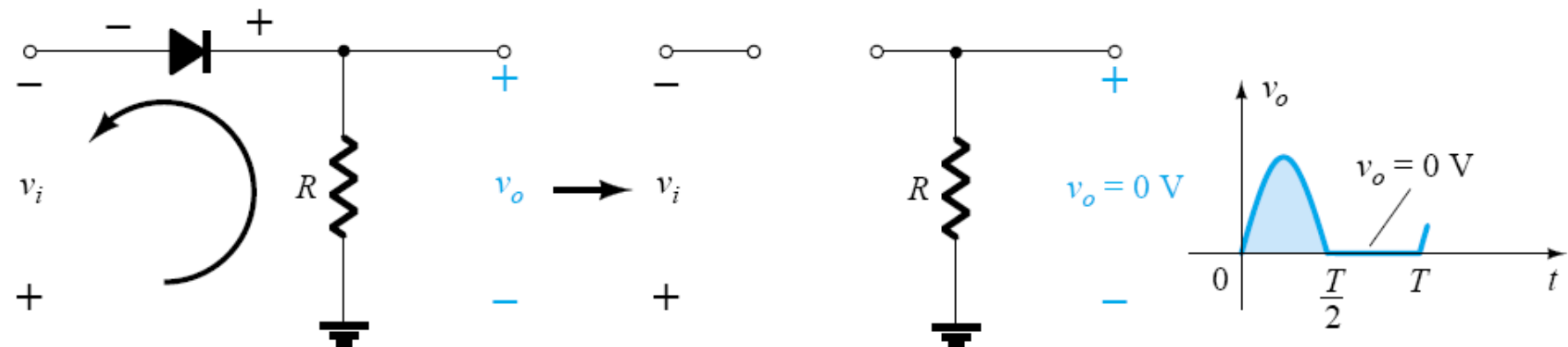

# AC INPUT → HALF WAVE RECTIFIER

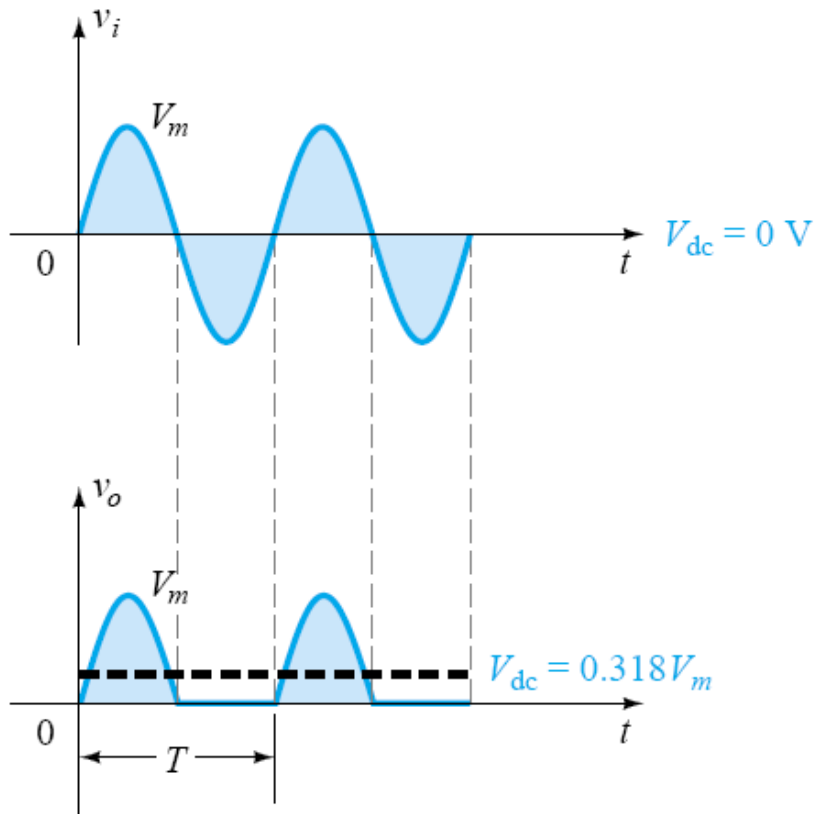

$V_{avg} = \text{Luasan kurva} / \text{Perioda}$

$$\text{area} = \int_0^{\pi} I_m \sin \alpha \, d\alpha = -I_m \cos \alpha \Big|_0^{\pi} = 2I_m$$


$$T = 2\pi$$

$$I_{avg} = \frac{2I_m}{2\pi} = \frac{I_m}{\pi} = 0.318I_m$$

$$V_{dc} = 0.318V_m$$









# AC INPUT → HALF WAVE RECTIFIER

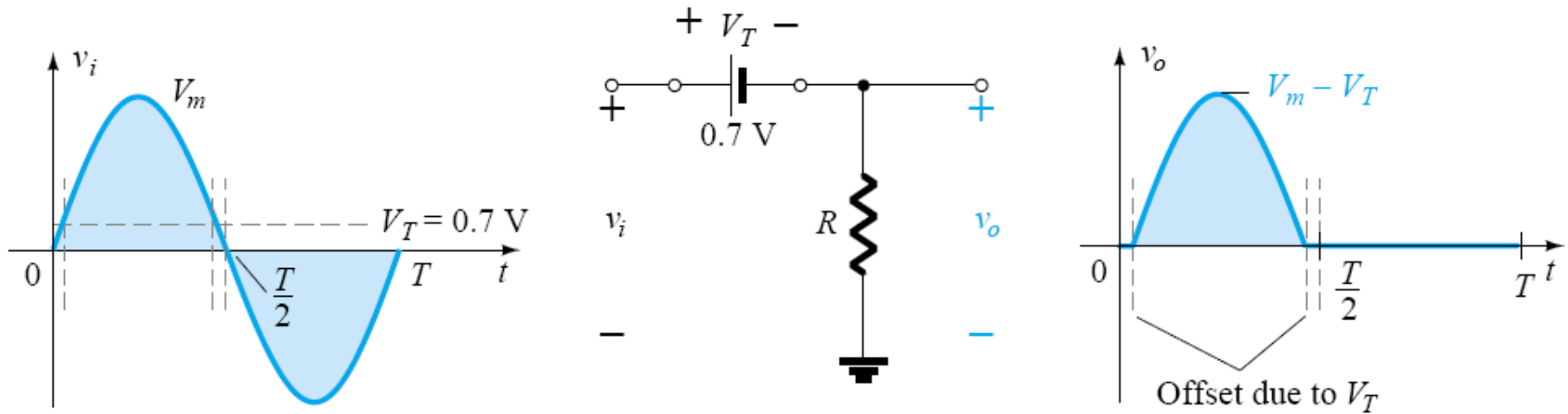


$$V_{dc} \cong 0.318(V_m - V_T)$$

## AC INPUT → HALF WAVE RECTIFIER

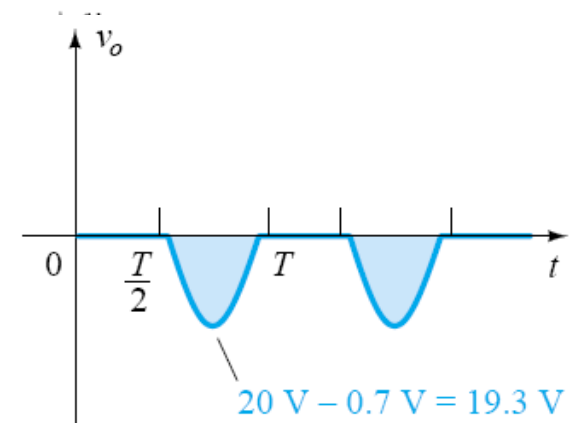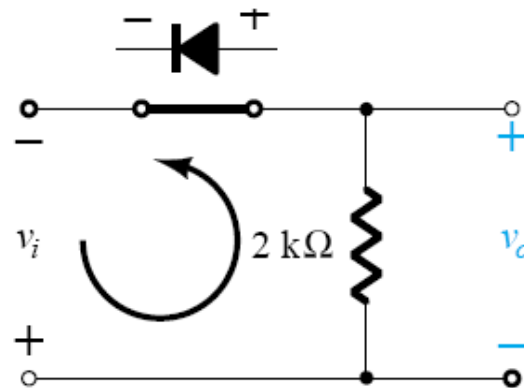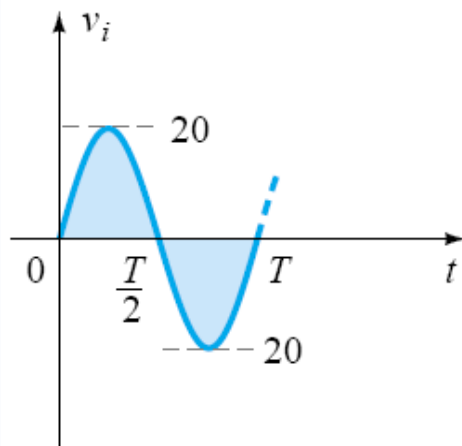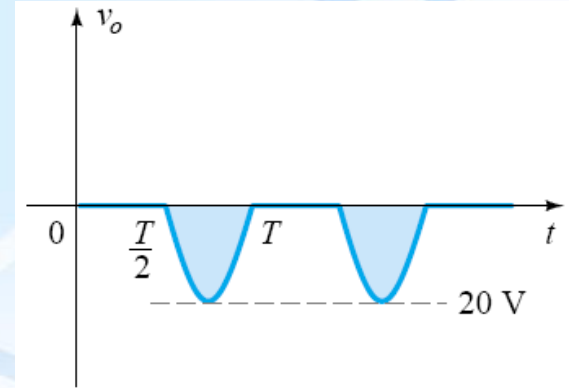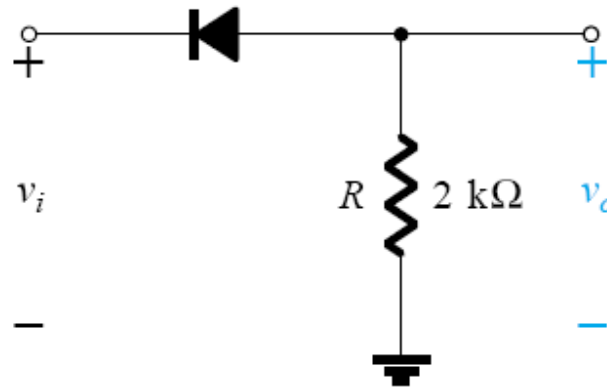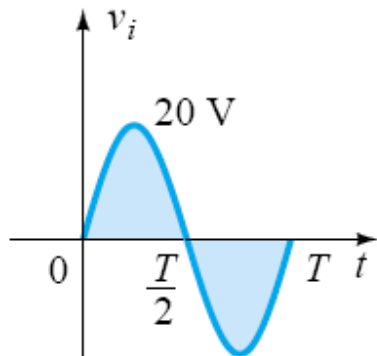

$$V_{dc} \cong -0.318(V_m - 0.7 \text{ V}) = -0.318(19.3 \text{ V}) \cong -6.14 \text{ V}$$

# PEAK INVERSE VOLTAGE (PIV)



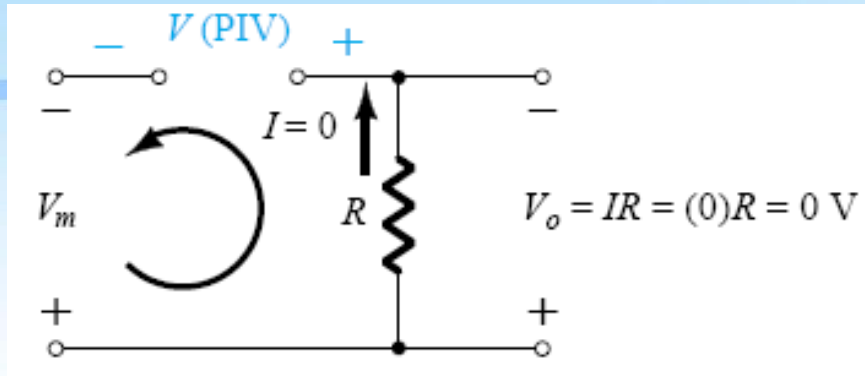


$$\text{PIV rating} \geq V_m$$

- ❑ PIV (*peak-inverse voltage*) atau tegangan puncak balik adalah Tegangan maksimum yang harus ditahan oleh dioda.
- ❑ Karena pada saat dioda mendapat bias mundur (balik) maka tidak ada arus yang mengalir dan semua tegangan dari sumber berada pada dioda.


# FULL-WAVE RECTIFICATION

## Bridge Network

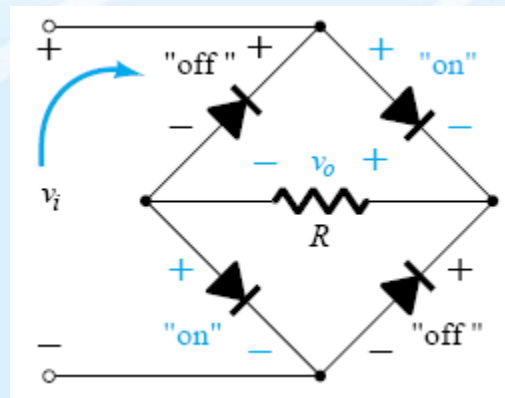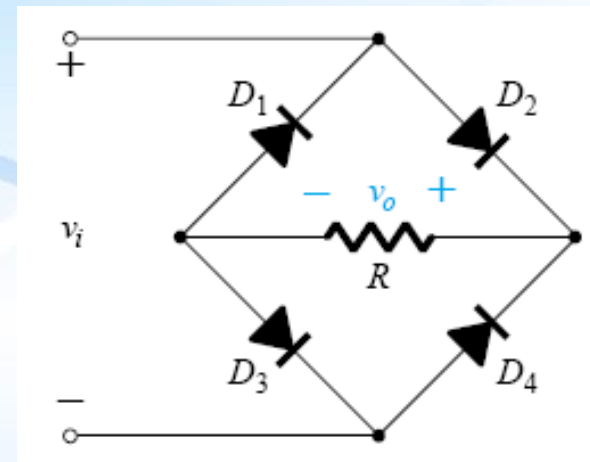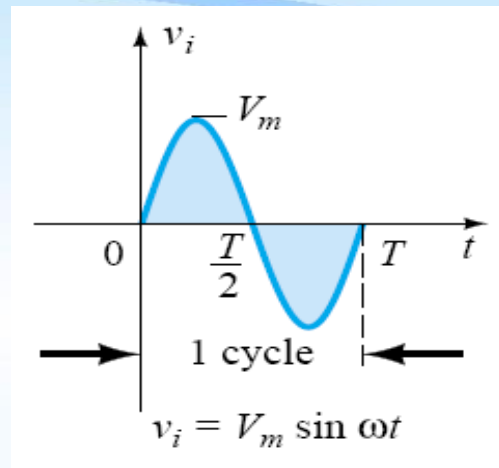


# FWR → BRIDGE NETWORK

## FASE POSITIF

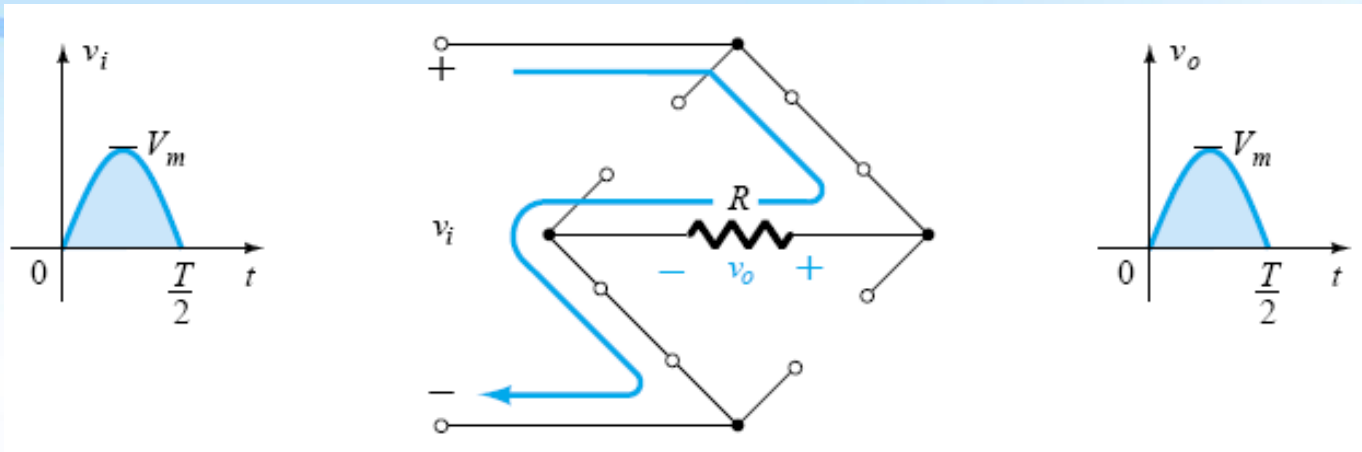


## FASE NEGATIF

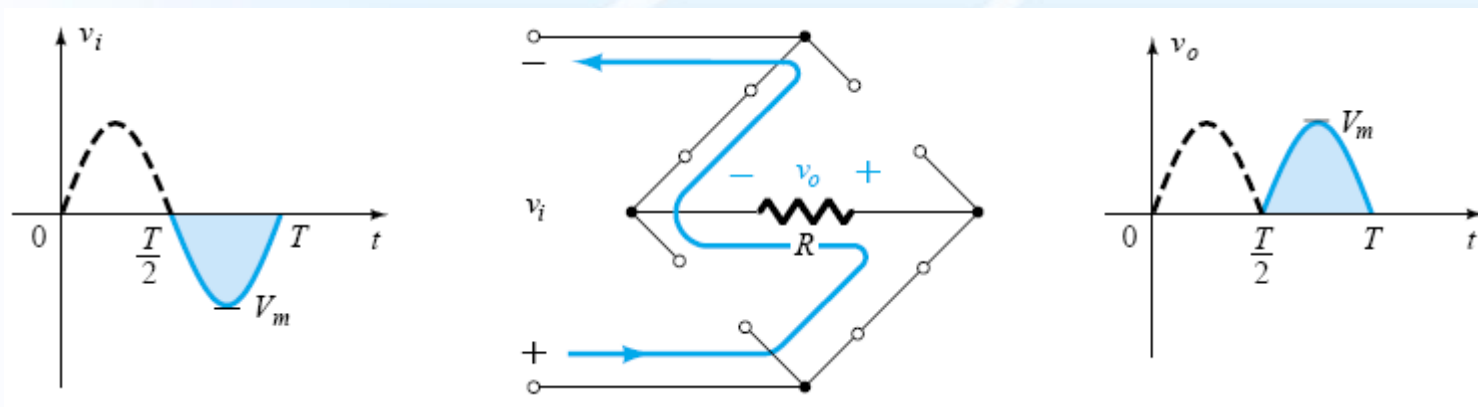

# FWR → BRIDGE NETWORK


Dengan Pendekatan Dioda Ideal

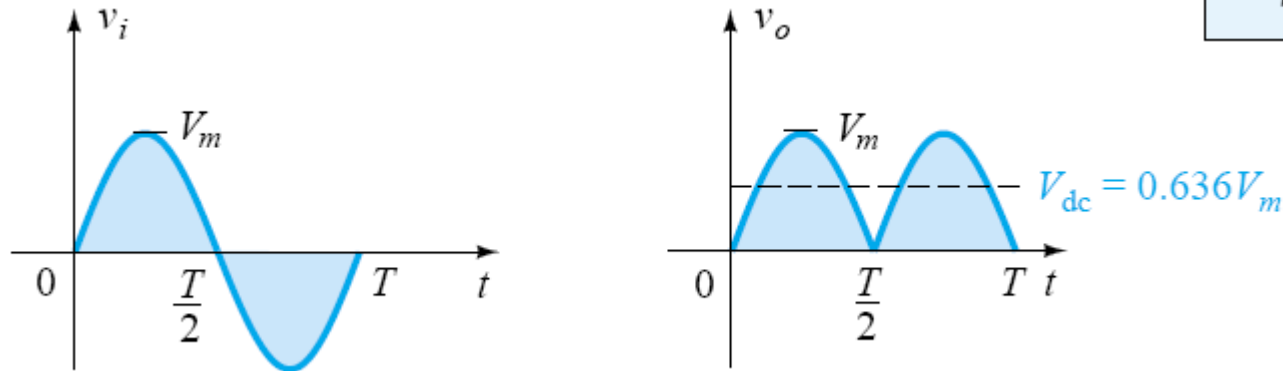

$$V_{dc} = 0.636V_m$$

$$PIV \geq V_m$$


Dengan Pendekatan Dioda Sederhana

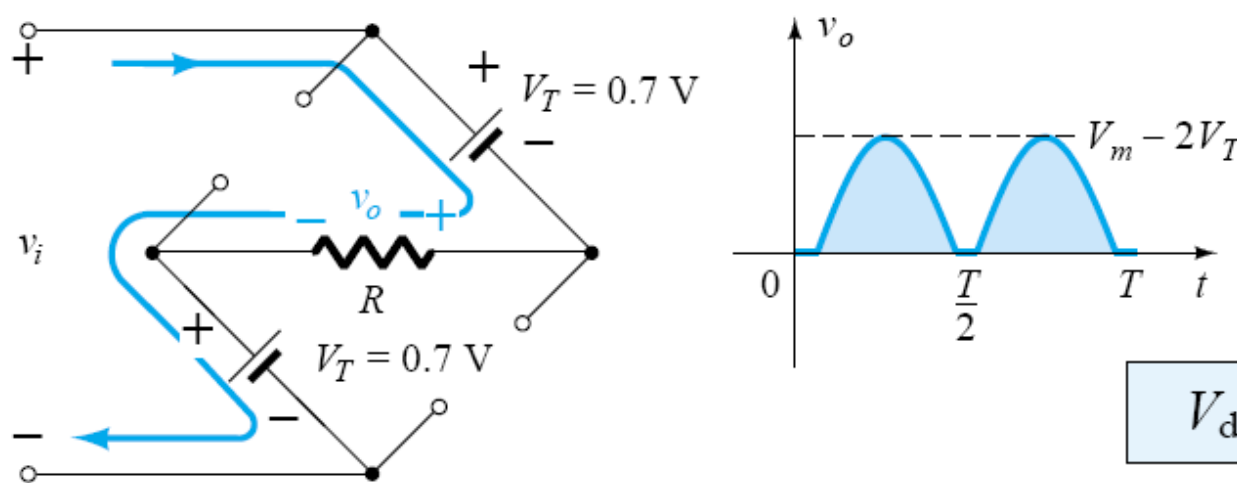

$$V_{dc} \approx 0.636(V_m - 2V_T)$$


# FULL-WAVE RECTIFICATION

## Center-Tapped Transformer

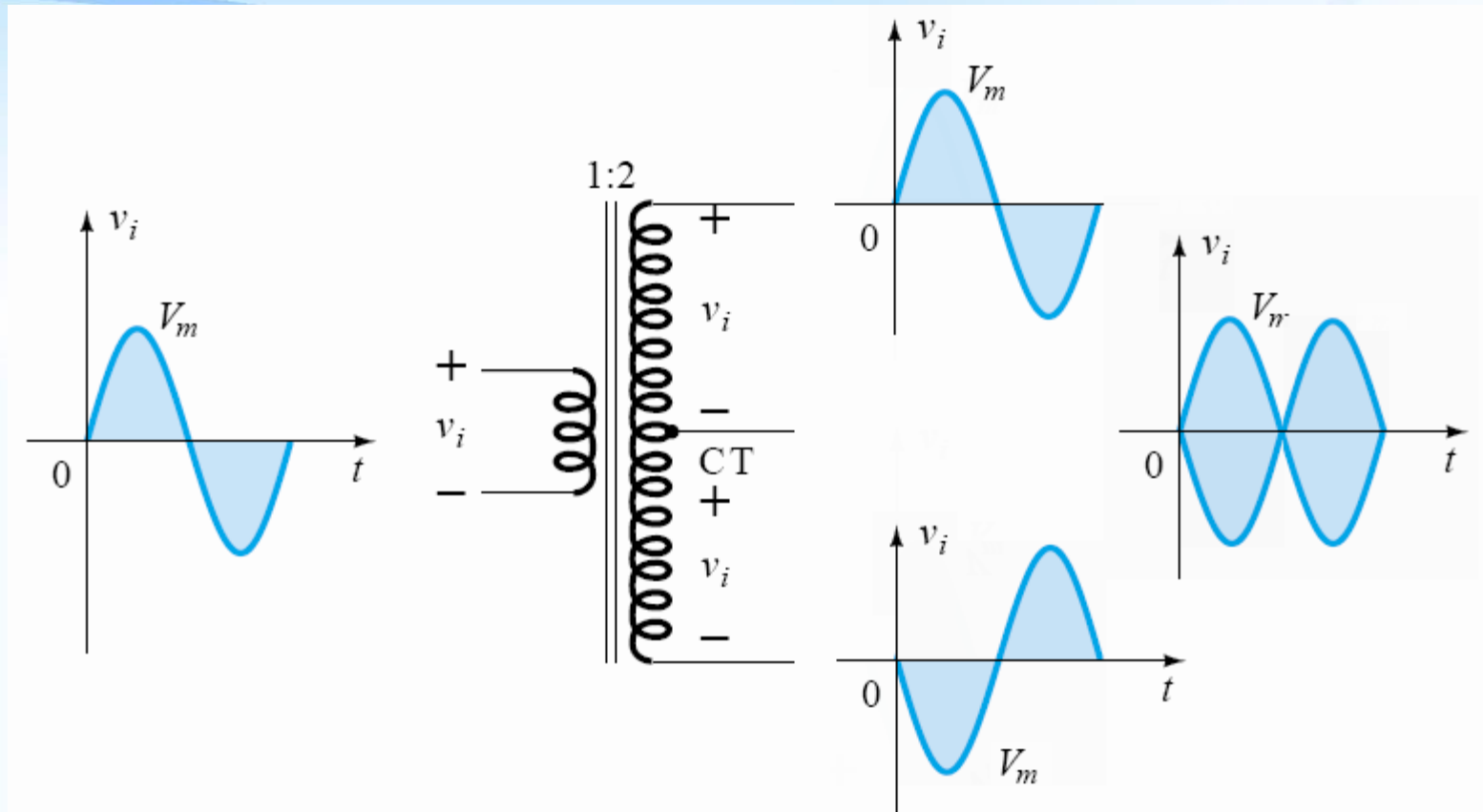



# FWR → CENTER-TAPPED TRANSFORMER

## FASE POSITIF

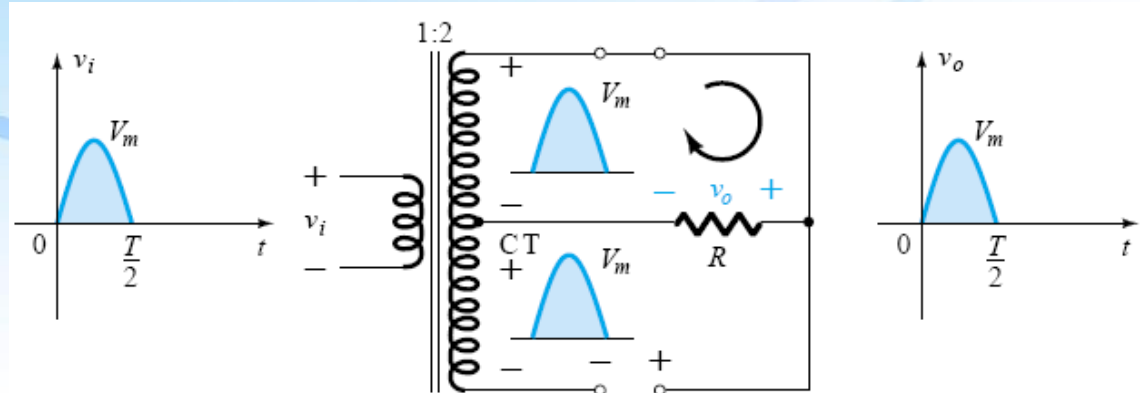

$$PIV \geq 2V_m$$

## FASE NEGATIF

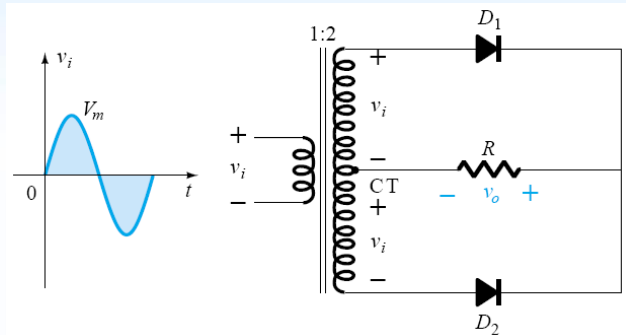
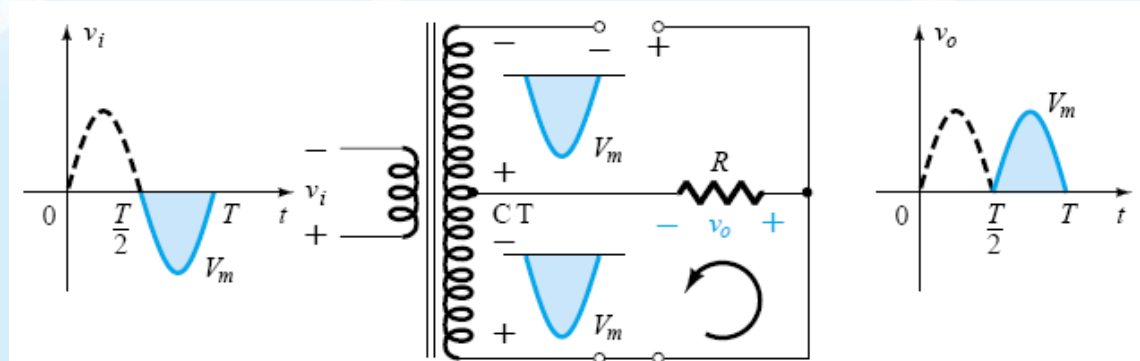







## CLIPPER

- ❑ Rangkaian clipper (pemotong) digunakan untuk memotong atau menghilangkan sebagian sinyal masukan yang berada di bawah atau di atas level tertentu.
- ❑ Rangkaian Clipper ada 2 : Seri dan Paralel
- ❑ Rangkaian clipper seri berarti diodanya berhubungan secara seri dengan beban,
- ❑ Rangkaian Clipper paralel berarti diodanya dipasang paralel dengan beban.



# SERIES CLIPPER

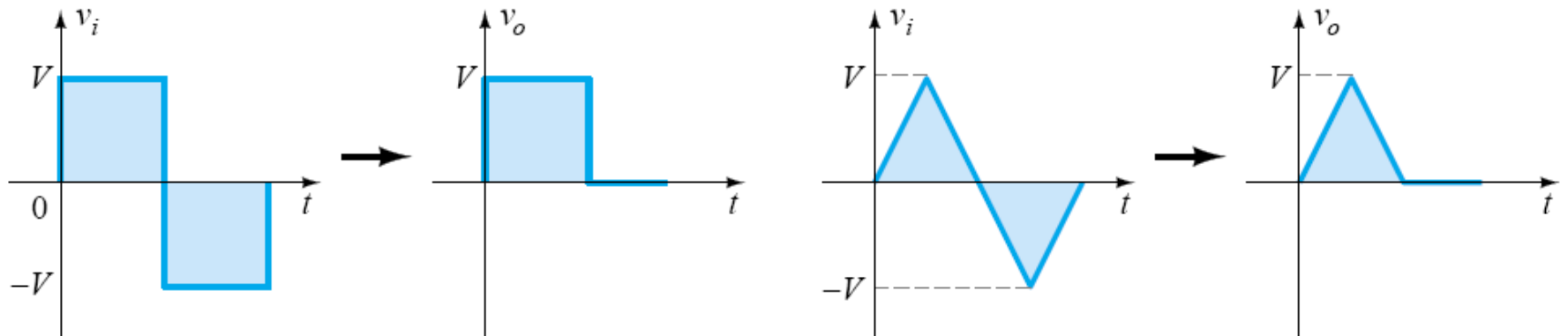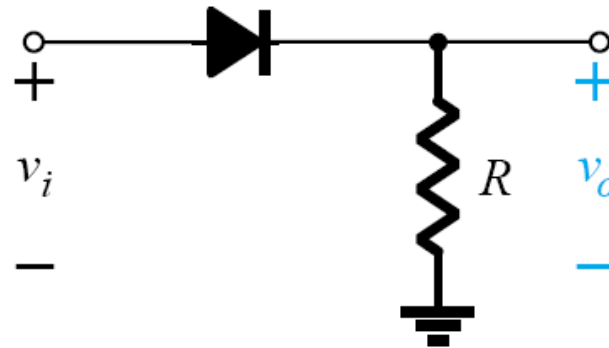



# SERIES CLIPPER

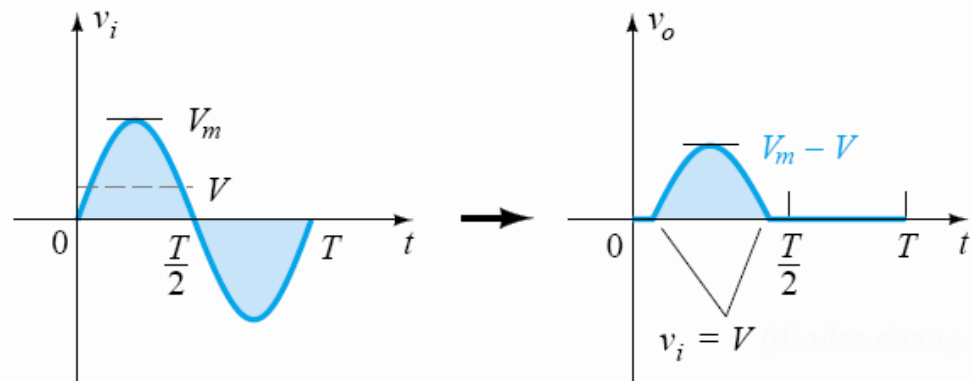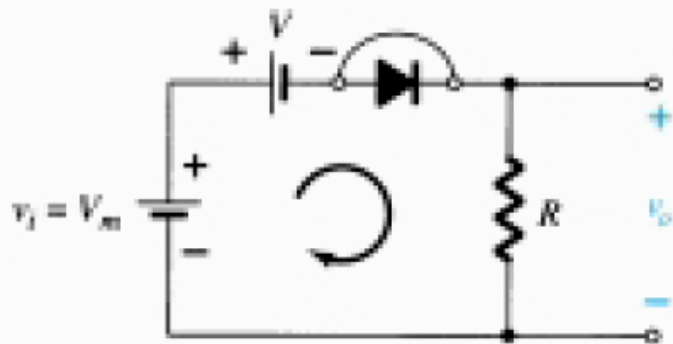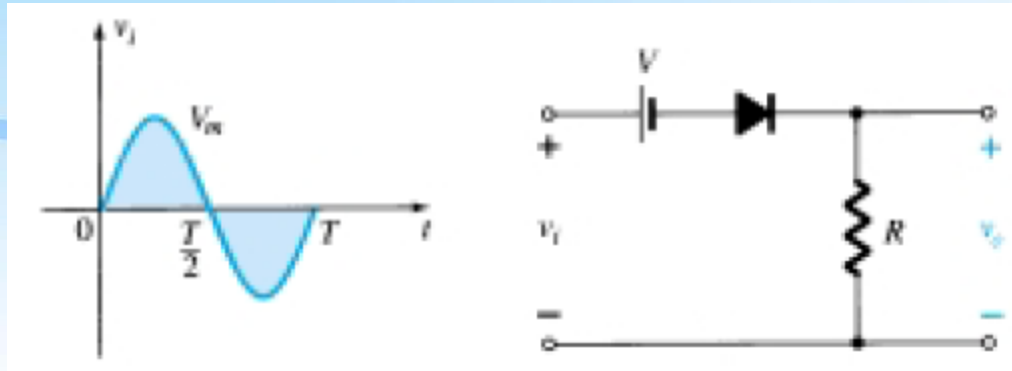

# SERIES CLIPPER


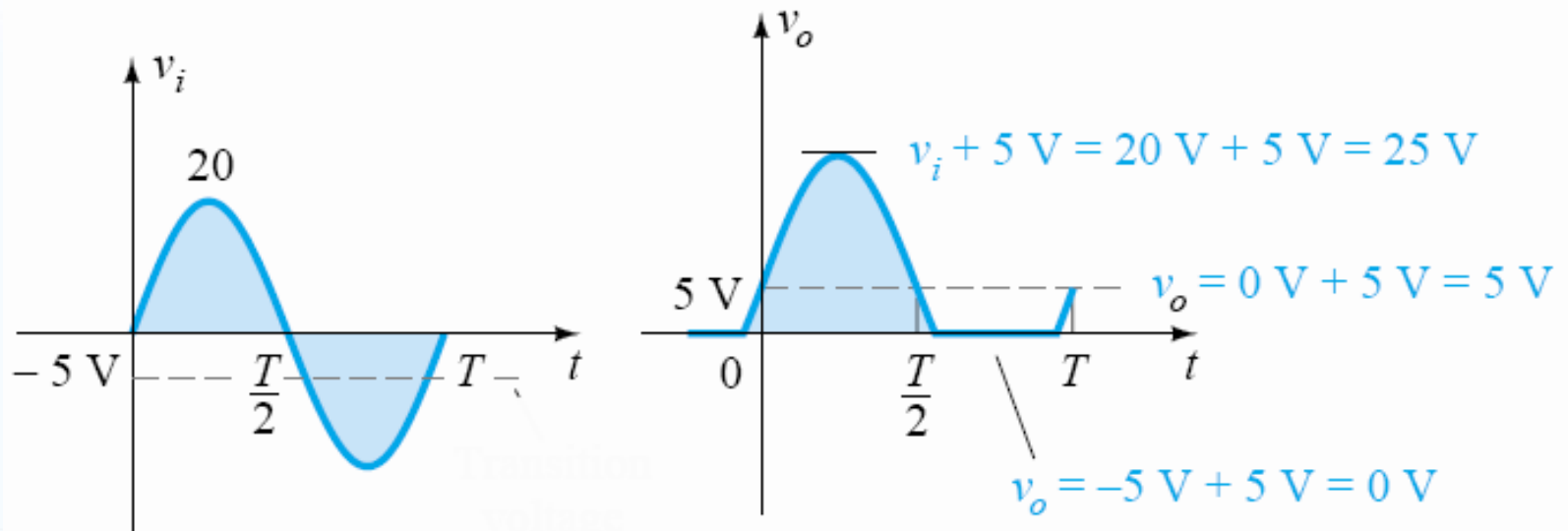
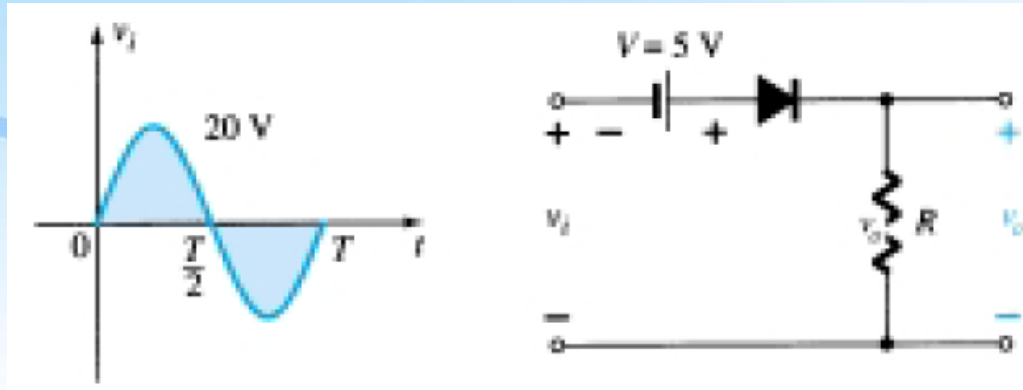


# SERIES CLIPPER


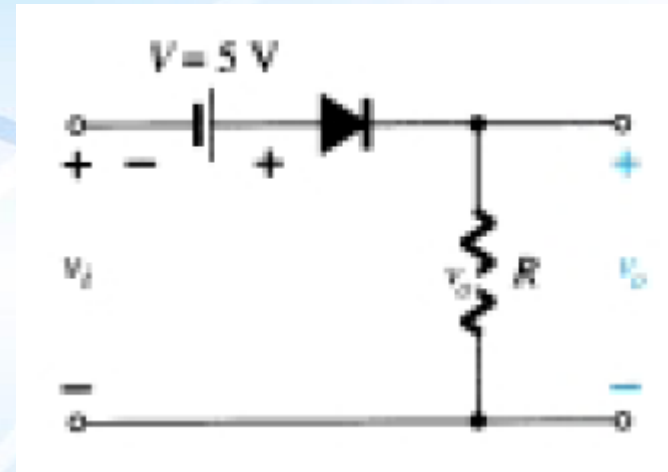
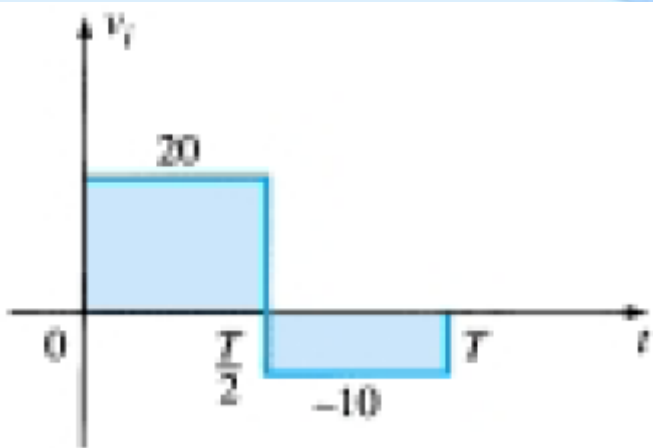


# PARALEL CLIPPER

PENDEKATAN DENGAN DIODA IDEAL

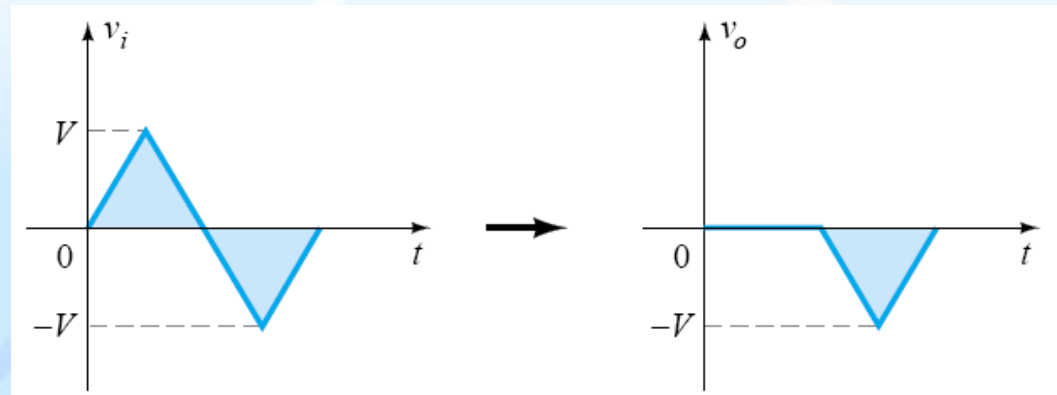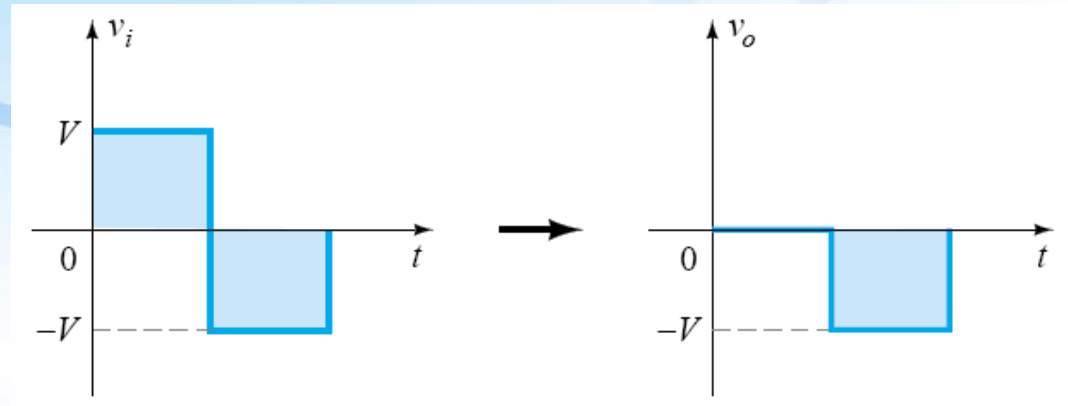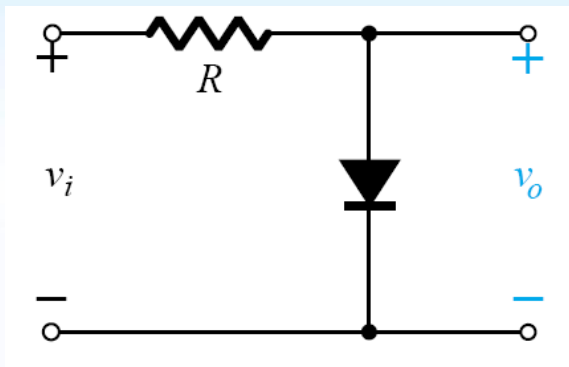


# PARALEL CLIPPER

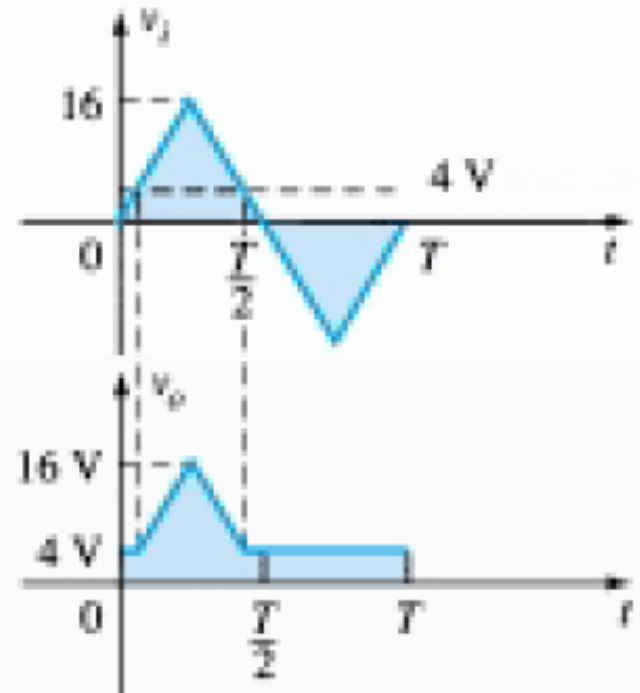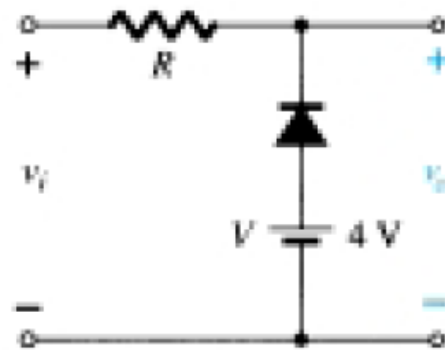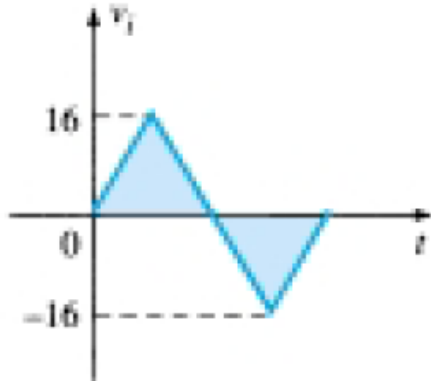


# CLIPPER

## Simple Series Clippers (Ideal Diodes)

POSITIVE

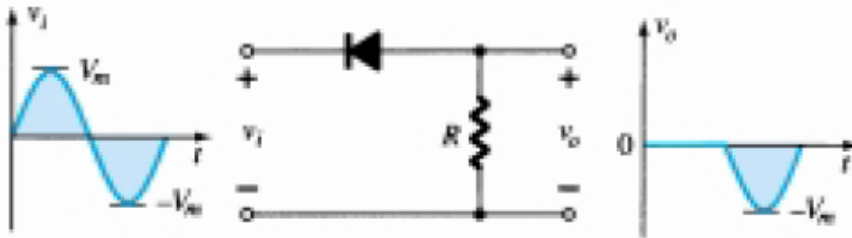


NEGATIVE

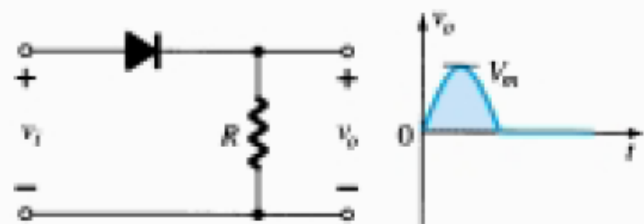


## Biased Series Clippers (Ideal Diodes)

POSITIVE

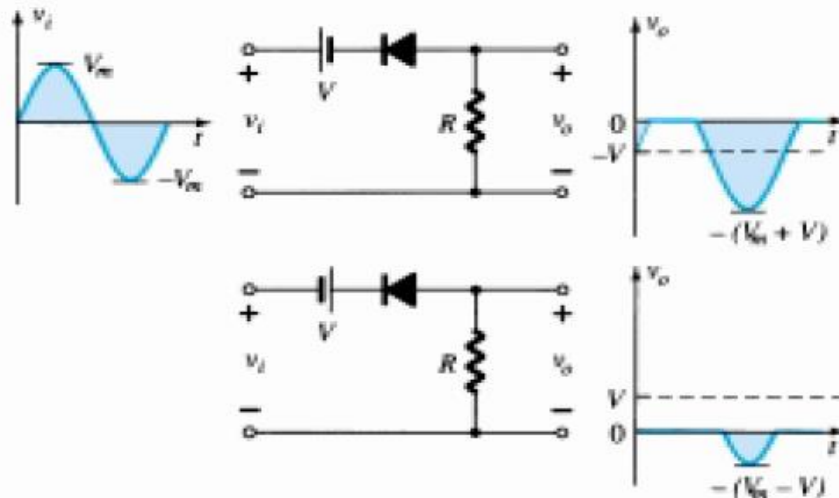


NEGATIVE

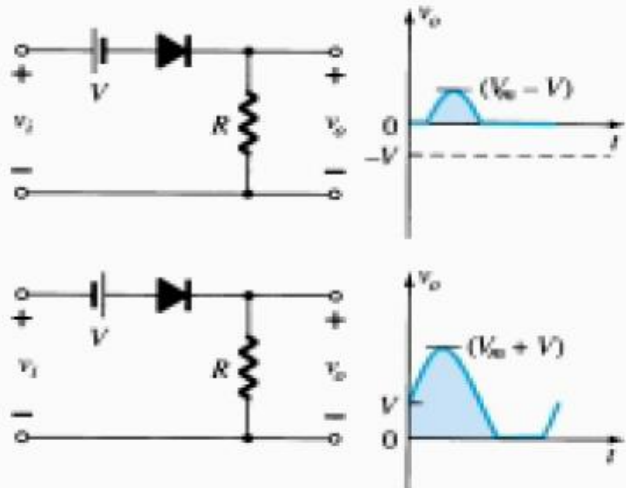




# CLIPPER

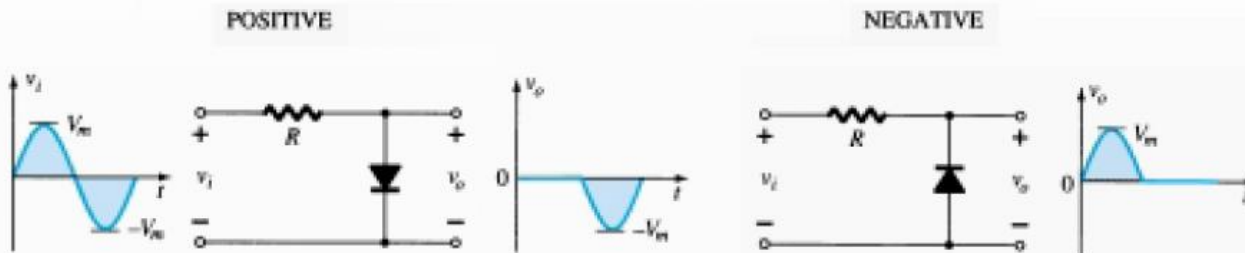
## Simple Parallel Clippers (Ideal Diodes)


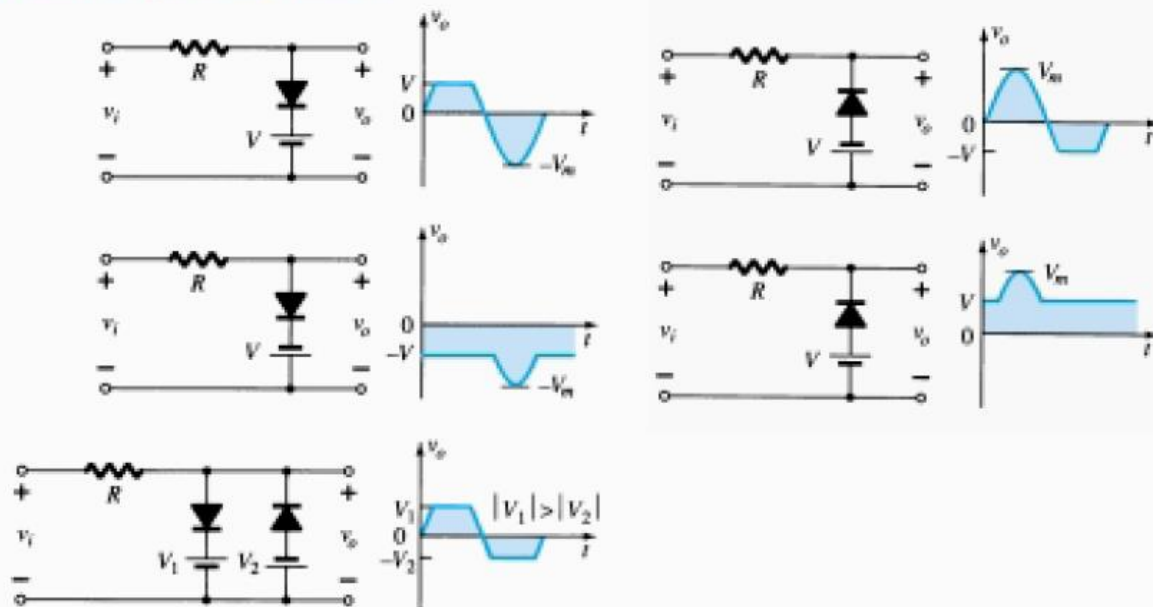
## Biased Parallel Clippers (Ideal Diodes)



## CLAMPERS

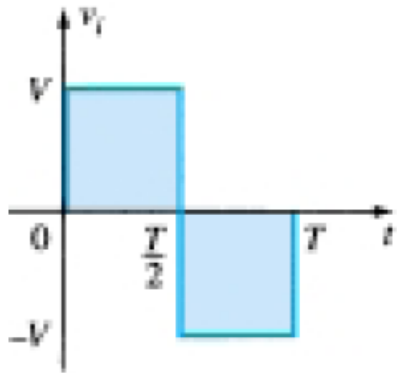

$$0 \rightarrow T/2$$







$$v_o = 0 \text{ V.}$$

$$T/2 \rightarrow T,$$






$$-V - V - v_o = 0$$

$$v_o = -2V$$

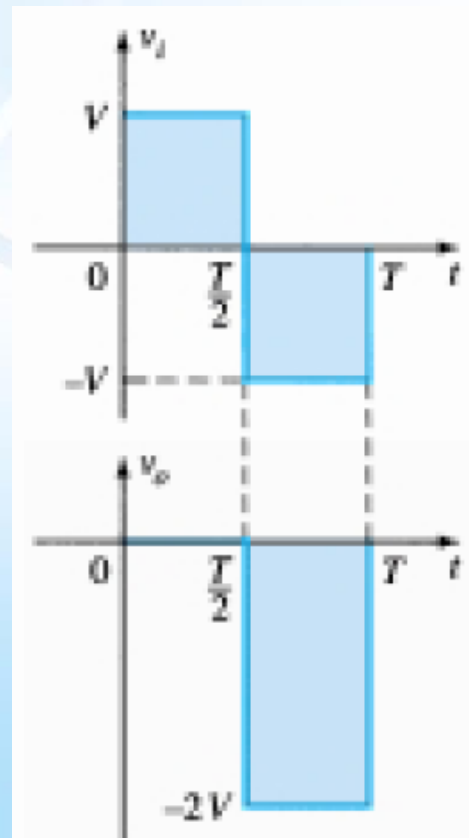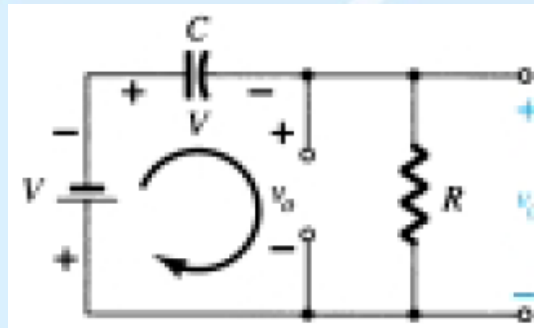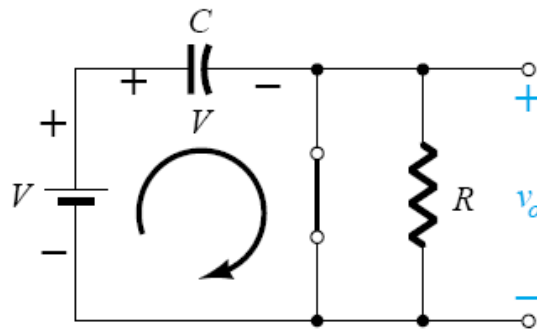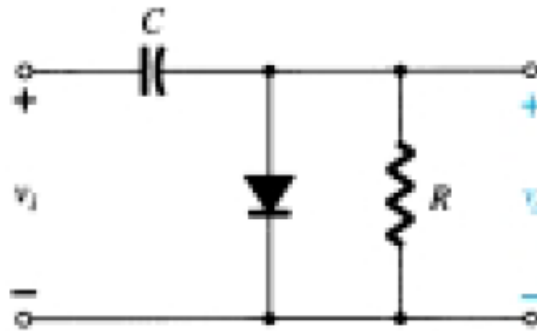


## CLAMPERS

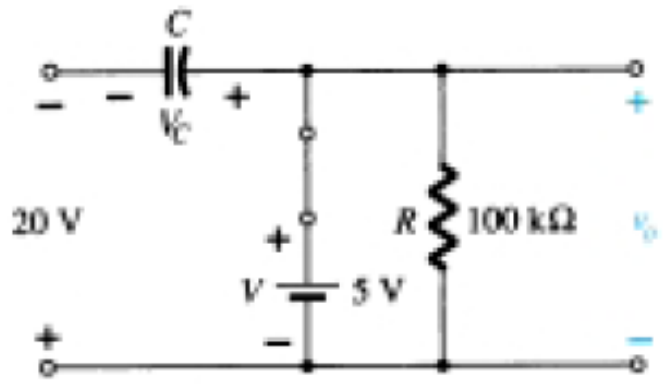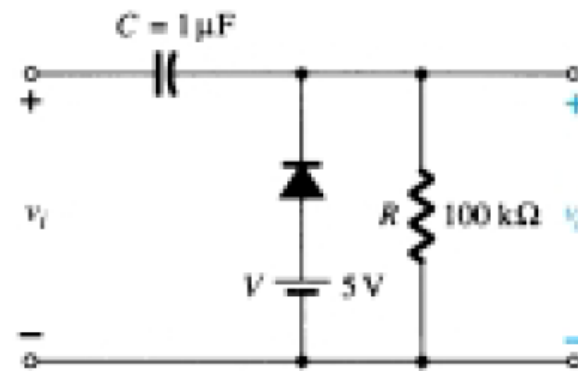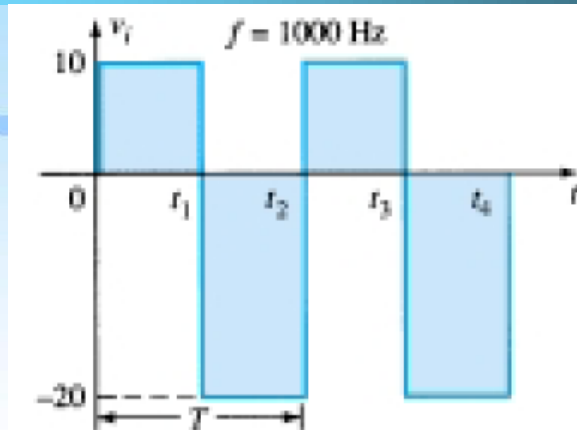

$$-20 \text{ V} + V_C - 5 \text{ V} = 0$$



$$V_C = 25 \text{ V}$$

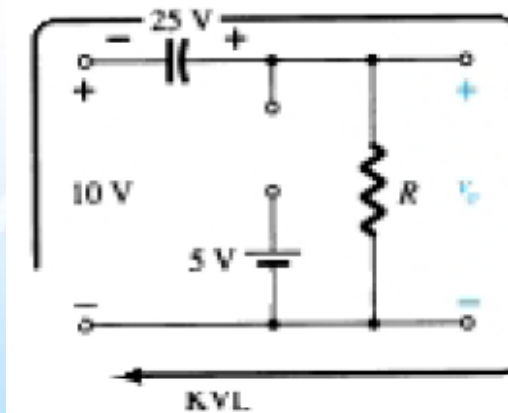

$$+10 \text{ V} + 25 \text{ V} - v_o = 0$$

$$v_o = 35 \text{ V}$$


# CLAMPERS

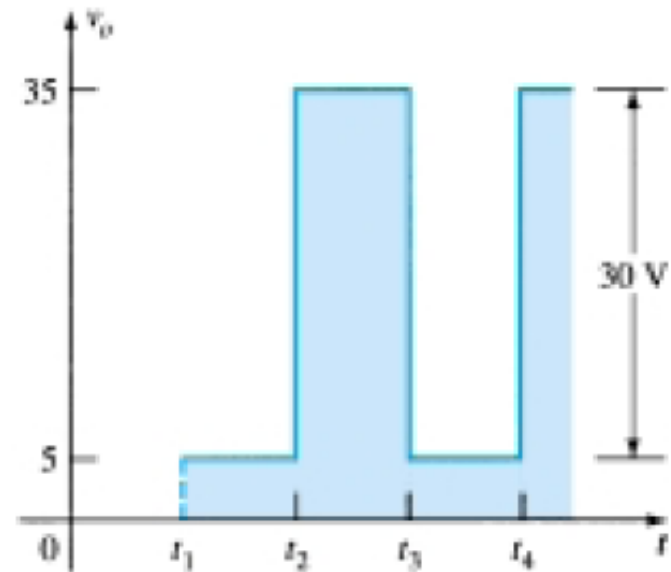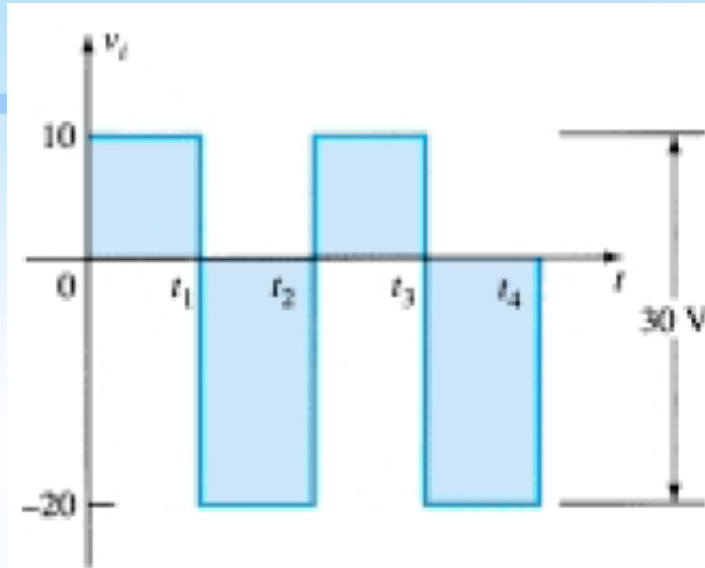



$$\tau = RC = (100 \text{ k}\Omega)(0.1 \text{ }\mu\text{F}) = 0.01 \text{ s} = 10 \text{ ms}$$

$$5\tau = 5(10 \text{ ms}) = 50 \text{ ms.}$$



## CLAMPERS

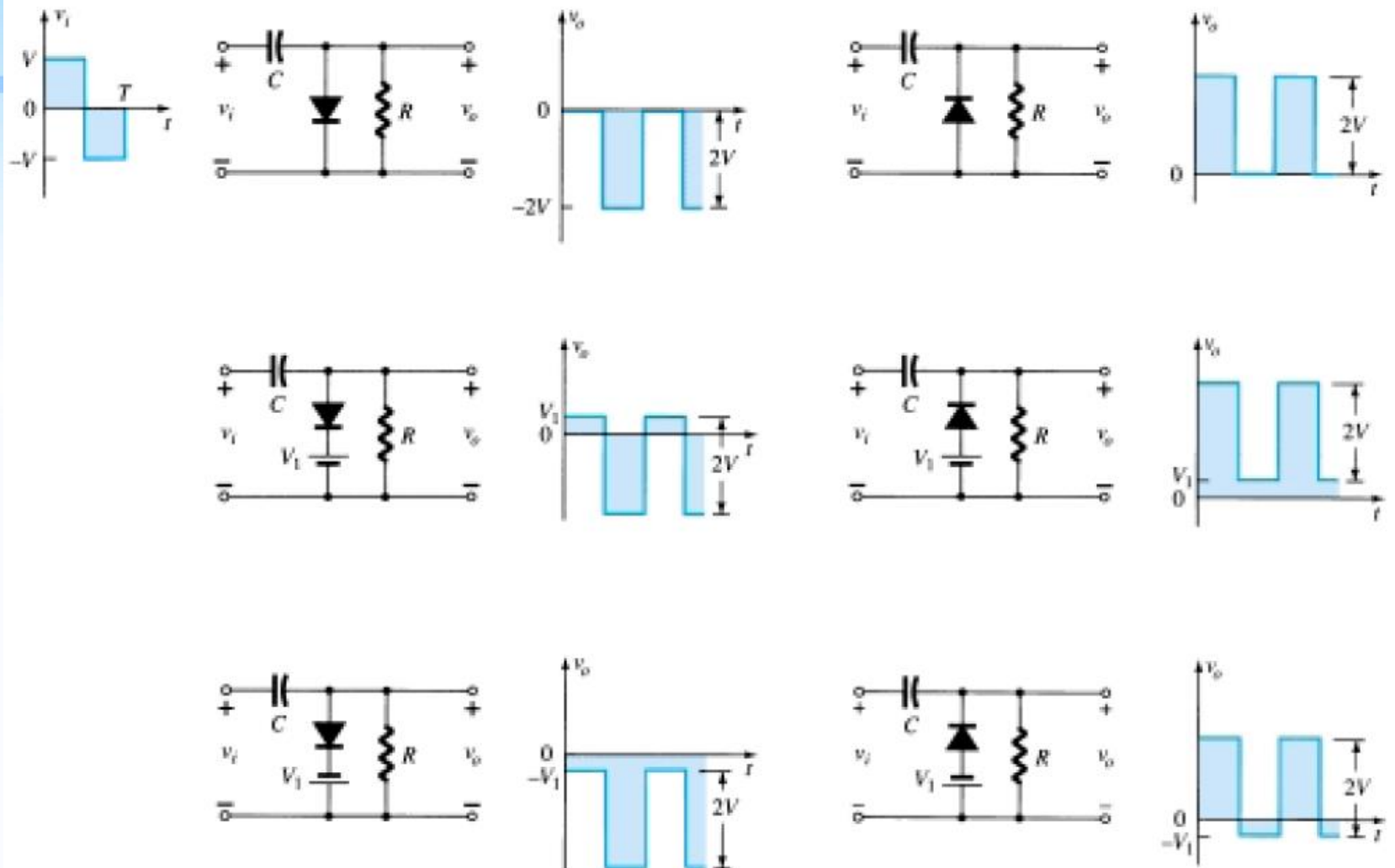

# CLAMPERS

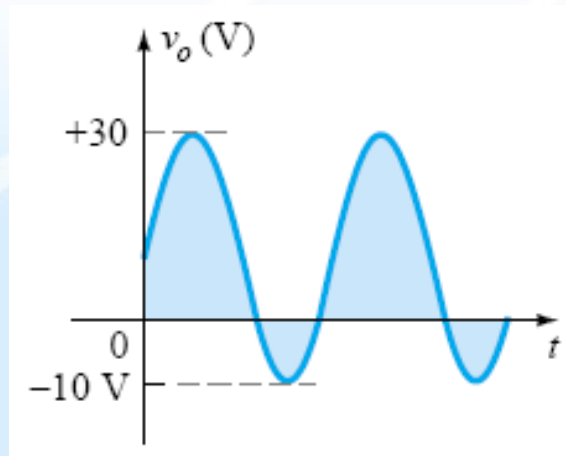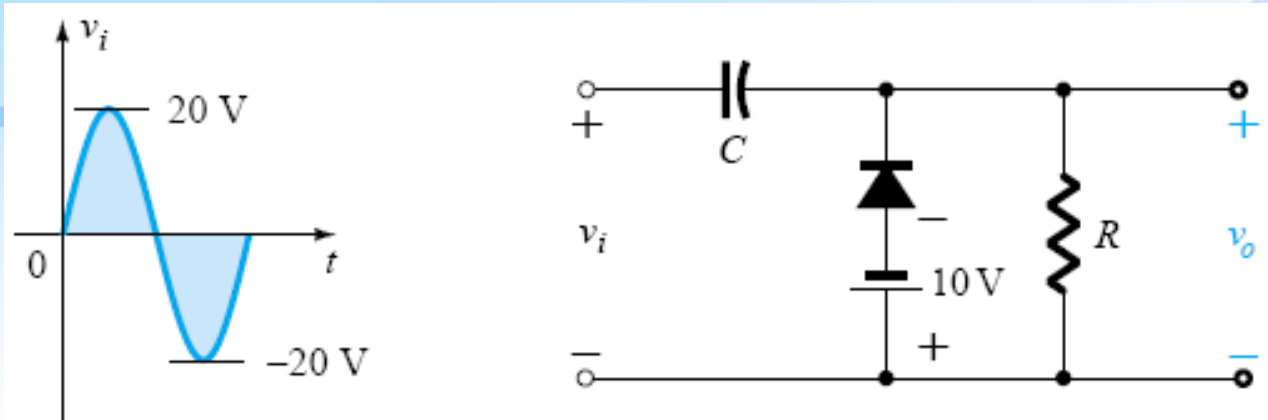


# DIODA ZENER

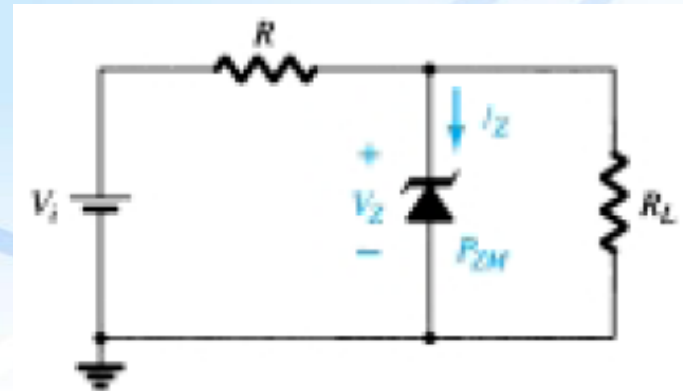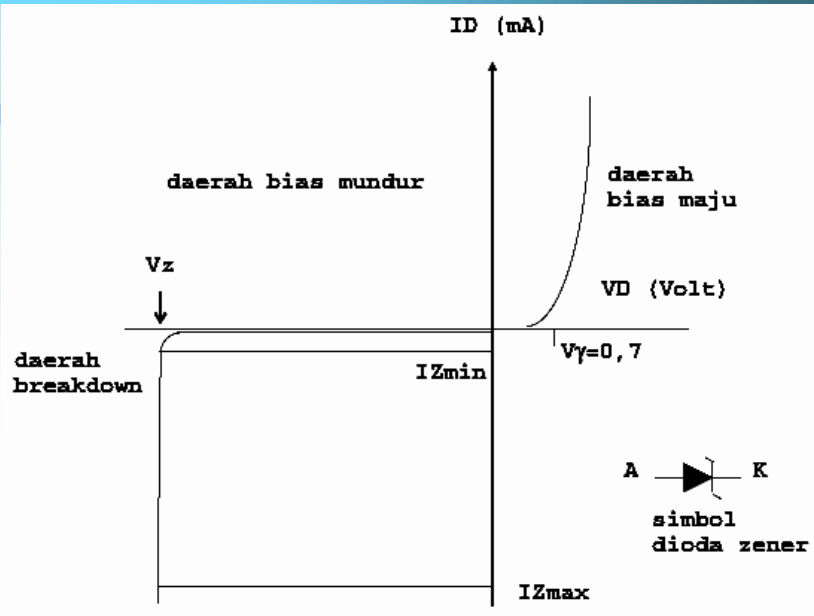

- ❑  $R_L$  harus lebih besar dari  $R_L$  minimum  $\rightarrow$   $R_L$  minimum, maka  $I_L$  menjadi maksimum, sehingga  $I_Z$  menjadi minimum.
- ❑  $V_i$  harus lebih besar dari  $V_i$  minimum  $\rightarrow$   $V_i$  minimum akan menjamin bahwa dioda mendapatkan tegangan *breakdown*.

## Contoh

- (a) For the Zener diode network of Fig. 2.109, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ .  
 (b) Repeat part (a) with  $R_L = 3 \text{ k}\Omega$ .

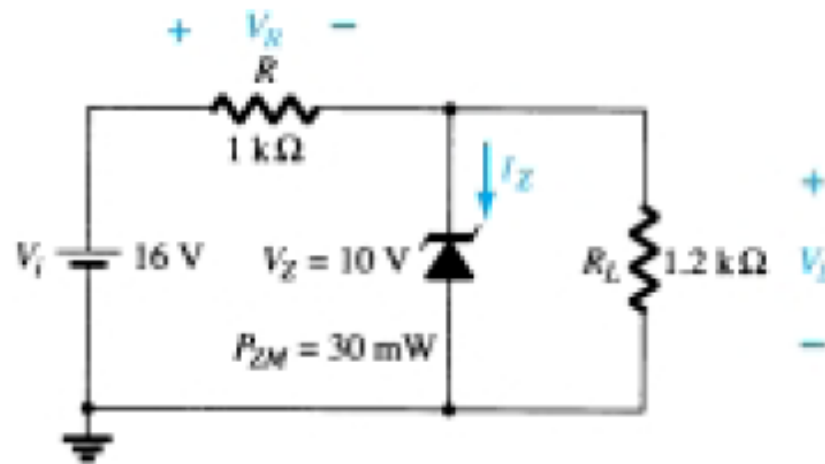


**Figure 2.109** Zener diode regulator for Example 2.26.

### Solution

- (a) Following the suggested procedure the network is redrawn as shown in Fig. 2.110. Applying Eq. (2.16) gives

$$V = \frac{R_L V_i}{R + R_L} = \frac{1.2 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 8.73 \text{ V}$$



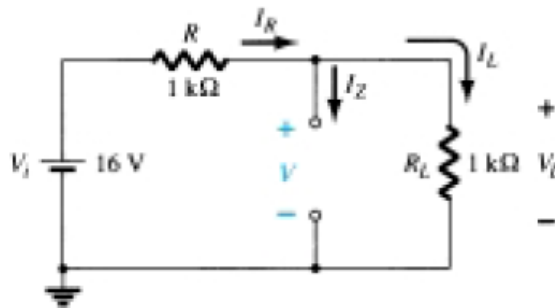

**Figure 2.110** Determining  $V$  for the regulator of Fig. 2.109.

Since  $V = 8.73 \text{ V}$  is less than  $V_Z = 10 \text{ V}$ , the diode is in the “off” state as shown on the characteristics of Fig. 2.111. Substituting the open-circuit equivalent will result in the same network as in Fig. 2.110, where we find that

$$V_L = V = 8.73 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 8.73 \text{ V} = 7.27 \text{ V}$$

$$I_Z = 0 \text{ A}$$

and

$$P_Z = V_Z I_Z = V_Z (0 \text{ A}) = 0 \text{ W}$$

(b) Applying Eq. (2.16) will now result in

$$V = \frac{R_L V_i}{R + R_L} = \frac{3 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 12 \text{ V}$$

Since  $V = 12 \text{ V}$  is greater than  $V_Z = 10 \text{ V}$ , the diode is in the “on” state and the network of Fig. 2.112 will result. Applying Eq. (2.17) yields


$$V_L = V_Z = 10 \text{ V}$$

and

$$V_R = V_i - V_L = 16 \text{ V} - 10 \text{ V} = 6 \text{ V}$$

with

$$I_L = \frac{V_L}{R_L} = \frac{10 \text{ V}}{3 \text{ k}\Omega} = 3.33 \text{ mA}$$

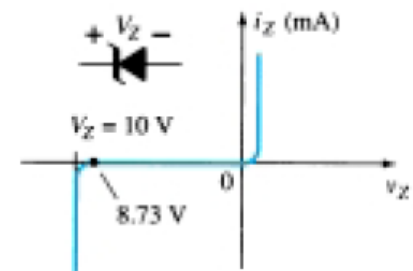

**Figure 2.111** Resulting operating point for the network of Fig. 2.109.

and 
$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$

so that 
$$I_Z = I_R - I_L \text{ [Eq. (2.18)]}$$
$$= 6 \text{ mA} - 3.33 \text{ mA}$$
$$= \mathbf{2.67 \text{ mA}}$$

The power dissipated,

$$P_Z = V_Z I_Z = (10 \text{ V})(2.67 \text{ mA}) = \mathbf{26.7 \text{ mW}}$$

which is less than the specified  $P_{ZM} = 30 \text{ mW}$ .

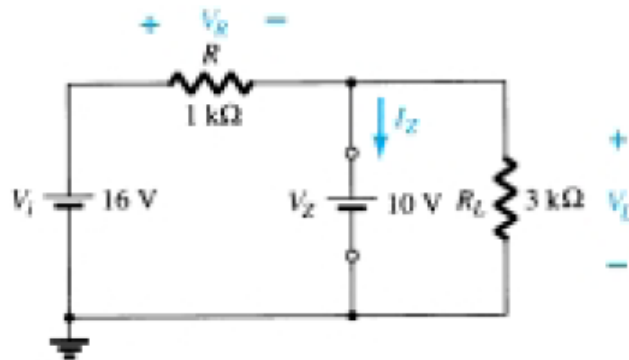


Figure 2.112 Network of Fig. 2.109 in the “on” state.

## CONTOH

Determine the current  $I$  for the network of Fig. 2.32.

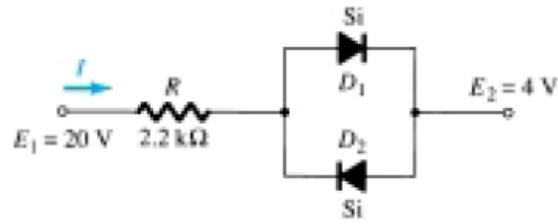


Figure 2.32 Network for Example 2.13.

## Solution

Redrawing the network as shown in Fig. 2.33 reveals that the resulting current direction is such as to turn on diode  $D_1$  and turn off diode  $D_2$ . The resulting current  $I$  is then

$$I = \frac{E_1 - E_2 - V_D}{R} = \frac{20 \text{ V} - 4 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega} \approx 6.95 \text{ mA}$$

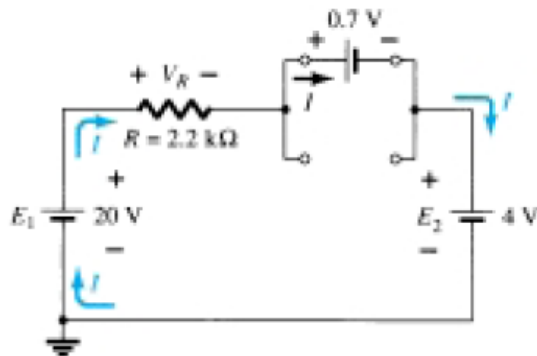


Figure 2.33 Determining the unknown quantities for the network of Example 2.13.

## CONTOH

Determine  $V_o$ ,  $I_1$ ,  $I_{D_1}$ , and  $I_{D_2}$  for the parallel diode configuration of Fig. 2.30.

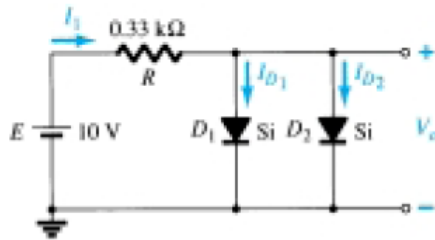


Figure 2.30 Network for Example 2.12.

## Solution

For the applied voltage the “pressure” of the source is to establish a current through each diode in the same direction as shown in Fig. 2.31. Since the resulting current direction matches that of the arrow in each diode symbol and the applied voltage is greater than 0.7 V, both diodes are in the “on” state. The voltage across parallel elements is always the same and

$$V_o = 0.7 \text{ V}$$

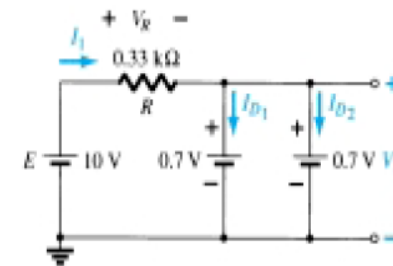


Figure 2.31 Determining the unknown quantities for the network of Example 2.12.



The current

$$I_1 = \frac{V_R}{R} = \frac{E - V_D}{R} = \frac{10 \text{ V} - 0.7 \text{ V}}{0.33 \text{ k}\Omega} = 28.18 \text{ mA}$$

Assuming diodes of similar characteristics, we have

$$I_{D_1} = I_{D_2} = \frac{I_1}{2} = \frac{28.18 \text{ mA}}{2} = 14.09 \text{ mA}$$

## CONTOH

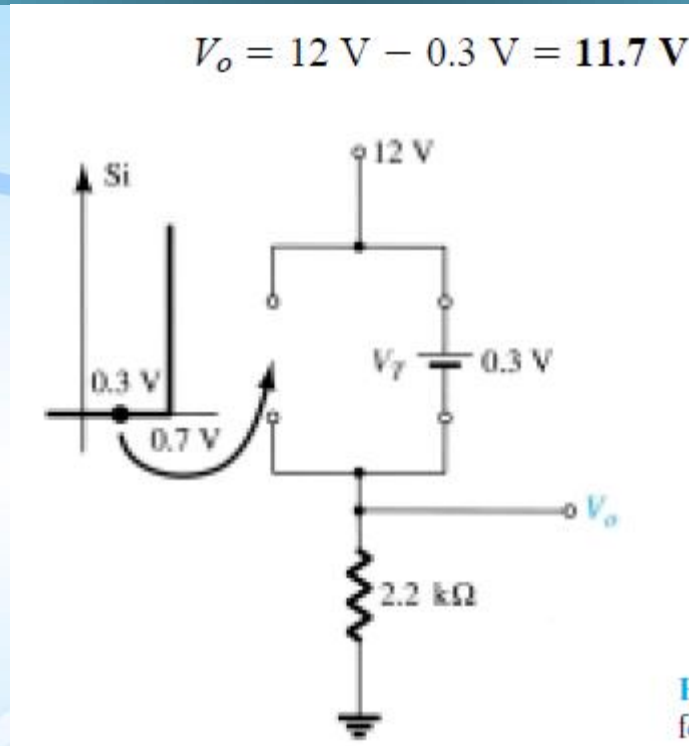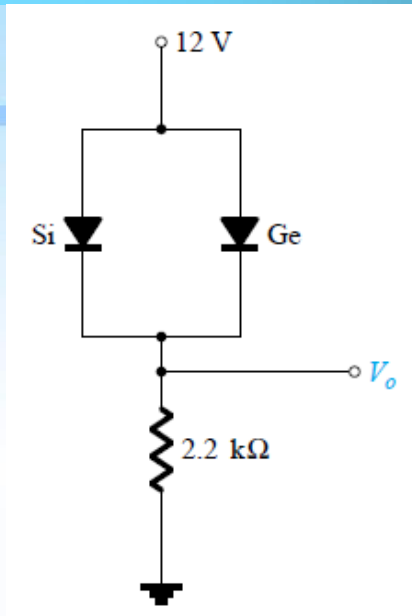

# CONTOH